

The Ideal Diode



Forward Bias

When Forward Biased

- The diode will have no resistance
- The diode will have no control over the current through it.
- The diode will have no voltage drop across its terminals.



Reverse Bias

When Reverse Biased

- The diode will have infinite resistance
- The diode will not pass current.
- The diode will drop the entire voltage across its terminals.


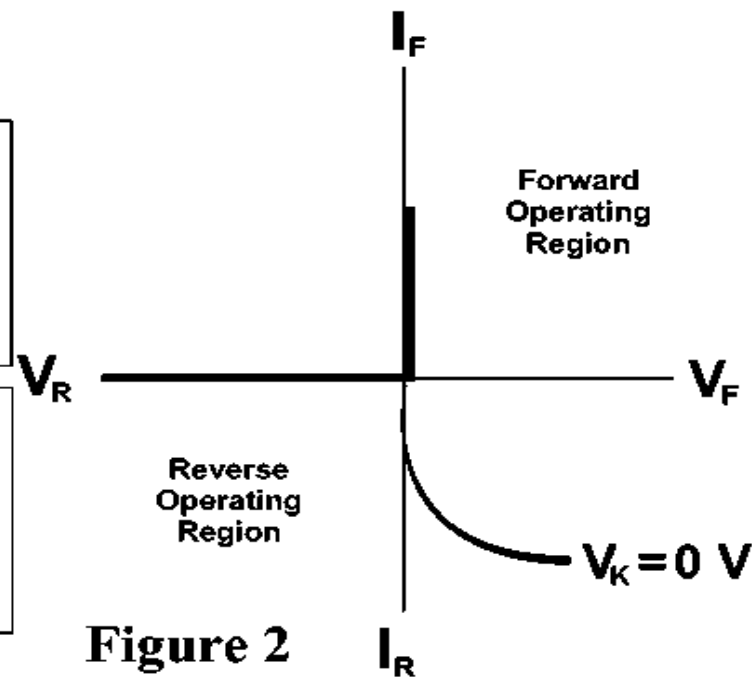


Figure 2

The Ideal Diode acts like a Switch


The Practical Diode

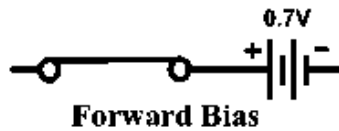

Forward Bias

Forward Biased Characteristics

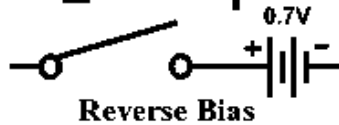- The diode current remains at zero until the knee voltage is reached.
- Once the applied voltage reaches the value of V_K , the diode turns on and forward conduction occurs
- As long as the diode is conducting, the value of V_F is approximately equal to V_K



Reverse Bias

Reverse Biased Characteristics

- The diode will have infinite resistance
- The diode will not pass current.
- The diode will drop the entire voltage across its terminals.


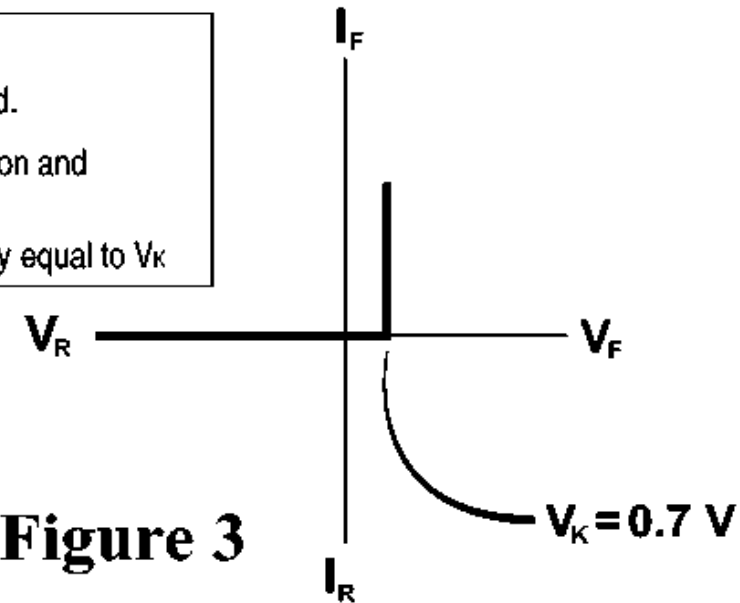


Figure 3

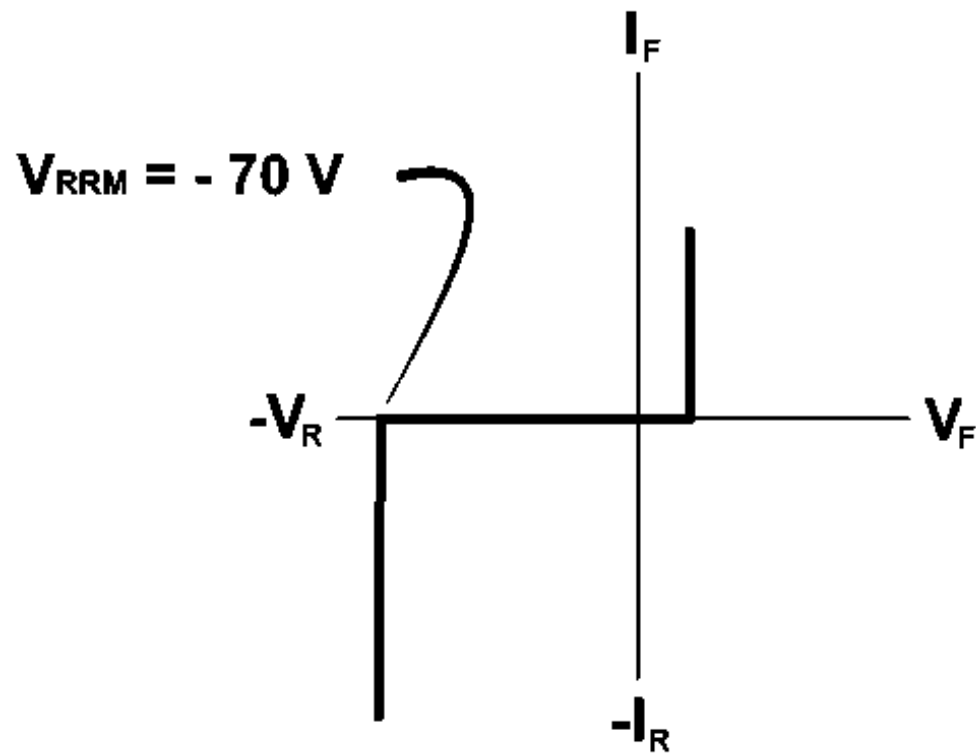


Peak Reverse Voltage (V_{RRM})

Figure 4



$$I_O = \frac{P_{D(max)}}{V_F}$$

Figure 5

$$V_{RRM} = -70 \text{ V}$$

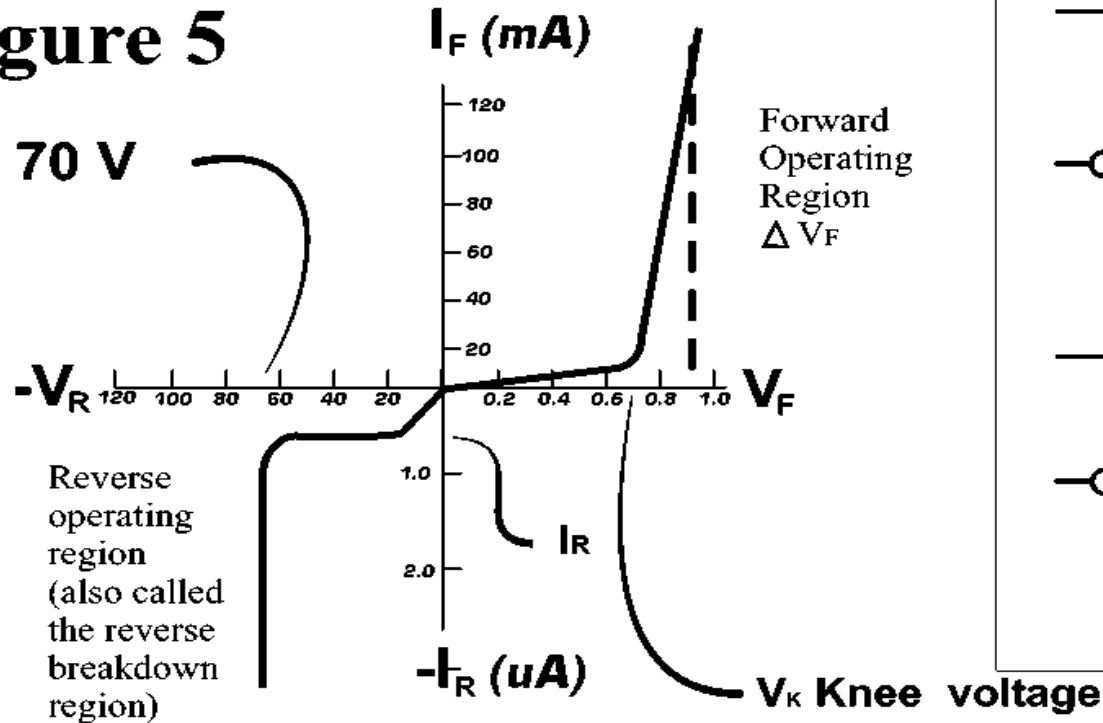

Complete Diode Model Curve

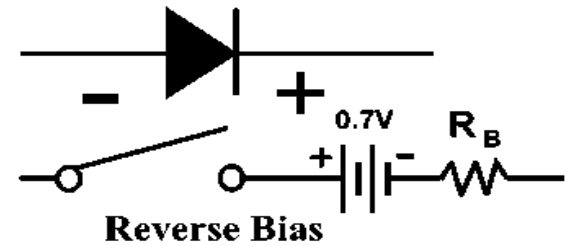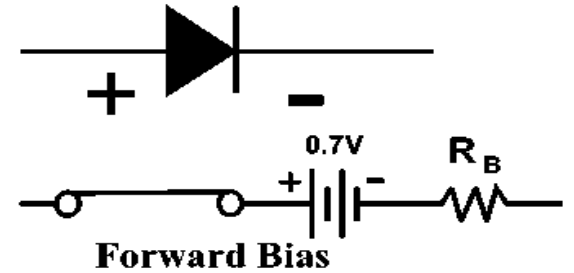

$$V_F = V_B + I_F R_B$$


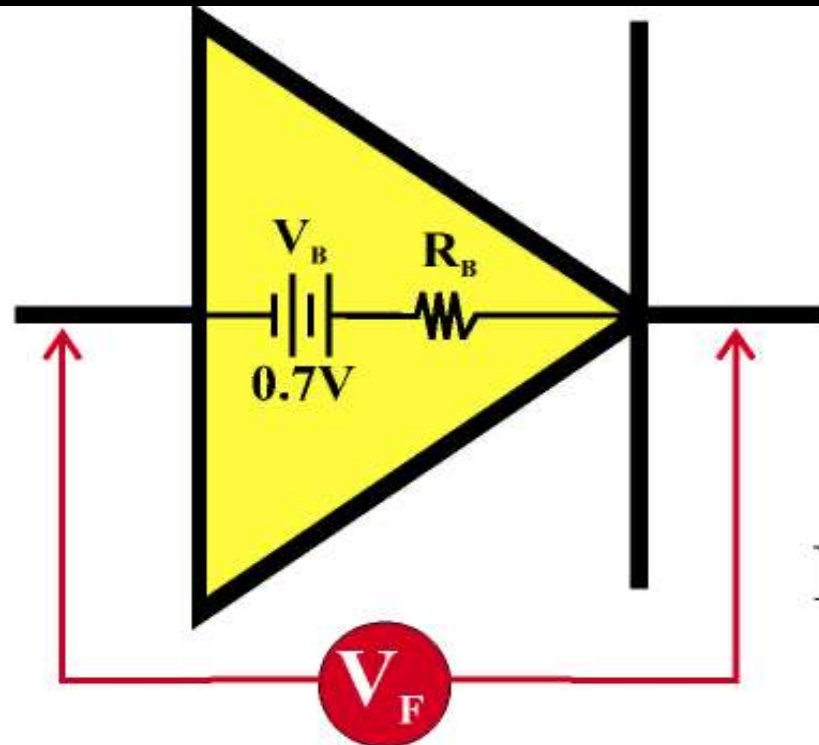


Figure 6

$$V_F = V_B + I_F R_B$$

Diode Equivalent Circuit

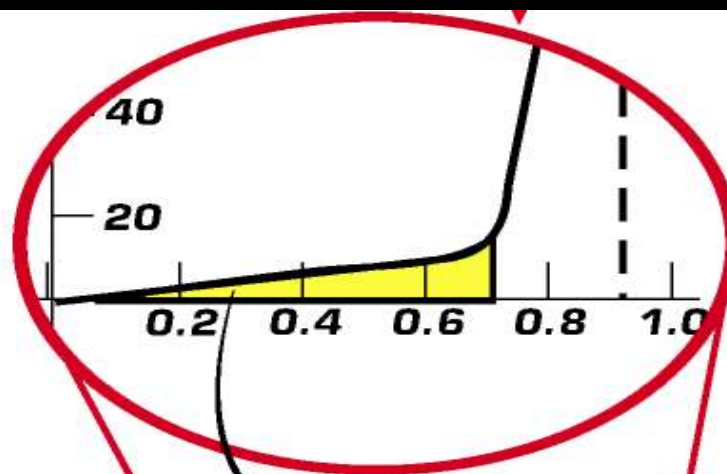

Diffusion Current
Area


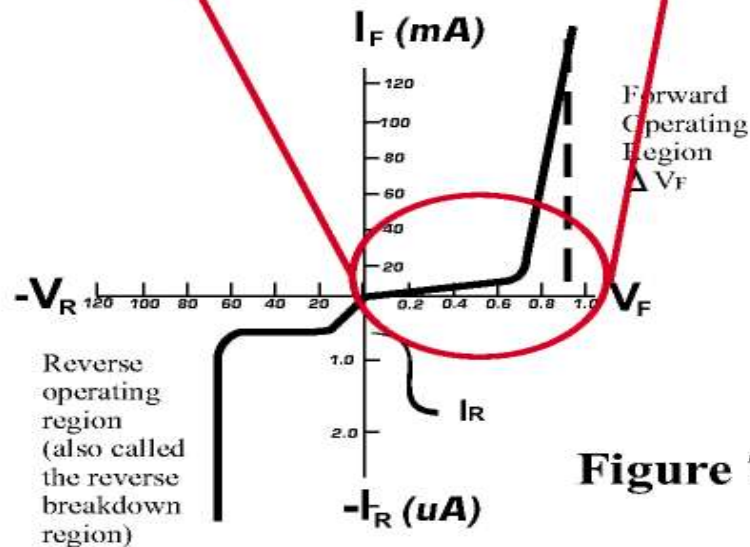
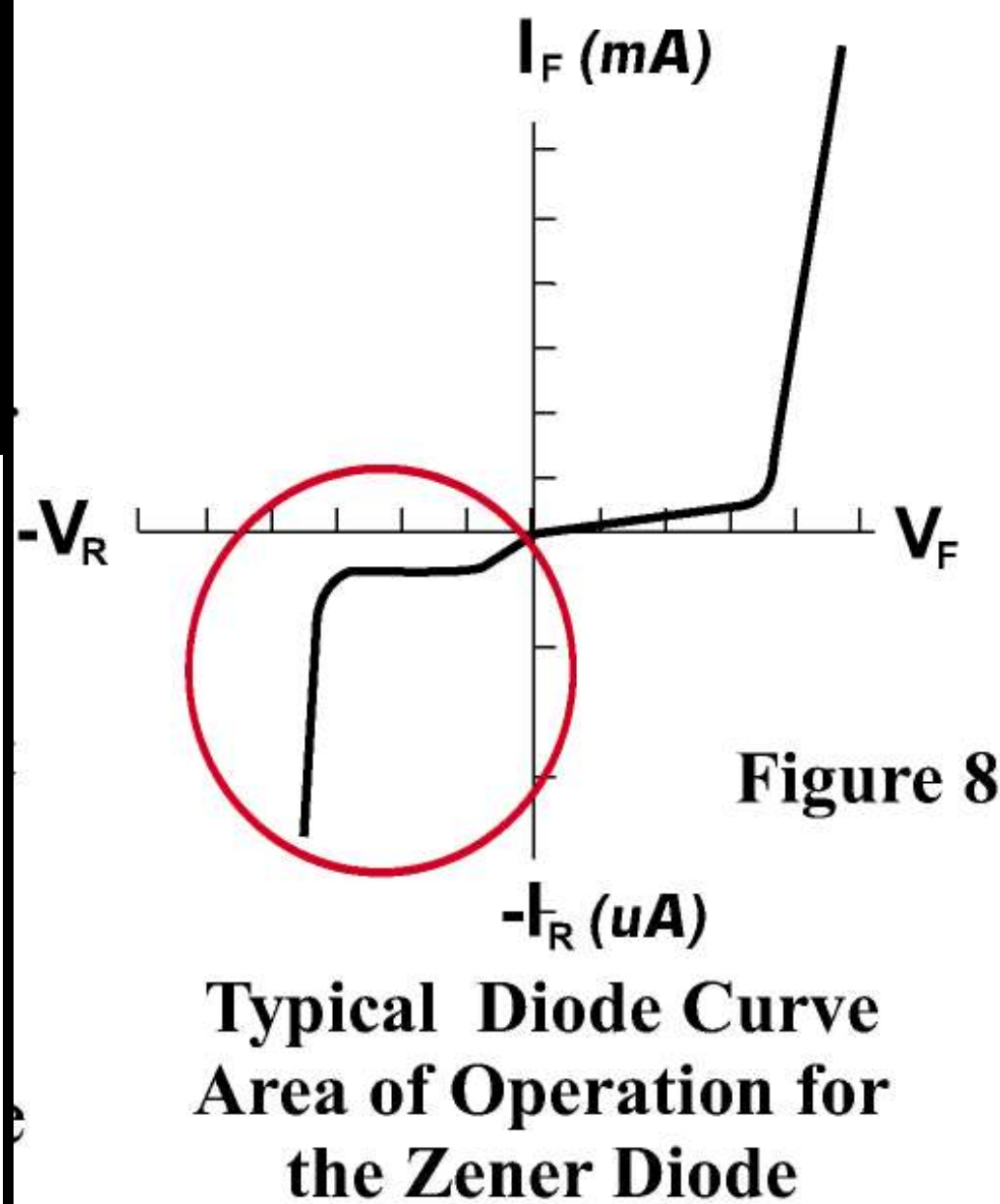


Figure 7

**Complete Diode Model Curve
Area Showing Diffusion Current**

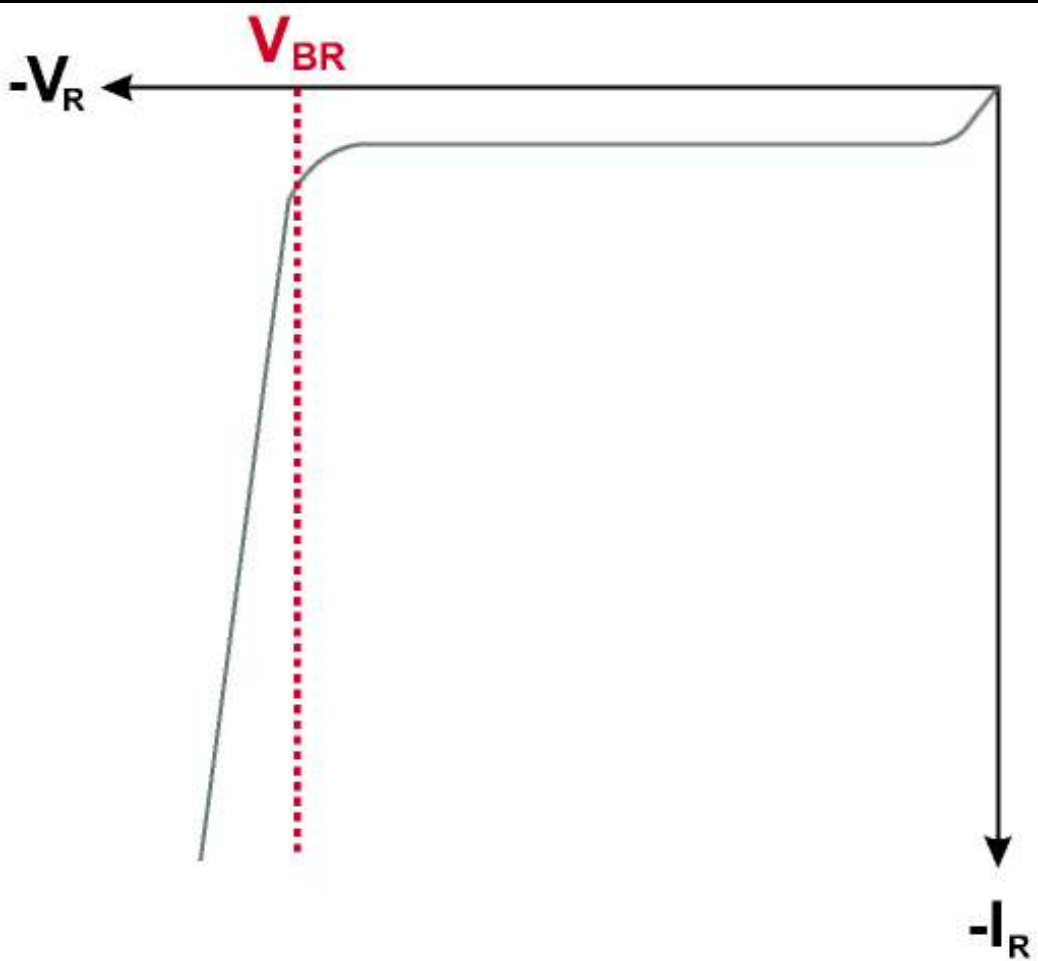

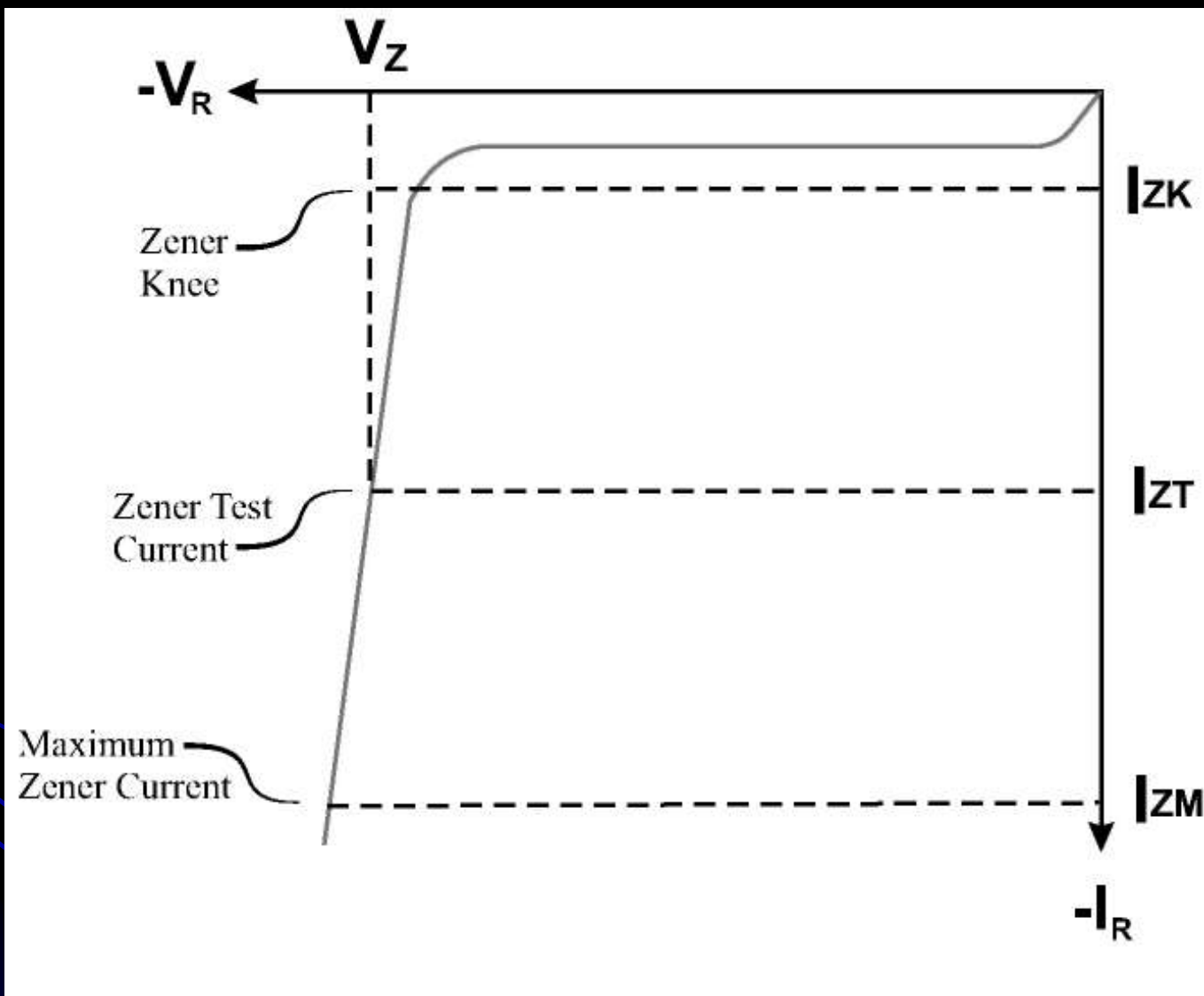


Figure 12

Figure 12

Z_Z Zener Impedance is the Zener Diode's opposition to a change in current.

$$Z_z = \frac{\Delta V_z}{\Delta I_z} \quad \Delta V_z = \text{the change in } V_z$$

$$Z_z = \frac{56 \text{ mV}}{2 \text{ mA}} = 28 \Omega$$

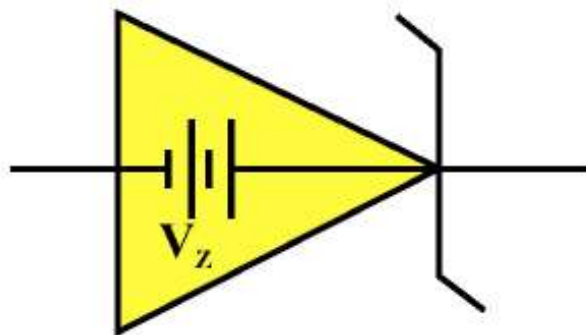
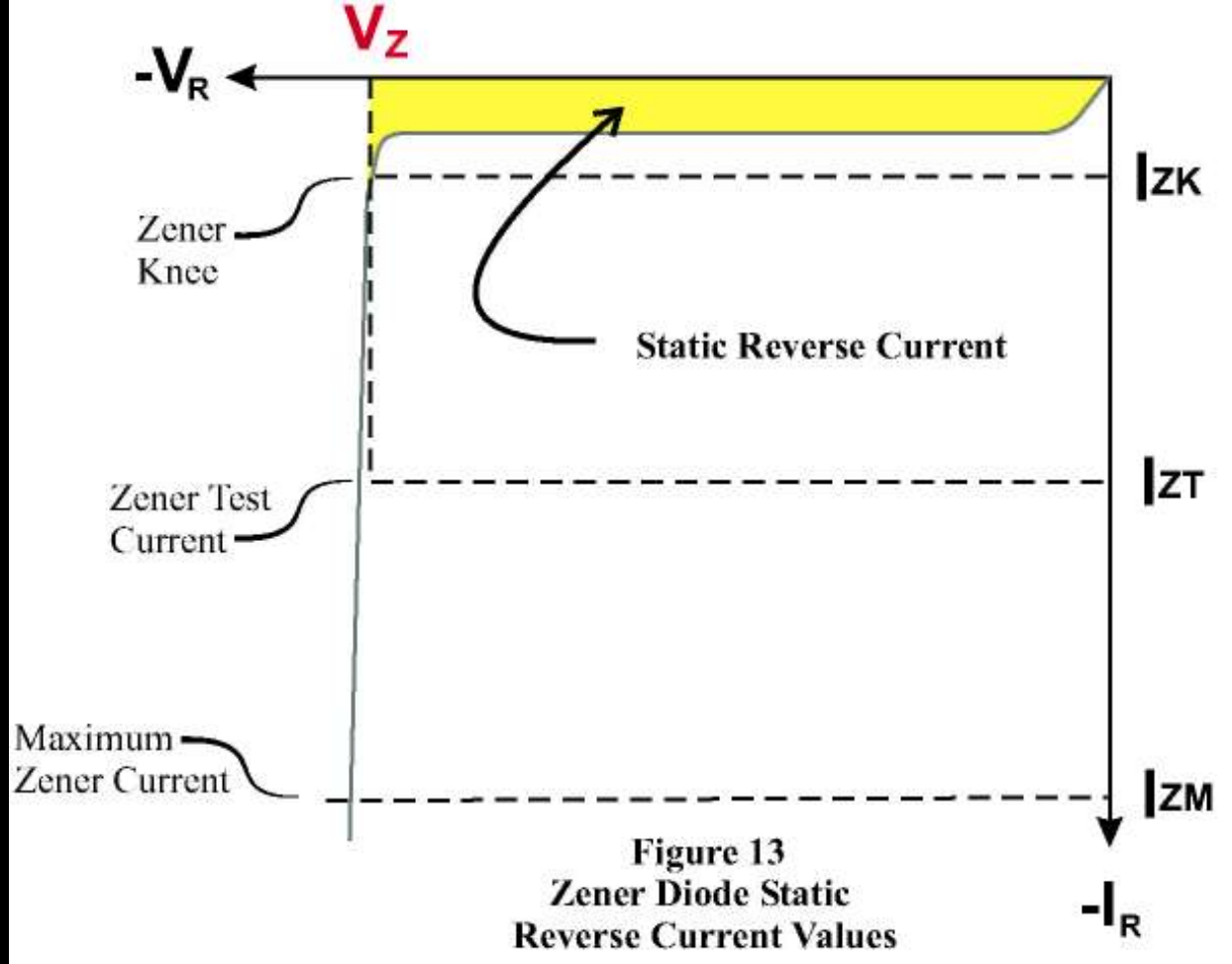


Fig. 14 (a) Ideal Zener Model

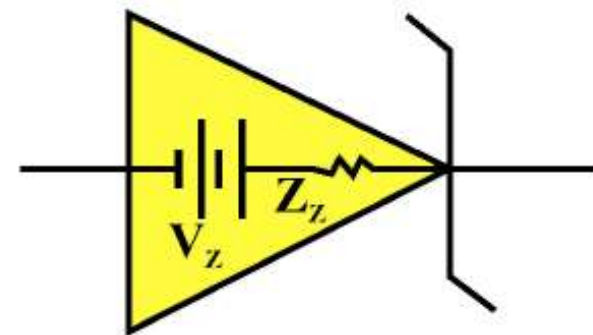


Fig. 14 (b) Practical Zener Model