

**FREE**  
**SUPPLEMENT**  
PIC TUTORIAL V2 Part 3

THE No.1 MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS


EVERYDAY

Vol.32 No.6

# PRACTICAL ELECTRONICS

CAN \$6.99/US \$4.95

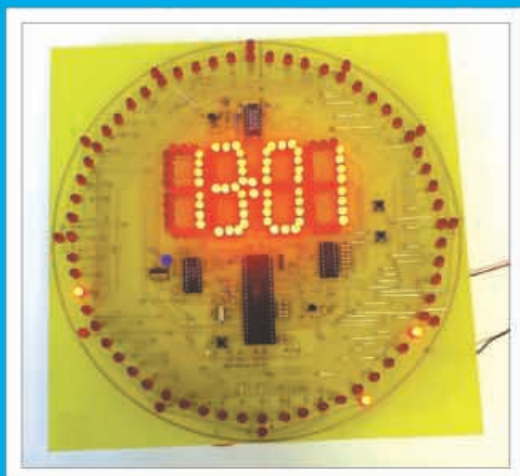
## PICRONOS LED Wall Clock/ Calendar/ Thermometer


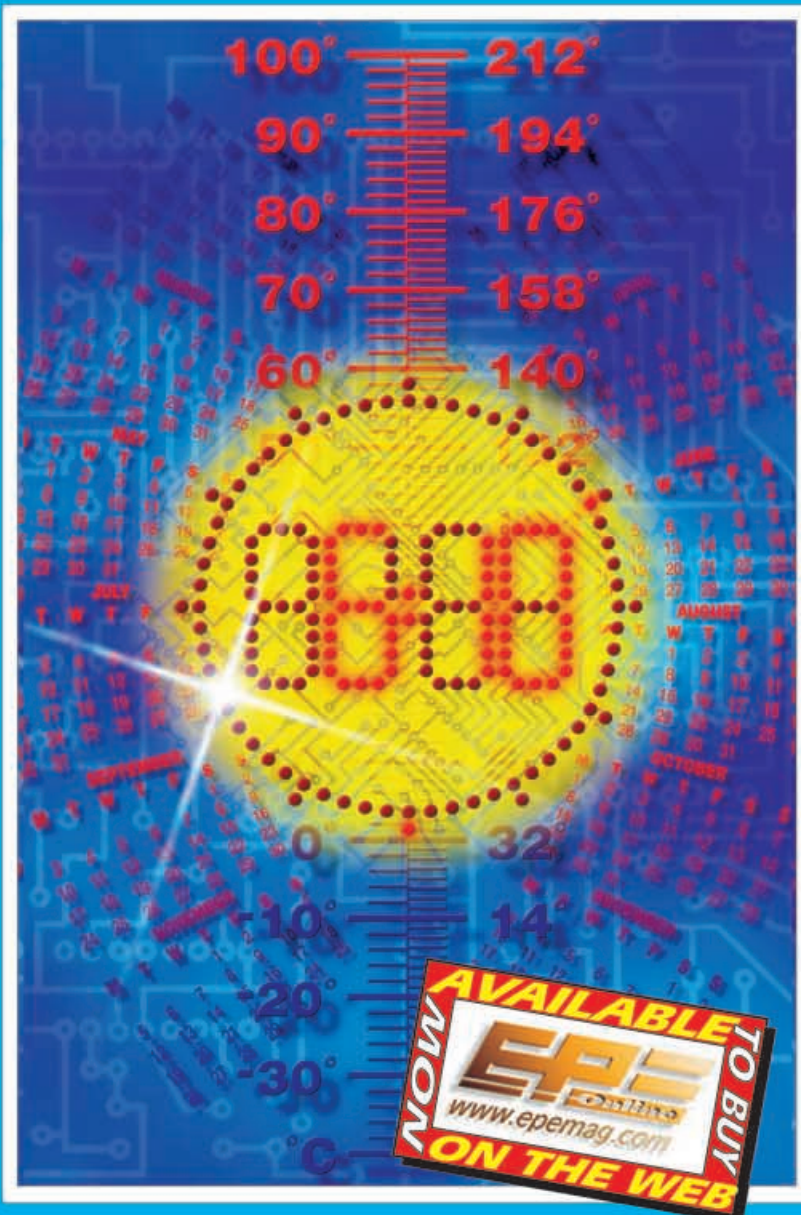
## FIDO Pedometer

■■■■■ New Series  
**RADIO CIRCUITS**  
Three circuits  
to build

■■■■■ PLUS  
**BACK TO BASICS 5**  
**THEREMIN • TWILIGHT SWITCH**



<http://www.epemag.wimborne.co.uk>

**Copyright © 2003, Wimborne Publishing Ltd**  
**(408 Wimborne Road East, Ferndown, Dorset, BH22 9ND, UK)**

**and TechBites Interactive Inc.,**  
**(PO Box 857, Madison, Alabama 35758, USA)**

**All rights reserved.**

## **WARNING!**

The materials and works contained within *EPE Online* — which are made available by Wimborne Publishing Ltd and Maxfield & Montrose Interactive Inc — are copyrighted. You are permitted to make a backup copy of the downloaded file and one (1) hard copy of such materials and works for your personal use. International copyright laws, however, prohibit any further copying or reproduction of such materials and works, or any republication of any kind.

Maxfield & Montrose Interactive Inc and Wimborne Publishing Ltd have used their best efforts in preparing these materials and works. However, Maxfield & Montrose Interactive Inc and Wimborne Publishing Ltd make no warranties of any kind, expressed or implied, with regard to the documentation or data contained herein, and specifically disclaim, without limitation, any implied warranties of merchantability and fitness for a particular purpose.

Because of possible variances in the quality and condition of materials and workmanship used by readers, *EPE Online*, its publishers and agents disclaim any responsibility for the safe and proper functioning of reader-constructed projects based on or from information published in these materials and works. In no event shall Maxfield & Montrose Interactive Inc or Wimborne Publishing Ltd be responsible or liable for any loss of profit or any other commercial damages, including but not limited to special, incidental, consequential, or any other damages in connection with or arising out of furnishing, performance, or use of these materials and works.






Colour CCTV camera, 8mm lens, 12V d.c. 200mA 562x628 Resolution 380 lines Automatic aperture lens Mirror function PAL Back Light Compensation MLR, 100x40x40mm. Ref EE2 £69



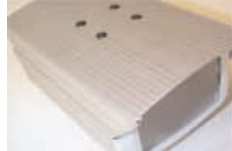Built-in Audio .15lux CCD camera 12V d.c. 200mA 480 lines s/n ratio >48db 1v P-P output 110x60x50mm. Ref EE1 £99



Metal CCTV camera housings for internal or external use. Made from aluminium and plastic they are suitable for mounting body cameras in. Available in two sizes 1 - 100x10x170mm and 2 - 100x70x280mm. Ref EE6 £22 EE7 £26 multi-position brackets. Ref EE8 £8



Excellent quality multi-purpose TV/TFT screen, works as just a LCD colour monitor with any of our CCTV cameras or as a conventional TV. Ideal for use in boats and caravans 49.7MHz-91.75MHz VHF channels 1-5, 168.25MHz-222.75MHz VHF channels 6-12, 471.25MHz-869.75MHz, Cable channels 112.325MHz-166.75MHz Z1-Z7, Cable channels 224.25MHz-446.75MHz Z8-Z35 5" colour screen. Audio output. 150mW. Connections, external aerial, earphone jack, audio/video input, 12V d.c. or mains, Accessories supplied Power supply, Remote control, Cigar lead power supply, Headphone Stand/bracket. 5" model £139 Ref EE9, 6" model £149. Ref EE10



Fully cased IR light source suitable for CCTV applications. The unit measures 10x10x150mm, is mains operated and contains 54 infra-red LEDs. Designed to mount on a standard CCTV camera bracket. The unit also contains a daylight sensor that will only activate the infra red lamp when the light level drops below a preset level. The infrared lamp is suitable for indoor or exterior use, typical useage would be to provide additional IR illumination for CCTV cameras. £49. Ref EE11



This device is mains operated and designed to be used with a standard CCTV camera causing it to scan. The black clips can be moved to adjust the span angle, the motor reversing when it detects a clip. With the clips removed the scanner will rotate constantly at approx 2.3rpm. 75x75x80mm £23. Ref EE12



Colour CCTV Camera measures 60x45mm and has a built in light level detector and 12 IR LEDs. 2 lux 12 IR LEDs 12V d.c. Bracket Easy connect leads £69. Ref EE15



A high quality external colour CCTV camera with built in Infra-red LEDs measuring 60x60x60mm Easy connect leads colour Waterproof PAL 1/4" CCD 542x588 pixels 420 lines .05 lux 3.6mm F2.78 deg lens 12V d.c. 400mA Built in light level sensor. £99. Ref EE13



A small compact colour CCTV camera measuring just 35x28x30mm (camera body) Camera is supplied complete with mounting bracket, built in IR, microphone and easy connect leads. Built in audio Built in IR LEDs Colour 380 line resolution PAL 0.2 us +18db sensitivity. Effective pixels 628x582 Power source 6-12V d.c. Power consumption 200mW £36. Ref EE16



Complete wireless CCTV system with video. Kit comprises pinhole colour camera with simple battery connection and a receiver with video output. 380 lines colour 2.4GHz 3 lux 6-12V d.c. manual tuning Available in two versions, pinhole and standard. £79 (pinhole) Ref EE17, £79 (standard). Ref EE18



Small transmitter designed to transmit audio and video signals on 2.4GHz. Unit measures 45x35x10mm. Ideal for assembly into covert CCTV systems Easy connect leads Audio and video input 12V d.c. Complete with aerial Selectable channel switch £30. Ref EE19



2.4GHz wireless receiver Fully cased audio and video 2.4GHz wireless receiver 190x140x30mm, metal case, 4 channel, 12V d.c. Adjustable time delay, 4s, 8s, 12s, 16s. £45. Ref EE20



Colour pinhole CCTV camera module with audio Compact colour pinhole camera measuring just 20x20x20mm, built-in audio and easy connect leads PAL CMOS sensor 6-9V d.c. Effective Pixels 628x582 Illumination 2 lux Definition >240 Signal/noise ratio >40db Power consumption 200mW £35. Ref £35



Self-cocking pistol plcr002 crossbow with metal body. Self-cocking for precise string alignment Aluminium alloy construction High tec fibre glass limbs Automatic safety catch Supplied with three bolts Track style for greater accuracy. Adjustable rearsight 50lb drawweight 150ft sec velocity Break action 17" string 30m range £21.65 Ref PLCR002 **INFRA-RED FILM** 6" square piece of flexible infra-red film that will only allow IR light through. Perfect for converting ordinary torches, lights, headlights etc to infra-red output only using standard light bulbs Easily cut to shape. 6" square £15. Ref IRRF2 or a 12" sq for £29 IRRF2A **NEW 12" 12" SQUARE SOLAR PANEL** Kevlar backed, 3watt output. Copper strips for easy solder connections £14.99. Ref 15P42 **PACK OF 4 JUST £39.95. Ref 15P42SP**



Dummy CCTV cameras These motorised cameras will work either on 2 AA batteries or with a standard DC adapter (not supplied) They have a built in movement detector that will activate the camera if movement is detected causing the camera to 'pan' Good deterrent. Camera measures 20cm high, supplied with rawl plugs and fixing screws. Camera also has a flashing red LED built in. £9.95. Ref CAMERAB

**BULL GROUP LTD**  
UNIT D, HENFIELD BUSINESS PARK,  
HENFIELD, SUSSEX BN5 9SL  
**TERMS: CASH, PO OR CHEQUE WITH ORDER PLUS £5.50 P&P (UK) PLUS VAT.**  
**24 HOUR SERVICE £7.50 (UK) PLUS VAT.**  
**OVERSEAS ORDERS AT COST PLUS £3.50**  
**(ACCESS/VISA/SWITCH ACCEPTED)**  
**'phone: 01273 491490 Fax 491813**  
**Sales@bullnet.co.uk**

## POWERSAFE DEEP CYCLE BATTERIES



**6V 100AH NOW ONLY £19 EACH**



**12V 51AH NOW ONLY £29.95 EACH**



We also have some used 2.3AH 12V (same as above) these are tested and in good condition and available at an extremely good price for bulk buyers, box of 30 just £49.99. Ref SLB23C



Aiptek Pocket DV Up to 2000 still pics before requiring download!! The all new Pocket DV, it's amazing... such advanced technology, such a tiny size - you will be the envy of your friends!! This camera will take up to 3.5 minutes of Video and Audio, up to 2000 digital still pictures or 30 minutes of voice recording!! Then just connect it to your PC via the USB cable (Supplied) and after transferring the data you can start all over again!! £69. Ref POCKETDV



The smallest PMR446 radios currently available (54x87x37mm). These tiny handheld PMR radios not only look great, but they are user friendly & packed with features including VOX, Scan & Dual Watch. Priced at £59.99 PER PAIR they are excellent value for money. Our new favourite PMR radios! Standby: - 35 hours Includes: - 2 x Radios, 2 x Belt Clips & 2 x Carry Strap £59.95 Ref ALAN1 Or supplied with 2 sets of rechargeable batteries and two mains chargers £84.99. Ref Alan2



Beltronics BEL550 Euroradarand GATSO detector Claimed Detection Range: GATSO up 400m. Radar & Laser guns up to 3 miles. Detects GATSO speed cameras at least 200 metres away, plenty of time to adjust your speed £319. Ref BEL550



Fully Portable - Use anywhere Six automatic programmer for full body pain relief, shoulder pain, back/neck pain, aching joints, rheumatic pain, sports injuries **EFFECTIVE DRUG FREE PAIN RELIEF TENS** (Transcutaneous Electrical Nerve Stimulation) units are widely used in hospitals, clinics throughout the United Kingdom for effective drug free pain relief. This compact unit is now approved for home use. TENS works by stimulating nerves close to the skin releasing endorphins (natures anesthetics) and helping to block the pain signals sent to the brain. Relief can begin within minutes, and a 30 minute treatment can give up to 12 hours relief or more. The TENS mini Microprocessors offer six types of automatic programme for shoulder pain, back/neck pain, aching joints, Rheumatic pain, migraines headaches, sports injuries, period pain. In fact all over body treatment. Will not interfere with existing medication. Not suitable for anyone with a heart pacemaker. Batteries supplied. £19.95 Ref TEN327 Spare pack of electrodes £5.99. Ref TEN327X

**SHOP ONLINE**  
**AT**  
**WWW.BULLNET.CO.UK**

ISSN 0262 3617

PROJECTS ... THEORY ... NEWS ...  
COMMENTS ... POPULAR FEATURES ...

VOL. 32. No. 6 JUNE 2003





Cover illustration by jgr22

# EVERYDAY PRACTICAL ELECTRONICS

INCORPORATING ELECTRONICS TODAY INTERNATIONAL

[www.epemag.wimborne.co.uk](http://www.epemag.wimborne.co.uk)

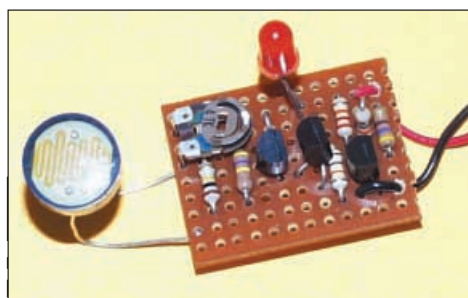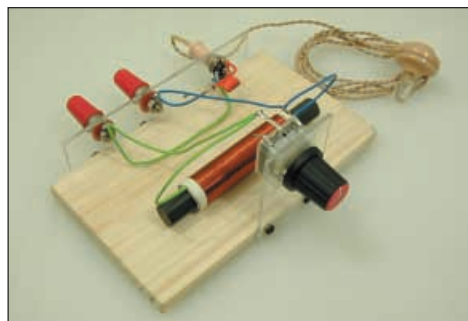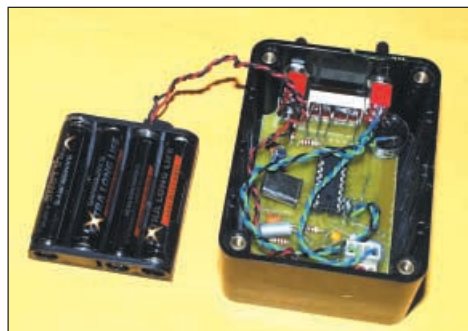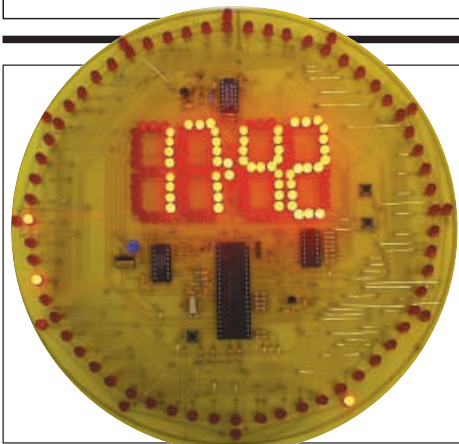EPE Online: [www.epemag.com](http://www.epemag.com)



## Projects and Circuits

- FIDO PEDOMETER** by Mike Boyden 388  
Keeping track of how far you've walked!
- PRACTICAL RADIO CIRCUITS – Part 1. Introduction,** 398  
**Simple Receivers and Headphone Amp** by Raymond Haigh  
Dispelling the mysteries of radio. A new series featuring a variety of practical circuits for the set builder and experimenter
- BACK TO BASICS – Part 5. Mini Theremin; Twilight Switch** 410  
by Bart Trepak. Concluding our illustration of how transistors can create useful designs
- INGENUITY UNLIMITED** 423  
Car Alarm Battery Saver
- PICRONOS L.E.D. WALL CLOCK** by John Becker 424  
Ancient and modern techniques display timely brilliance on a grand scale!

## Series and Features

- TECHNO TALK** by Andy Emmerson 395  
Powerline comms – boon or bogey?
- CIRCUIT SURGERY** by Alan Winstanley and Ian Bell 406  
More about reading circuit diagrams
- NEW TECHNOLOGY UPDATE** by Ian Poole 414  
Adding silicon to Li-Ion battery electrodes improves charge level performance
- INTERFACE** by Robert Penfold 418  
MSCOMM voltage levels, and batch counting
- NET WORK – THE INTERNET PAGE** surfed by Alan Winstanley 433  
Crediting PayPal

## Regulars and Services

- EDITORIAL** 387
- SHOPTALK** with David Barrington 392  
The *essential* guide to component buying for *EPE* projects
- PLEASE TAKE NOTE** PIC Toolkit TK3 V1.42 introduced 392
- NEWS** – Barry Fox highlights technology's leading edge 396  
Plus everyday news from the world of electronics
- BACK ISSUES** Did you miss these? Many now on CD-ROM! 415
- CD-ROMS FOR ELECTRONICS** 420  
A wide range of CD-ROMs for hobbyists, students and engineers
- READOUT** John Becker addresses general points arising 431
- PRINTED CIRCUIT BOARD AND SOFTWARE SERVICE** 434  
PCBs for *EPE* projects. Plus *EPE* project software
- DIRECT BOOK SERVICE** 436  
A wide range of technical books available by mail order, plus more CD-ROMs
- ADVERTISERS INDEX** 440

### FREE SUPPLEMENT

- EPE PIC TUTORIAL V2 – Part 3** between pages 408 and 409  
Concluding the enhanced revision of our highly acclaimed series of 1998, plus a brief look at some advanced concepts and two other PIC families

© Wimborne Publishing Ltd 2003. Copyright in all drawings, photographs and articles published in EVERYDAY PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our July 2003 issue will be published on Thursday, 12 June 2003. See page 379 for details

Readers Services • Editorial and Advertisement Departments 387

# NEXT MONTH

## EPE MINI METAL DETECTOR

Beat frequency oscillator (b.f.o.) metal detectors were very popular in the '60s and '70s, soon after the advent of the first commercial transistors. Some models sold thousands of times over. But these quickly went out of fashion as superior induction balance (i.b.) and pulse induction (p.i.) designs appeared on the market. However, b.f.o. metal detectors still have significant advantages in the areas of cost and ease of construction, and may be better suited to certain applications, such as pipe-finding or probing. Also, they are particularly well suited to miniaturisation. It is this last feature, especially, which is exploited in this design – a miniature b.f.o. metal detector which may be worn on the wrist – and, for good measure, a pinpointer, which is used to pinpoint items found with a larger detector.

While the performance of the EPE Mini is nothing to write home about, it is sufficiently sensitive to be of genuine use. It will easily detect an old Victorian penny at 55mm, and a tiny 15mm diameter coin at 35mm. It will discriminate between ferrous and non-ferrous metals (e.g. iron and copper), thus giving a good indication as to whether a “noble” metal has been found, or just a rusty piece of iron.

The EPE Mini has many potential uses. It may be used for detecting treasure (we hope!) during idle moments in the school grounds or on the beach. It may be used as a pipe-finder or cable locator. It may also be optimised to detect very small items, such as small nails and screws in furniture.

Besides this, the EPE Mini may well be the first metal detector to be worn on the wrist. Despite its diminutive size it is easy to build, with just eight standard size components mounted on its miniature printed circuit board.



## PRACTICAL RADIO CIRCUITS

Part 2 of our new radio circuits series looks at regeneration or “Q” multiplication. A simple “Q” multiplier project is described which can be added to the MK484 TRF Receiver featured in Part 1 to improve its performance. This is followed by a design for a classic two transistor medium wave reflex receiver together with full constructional details.

In order to provide these projects with loudspeaker output an easy-to-build speaker amplifier is also fully described, this circuit uses just five components, including the speaker, to give up to 1W r.m.s. output. Plus three more practical circuits.

## LOW RANGE OHMMETER ADAPTOR MK2

Taking measurements of low resistance components and printed circuit board tracks below 10Ω is a common requirement in electronics. However, most multimeters are not able to measure low resistances accurately as their resolution is inadequate.

This article presents an adaptor that can be connected to most multimeters to enable low resistance readings to be taken. The operation of the adaptor is based on the circuit published in EPE September 1995, but provides improved temperature stability.

The exact accuracy of the design (i.e. lower limit) depends simply on the quality of the meter used with the adaptor. A normal digital meter should be able to register values down to about 0.01Ω.

# NO ONE DOES IT BETTER



**DON'T MISS AN  
ISSUE – PLACE YOUR  
ORDER NOW!**

**Demand is bound to be high**

**JULY 2003 ISSUE ON SALE THURSDAY, JUNE 12**



# QUASAR ELECTRONICS LIMITED

PO Box 6935, BISHOPS STORTFORD, Herts. CM23 4WP

TEL: 0871 717 7168 FAX: 0871 277 2728

ADD £2.00 P&P to all orders (or 1st Class Recorded £4, Next day (Insured £250) £7, Europe £500, Rest of World £100). We accept all major credit cards. Make cheques/POs payable to Quasar Electronics. Prices include 17.5% VAT. MAIL ORDER ONLY  
FREE CATALOGUE with order or send 2 x 1st class stamps (refundable) for details of over 150 kits & publications.



## PROJECT KITS

Our electronic kits are supplied complete with all components, high quality PCBs (NOT cheap Tripad strip board!) and detailed assembly/operating instructions

- **2 x 25W CAR BOOSTER AMPLIFIER** Connects to output of an existing car stereo cassette player, CD player or radio. Heatsinks provided. PCB 76x75mm. **1046KT £24.95**
- **3-CHANNEL WIRELESS LIGHT MODULATOR** No electrical connection with amplifier. Light modulation achieved via a sensitive electret microphone. Separate sensitivity control per channel. Power handling 400W/channel. PCB 54x112mm. Mains powered. Box provided. **6014KT £24.95**
- **12 RUNNING LIGHT EFFECT** Exciting 12 LED light effect ideal for parties, discos, shop-windows & eye-catching signs. PCB design allows replacement of LEDs with 220V bulbs by inserting 3 TRIACs. Adjustable rotation speed & direction. PCB 54x112mm. **1026KT £15.95; BOX (for mains operation) 2026BX £5.00**
- **DISCO STROBE LIGHT** Probably the most exciting of all light effects. Very bright strobe tube. Adjustable strobe frequency: 1-60Hz. Mains powered. PCB: 60x68mm. Box provided. **6037KT £28.95**
- **ANIMAL SOUNDS** Cat, dog, chicken & cow. Ideal for kids farmyard toys & schools. **SG10M £5.95**
- **3 1/2 DIGIT LED PANEL METER** Use for basic voltage/current displays or customise to measure temperature, light, weight, movement, sound levels, etc. with appropriate sensors (not supplied). Various input circuit designs provided. **3067KT £13.95**
- **IR REMOTE TOGGLE SWITCH** Use any TV/VCR remote control unit to switch onboard 12V/1A relay on/off. **3058KT £10.95**
- **SPEED CONTROLLER** for any common DC motor up to 100W/5A. Pulse width modulation gives maximum torque at all speeds. 5-15VDC. Box provided. **3067KT £12.95**
- **3 x 8 CHANNEL IR RELAY BOARD** Control eight 12V/1A relays by Infra Red (IR) remote control over a 20m range in sunlight. 6 relays turn on only, the other 2 toggle on/off. 3 operation ranges determined by jumpers. Transmitter cable & all components provided. Receiver PCB 76x89mm. **3072KT £52.95**

## PRODUCT FEATURE

### COMPUTER TEMPERATURE DATA LOGGER

PC serial port controlled 4-channel temperature meter (either deg C or F). Requires no external power. Allows continuous temperature data logging of up to four temperature sensors located 200m+ from motherboard/PC. Ideal use for old 386/486 computers. Users can tailor input data streams to suit their purpose (dump it to a spreadsheet or write your own BASIC programs using the INPUT command to grab the readings). PCB just 38mm x 38mm. Sensors connect via four 3-pin headers. 4 header cables supplied but only one DS18S20 sensor.  
Kit software available free from our website.  
**ORDERING:** 3145KT £23.95 (kit form); AS3145 £29.95 (assembled); Additional DS18S20 sensors £4.95 each



- **SOUND EFFECTS GENERATOR** Easy to build. Create an almost infinite variety of interesting/unusual sound effects from birds chirping to sirens. 9VDC. PCB 54x85mm. **1045KT £8.95**
- **ROBOT VOICE EFFECT** Make your voice sound similar to a robot or Darlek. Great fun for discos, school plays, theatre productions, radio stations & playing jokes on your friends when answering the phone! PCB 42x71mm. **1131KT £8.95**
- **AUDIO TO LIGHT MODULATOR** Controls intensity of one or more lights in response to an audio input. Sale, modern opto-coupler design. Mains voltage experience required. **3012KT £8.95**
- **MUSIC BOX** Activated by light. Plays 8 Christmas songs and 5 other tunes. **3104KT £7.95**
- **20 SECOND VOICE RECORDER** Uses non-volatile memory - no battery backup needed. Record/replay messages over & over. Playback as required to great customers etc. Volume control & built-in mic. 6VDC. PCB 50x73mm. **3131KT £12.95**
- **TRAIN SOUNDS** 4 selectable sounds: whistle blowing, level crossing bell, 'clackety-clack' & 4 in sequence. **SG01M £6.95**
- **PC CONTROLLED RELAY BOARD** Convert any 286 upward PC into a dedicated automatic controller to independently turn on/off up to eight lights, motors & other devices around the home, office, laboratory or factory. Each relay output is capable of switching 250VAC/4A. A suite of DOS and Windows control programs are provided together with all components (except box and PC cable). 12VDC. PCB 70x200mm. **3074KT £31.95**
- **2 CHANNEL UHF RELAY SWITCH** Contains the same transmitter/receiver pair as 30A15 below plus the components and PCB to control two 240VAC/10A relays (also supplied). Ultra bright LEDs used to indicate relay status. **3092KT £27.95**
- **TRANSMITTER RECEIVER PAIR** 2-button keyboard style 300-375MHz Tx with 30m range. Receiver encoder module with matched decoder IC. Components must be built into a circuit like kit 3082 above. **30A15 £14.95**
- **PIC 16C71 FOUR SERVO MOTOR DRIVER** Simultaneously control up to 4 servo motors. Software & all components (except servo/control pots) supplied. 5VDC. PCB 50x70mm. **3102KT £15.95**
- **UNIPOLAR STEPPER MOTOR DRIVER** for any 5/6/8 lead motor. Fast/slow & single step rates. Direction control & on/off switch. Wave, 2-phase & half-wave step modes. 4 LED indicators. PCB 50x65mm. **3109KT £14.95**
- **PC CONTROLLED STEPPER MOTOR DRIVER** Control two unipolar stepper motors (3A max. each) via PC printer port. Wave, 2-phase & half-wave step modes. Software accepts 4 digital inputs from external switches & will single step motors. PCB fits in D-shell case provided. **3113KT £17.95**
- **12-BIT PC DATA ACQUISITION/CONTROL UNIT** Similar to kit 3093 above but uses a 12 bit Analogue-to-Digital Converter (ADC) with internal analogue multiplexer. Reads 8 single ended channels or 4 differential inputs or a mixture of both. Analogue inputs read 0-4V. Four TTL/CMOS compatible digital input/outputs. ADC conversion time <10µs. Software (C, QB & Win), extended D shell case & all components (except sensors & cable) provided. **3118KT £52.95**



### THE EXPERTS IN RARE & UNUSUAL INFORMATION!

Full details of all X-FACTOR PUBLICATIONS can be found in our catalogue. N.B. Minimum order charge for reports and plans is £5.00 PLUS normal P&P.

- **SUPER-EAR LISTENING DEVICE** Complete plans to build your own parabolic dish microphone. Listen to distant voices and sounds through open windows and even walls! Made from readily available parts. **R002 £3.50**
- **LOCKS** - How they work and how to pick them. This fact filled report will teach you more about locks and the art of lock picking than many books we have seen at 4 times the price. Packed with information and illustrations. **R008 £3.50**
- **RADIO & TV JOKER PLANS** We show you how to build three different circuits for disrupting TV picture and sound plus FM radio! May upset your neighbours & the authorities!! DISCRETION REQUIRED. **R017 £3.50**
- **INFINITY TRANSMITTER PLANS** Complete plans for building the famous Infinity Transmitter. Once installed on the target phone, device acts like a room bug. Just call the target phone & activate the unit to hear all room sounds. Great for home-office security! **R019 £3.50**
- **THE ETHER BOX CALL INTERCEPTOR PLANS** Grabs telephone calls out of thin air! No need to wire-in a phone bug. Simply place this device near the phone lines to hear the conversations taking place. **R025 £3.00**
- **CASH CREATOR BUSINESS REPORTS** Need ideas for making some cash? Well this could be just what you need! You get 40 reports (approx. 800 pages) on floppy disk that give you information on setting up different businesses. You also get valuable reproduction and duplication rights so that you can sell the manuals as you like. **R030 £7.50**

## SURVEILLANCE

High performance surveillance bugs. Room transmitters supplied with sensitive electret microphone & battery holder/cell. All transmitters can be received on an ordinary VHF/FM radio between 88-108MHz. Available in Kit Form (KT) or Assembled & Tested (AS).

### ROOM SURVEILLANCE

● **MTX - MINIATURE 3V TRANSMITTER** Easy to build & guaranteed to transmit 300m+ @ 3V. Long battery life. 3-5V operation. Only 45x18mm. **B 3007KT £5.95 AS3007 £11.95**

● **MTX - MINIATURE 9V TRANSMITTER** Our best selling bug. Super sensitive, high power - 500m range @ 9V (over 1km with 18V supply and better aerial). 45x19mm. **3018KT £7.95 AS3018 £12.95**

● **HPTX - HIGH POWER TRANSMITTER** High performance, 2 stage, transmitter gives greater stability & higher quality reception. 1000m range 6-12V DC operation. Size 70x15mm. **3032KT £9.95 AS3032 £18.95**

● **MMTX - MICRO-MINIATURE 9V TRANSMITTER** The ultimate bug for its size, performance and price. Just 15x25mm. 500m range @ 9V. Good stability. 6-18V operation. **3051KT £8.95 AS3051 £14.95**

● **VTX - VOICE ACTIVATED TRANSMITTER** Operates only when sounds detected. Low standby current. Variable trigger sensitivity. 500m range. Peaking circuit supplied for maximum RF output. On/off switch. 6V operation. Only 63x38mm. **3028KT £12.95 AS3028 £24.95**

● **HARDWIRED BUGTWO STATION INTERCOM** Each station has its own amplifier, speaker and mic. Can be set up as either a hard-wired bug or two-station intercom. 10m x 2-core cable supplied. 9V operation. **3021KT £15.95 (kit form only)**

● **TRVS - TAPE RECORDER VOX SWITCH** Used to automatically operate a tape recorder (not supplied) via its REMOTE socket when sounds are detected. All conversations recorded. Adjustable sensitivity & turn-off delay. 115x19mm. **3013KT £9.95 AS3013 £21.95**

### TELEPHONE SURVEILLANCE

● **MTTX - MINIATURE TELEPHONE TRANSMITTER** Attaches anywhere to phone line. Transmits only when phone is used! Tune-in your radio and hear both parties. 300m range. Uses line as aerial & power source. 20x45mm. **3016KT £8.95 AS3016 £14.95**

● **TRI - TELEPHONE RECORDING INTERFACE** Automatically records all conversations. Connects between phone line & tape recorder (not supplied). Operates recorders with 1.5-12V battery systems. Powered from line. 50x33mm. **3033KT £9.95 AS3033 £18.95**

● **TPA - TELEPHONE PICK-UP AMPLIFIER/WIRELESS PHONE BUG** Place pick-up coil on the phone line or near phone earpiece and hear both sides of the conversation. **3055KT £11.95 AS3055 £20.95**

### HIGH POWER TRANSMITTERS

● **1 WATT FM TRANSMITTER** Easy to construct. Delivers a crisp, clear signal. Two-stage circuit. Kit includes microphone and requires a simple open dipole aerial. 6-30VDC. PCB 42x45mm. **1009KT £12.95**

● **4 WATT FM TRANSMITTER** Comprises three RF stages and an audio preamplifier stage. Piezoelectric microphone supplied or you can use a separate preamplifier circuit. Antenna can be an open dipole or Ground Plane. Ideal project for those who wish to get started in the fascinating world of FM broadcasting and want a good basic circuit to experiment with. 12-18VDC. PCB 44x146mm. **1028KT £22.95 AS1028 £34.95**

● **15 WATT FM TRANSMITTER (PRE-ASSEMBLED & TESTED)** Four transistor based stages with Philips BL785 in final stage. 15 Watts RF power on the air. 88-108MHz. Accepts open circuit, Ground Plane, 5/8, J, or YAGI antennas. 12-18VDC. PCB 70x220mm. SWS meter needed for alignment. **1021KT £99.95**

● **SIMILAR TO ABOVE BUT 25W Output. 1031KT £109.95**

700W power. PCB: 48mm x 65mm. Box provided. **6074KT £17.95**

● **3 INPUT MONO MIXER** Independent level control for each input and separate bass/treble controls. Input sensitivity: 240mV. 18V DC. PCB: 60mm x 185mm. **1052KT £16.95**

● **NEGATIVE/POSITIVE ION GENERATOR** Standard Cockcroft-Walton multiplier circuit. Mains voltage experience required. **3057KT £10.95**

● **LED DICE** Classic intro to electronics & circuit analysis. 7 LED's simulate dice roll, slow down & land on a number at random. 555 IC circuit. **3003KT £9.95**

● **STAIRWAY TO HEAVEN** Tests hand-eye co-ordination. Press switch when green segment of LED lights to climb the stairway - miss & start again! Good intro to several basic circuits. **3005KT £9.95**

● **ROULETTE LED** Ball spins round the wheel, slows down & drops into a slot. 10 LED's. Good intro to CMOS decade counters & Op-Amps. **3006KT £10.95**

● **12V XENON TUBE FLASHER TRANSFORMER** Steps up a 12V supply to flash a 25mm Xenon tube. Adjustable flash rate. **3163KT £13.95**

● **LED FLASHER** 1.5 ultra bright red LED's flash in 7 selectable patterns. **3037MKT £5.95**

● **LED FLASHER 2** Similar to above but flash in sequence or randomly. Ideal for model railways. **3052MKT £5.95**

● **INTRODUCTION TO PIC PROGRAMMING.** Learn programming from scratch. Programming hardware, a P16F84 chip and a two-part, practical, hands-on tutorial series are provided. **3081KT £21.95**

● **SERIAL PIC PROGRAMMER** for all 8/18/28/40 pin DIP serial programmed PICs. Shareware software supplied limited to programming 256 bytes (registration costs £14.95). **3096KT £10.95**

● **ATMEL 89C051 PROGRAMMER** Simple-to-use yet powerful programmer for the Atmel 89C051, 89C2051 & 89C4051 uC's. Programmer does NOT require special software other than a terminal emulator program (built into Windows). Can be used with ANY computer/operating system. **3121KT £24.95**

● **3V/1.5V TO 9V BATTERY CONVERTER** Replace expensive 9V batteries with economic 1.5V batteries. IC based circuit steps up 1 or 2 'AA' batteries to give 9V/18mA. **3035KT £5.95**

● **STABILISED POWER SUPPLY 3-30V/2.5A** Ideal for hobbyist & professional laboratory. Very reliable & versatile design at an extremely reasonable price. Short circuit protection. Variable DC voltages (3-30V). Rated output 2.5 Amps. Large heatsink supplied. You just supply a 24VAC/3A transformer. PCB 55x112mm. Mains operation. **1007KT £16.95**

● **STABILISED POWER SUPPLY 2-30V/5A** As kit 1007 above but rated at 5Amp. Requires a 24VAC/5A transformer. **1096KT £27.95**

● **MOTORBIKE ALARM** Uses a reliable vibration sensor (adjustable sensitivity) to detect movement of the bike to trigger the alarm & switch the output relay to which a siren, bikes horn, indicators or other warning device can be attached. Auto-reset. 6-12VDC. PCB 57x64mm. **1011KT £11.95 Box 2011BX £7.00**

● **CAR ALARM SYSTEM** Protect your car from theft. Features vibration sensor, courtesy/boot light voltage drop sensor and bonnet/boot earth switch sensors. Entry/exit delays, auto-reset and adjustable alarm duration. 6-12V DC. PCB: 47mm x 55mm. **1019KT £11.95 Box 2019BX £8.00**

● **PIEZO SCREAMER** 110dB of ear piercing noise. Fits in box with 2 x 35mm piezo elements built into their own resonant cavity. Use as an alarm siren or just for fun! 6-9VDC. **3015KT £10.95**

● **COMBINATION LOCK** Versatile electronic lock comprising main circuit & separate keypad for remote opening of lock. Relay supplied. **3029KT £10.95**

● **ULTRASONIC MOVEMENT DETECTOR** Crystal locked detector frequency for stability & reliability. PCB 75x40mm houses all components. 4-7m range. Adjustable sensitivity. Output will drive external relay/circuits. 9VDC. **3049KT £13.95**

● **PIR DETECTOR MODULE** 3-led assembled unit just 25x35mm as used in commercial burglar alarm systems. **3076KT £8.95**

● **INFRARED SECURITY BEAM** When the invisible IR beam is broken a relay is tripped that can be used to sound a bell or alarm. 25 metre range. Mains rated relays provided. 12VDC operation. **3130KT £12.95**

● **SQUARE WAVE OSCILLATOR** Generates square waves at 6 preset frequencies in factors of 10 from 1Hz-100KHz. Visual output indicator. 5-18VDC. Box provided. **3111KT £8.95**


● **PC DRIVEN POKER SCORE SAMPLER/DATA LOGGER** Analogue voltage sampler records voltages up to 2V or 20V over periods from milli-seconds to months. Can also be used as a simple digital scope to examine audio & other signals up to about 5KHz. Software & D-shell case provided. **3112KT £18.95**

● **20 MHz FUNCTION GENERATOR** Square, triangular and sine waveform up to 20MHz over 3 ranges using 'coarse' and 'fine' frequency adjustment controls. Adjustable output from 0-2V p-p. A TTL output is also provided for connection to a frequency meter. Uses MAX038 IC. Plastic case with printed front/rear panels & all components provided. 7-12VAC. **3101KT £69.95**

**BARGAIN BUY!!**

Great introduction to electronics. Ideal for the budding electronics expert! Build a radio, burglar alarm, water detector, Morse code practice circuit, simple computer circuits, and much more! NO soldering, tools or previous electronics knowledge required. Circuits can be built and unassembled repeatedly. Comprehensive 68-page manual with explanations, schematics and assembly diagrams. Suitable for age 10+. Excellent for schools. Requires 2 x AA batteries. Order Code EPL030 ONLY £14.95 (phone for bulk discounts). 130, 300 and 500-in-ONE also available.

## 30-in-ONE Electronic Projects Lab

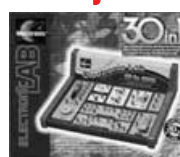

**WEB: <http://www.QuasarElectronics.com>  
email: [epesales@QuasarElectronics.com](mailto:epesales@QuasarElectronics.com)**

**Secure Online Ordering Facilities  
Full Kit Listing, Descriptions & Photos  
Kit Documentation & Software Downloads**


## Enhanced 'PICALL' ISP PIC Programmer

Kit will program virtually ALL 8 to 40 pin\* serial and parallel programmed PIC micro-controllers. Connects to PC parallel port. Supplied with fully functional pre-registered PICALL DOS and WINDOWS AVR software packages, all components and high quality DSPTH board. Also programs certain ATMEL AVR, SCENIX SX and EEPOM 24C devices. New devices can be added to the software as they are released. Blank chip auto detect feature for super-fast bulk programming. Hardware now supports ISP programming. \*A 40 pin wide ZIF socket is required to program 0-3in. devices (Order Code AZIF40 @ £15.00).



Order Ref	Description	inc. VAT ea
3144KT	Enhanced 'PICALL' ISP PIC Programmer	£59.95
AS3144	Assembled Enhanced 'PICALL' ISP PIC Programmer	£64.95
AS3144ZIF	Assembled Enhanced 'PICALL' ISP PIC Programmer c/w ZIF socket	£79.95

## ATMEL AVR Programmer

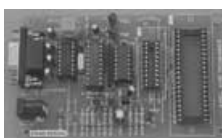


Powerful programmer for Atmel AT90Sxxxx (AVR) micro controller family. All fuse and lock bits are programmable. Connects to serial port. Can be used with ANY computer and operating system. Two LEDs to indicate programming status. Supports 20-pin DIP AT90S1200 & AT90S2313 and 40-pin DIP AT90S4414 & AT90S8515 devices. NO special software required – uses any terminal emulator program (built into Windows). The programmer is supported by BASCOM-AVR Basic Compiler software (see website for details).

Order Ref	Description	inc. VAT ea
3122KT	ATMEL AVR Programmer	£24.95
AS3122	Assembled 3122	£34.95

Atmel 89Cx051 and 89xxx programmers also available.
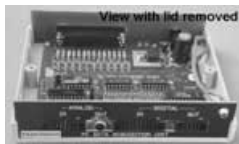
## PC Data Acquisition & Control Unit

With this kit you can use a PC parallel port as a real world interface. Unit can be connected to a mixture of analogue and digital inputs from pressure, temperature, movement, sound, light intensity, weight sensors, etc. (not supplied) to sensing switch and relay states. It can then process the input data and use the information to control up to 11 physical devices such as motors, sirens, other relays, servo motors & two-stepper motors.



### FEATURES:

- 8 Digital Outputs: Open collector, 500mA, 33V max.
  - 16 Digital Inputs: 20V max. Protection 1K in series, 5.1V Zener to ground.
  - 11 Analogue Inputs: 0-5V, 10 bit (5mV/step.)
  - 1 Analogue Output: 0-2.5V or 0-10V. 8 bit (20mV/step.)
- All components provided including a plastic case (140mm x 110mm x 35mm) with pre-punched and silk screened front/rear panels to give a professional and attractive finish (see photo) with screen printed front & rear panels supplied. Software utilities & programming examples supplied.

Order Ref	Description	inc. VAT ea
3093KT	PC Data Acquisition & Control Unit	£99.95
AS3093	Assembled 3093	£124.95

*See opposite page for ordering information on these kits*

## ABC Mini 'Hotchip' Board




Currently learning about microcontrollers? Need to do something more than flash a LED or sound a buzzer? The ABC Mini 'Hotchip' Board is based on Atmel's AVR 8535 RISC technology and will interest both the beginner and expert alike. Beginners will find that they can write and test a simple program, using the BASIC programming language, within an hour or two of connecting it up.

Experts will like the power and flexibility of the ATMEL microcontroller, as well as the ease with which the little Hot Chip board can be "designed-in" to a project. The ABC Mini Board 'Starter Pack' includes just about everything you need to get up and experimenting right away. On the hardware side, there's a pre-assembled micro controller PC board with both parallel and serial cables for connection to your PC. Windows software included on CD-ROM features an Assembler, BASIC compiler and in-system programmer. The pre-assembled boards only are also available separately.


Order Ref	Description	inc. VAT ea
ABCMINISP	ABC MINI Starter Pack	£64.95
ABCMINIB	ABC MINI Board Only	£39.95
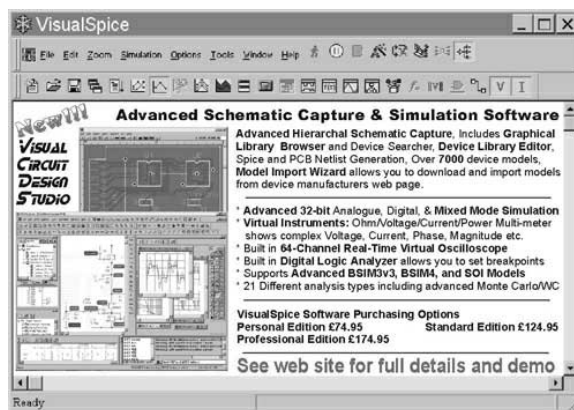
## Advanced 32-bit Schematic Capture and Simulation Visual Design Studio


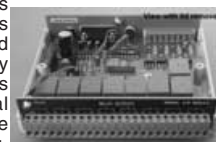
## Serial Port Isolated I/O Controller

Kit provides eight relay outputs capable of switching 4 amps at mains voltages and four optically isolated digital inputs. Can be used in a variety of control and sensing applications including load switching, external switch input sensing, contact closure and external voltage sensing. Programmed via a computer serial port, it is compatible with ANY computer & operating system. After programming, PC can be disconnected. Serial cable can be up to 35m long, allowing 'remote' control. User can easily write batch file programs to control the kit using simple text commands. NO special software required – uses any terminal emulator program (built into Windows). All components provided including a plastic case with pre-punched and silk screened front/rear panels to give a professional and attractive finish (see photo).



Order Ref	Description	inc. VAT
3108KT	Serial Port Isolated I/O Controller Kit	£54.95
AS3108	Assembled Serial Port Isolated I/O Controller	£64.95



# FREE Catalogue Available On Request



WCN Supplies • Dept EPE • The Old Grain Store • Rear Of 62 Rumbridge Street • Totton • Southampton • SO40 9DS  
Telephone or Fax On Southampton 023 8066 0700 • Email: [info@wcsupplies.fsnet.co.uk](mailto:info@wcsupplies.fsnet.co.uk)

**Telephone, Fax Or Email For Your Free Catalogue**

## SPECIAL OFFERS



**TEKTRONIX 2445A**  
4-ch 150MHz delay,  
cursors etc. Supplied  
with 2 Tektronix probes.  
ONLY **£425**

**TEKTRONIX 2232** Digital Storage Scope.  
Dual Trace, 100MHz, 100MS with probes ..... £525  
**CIRRUS CRL254** Sound Level Meter  
with Callibrator 80-120dB, LEO ..... £95  
**BECKMAN HD110** Handheld 3 1/2 digit DMM, 28  
ranges, with battery, leads and carrying case ..... £30  
**WAYNE KERR B424** Component Bridge ..... £50  
**RACAL 9300** True RMS Voltmeter, 5Hz-20MHz  
usable to 60MHz, 10V-316V ..... £50  
**RACAL 9300B**, as above ..... £75

**H.P. 3312A** Function Gen., 0-1Hz-13MHz,  
AM/FM Sweep/Tri/Gate/Burst etc. .... £300  
**FARNELL AMM255** Automatic Mo  
Meter, 1-5MHz-2GHz, unused ..... £300  
**FARNELL DSG1** Low Frequency Syn Sig. Gen.,  
0-001Hz-99-99kHz, low distortion, TTL  
Square/Pulse Outputs etc. .... £95  
**FLUKE 8060A** Handheld True RMS, DMM,  
4 1/2 digit ..... As new £150, used £95  
**H.P. 3310A** Function Gen., 0-005Hz-5MHz,  
Sine/Sq/Tri/Ramp/Pulse ..... £125  
**FARNELL LFM4** Sine/Sq Oscillator, 10Hz-1MHz,  
low distortion, TTL output, Amplitude Meter ..... £125  
**H.P. 545A** Logic Probe with 546A Logic  
Pulser and 547A Current Tracer ..... £90  
**FLUKE 77** Multimeter, 3 1/2-digit, handheld ..... £60  
**FLUKE 77 Series 11** ..... £70  
**HEME 1000** L.C.D. Clamp Meter, 00-1000A,  
in carrying case ..... £80

**BLACK STAR ORION PAL/TV** Colour Pattern  
Generator ..... from £75-£125  
**THURBY/THANDER TG210** Function Generator,  
0-002Hz-2MHz, TTL etc. .... £80-£95  
**THURBY/THANDER P.S.U. PL320QMD**, 0V-32V,  
0A-2A Twice (late colours) ..... £200

**Datron 1061A** ..... **£225**  
High Quality 6 1/2 digit Bench  
Multimeter  
True RMS/4 wire/Current Converter

**Racal Receiver RA1772** ..... **£250**  
50kHz-30MHz

## JUST IN

**H.P. 8460A** Signal Generator, AM/FM, 500kHz-512MHz ..... £250  
**KENWOOD CS4025** Oscilloscope, dual trace, 20MHz ..... £125  
**LEADER LBO523** Oscilloscope, dual trace, 35MHz ..... £140  
**GOULD OS300** Oscilloscope, dual trace, 20MHz ..... £95  
**NATIONAL PANASONIC VP7705A** Distortion Analyser ..... £125  
**KENWOOD VT176** Millivoltmeter 2-channel ..... £50  
**KENWOOD FL140** Wow & Flutter Meter ..... £50  
**KENWOOD FL180A** Wow & Flutter Meter ..... Used £75  
**BIRD 43** Watt Meter ..... £125  
**GOODWILL CVT427** Dual Ch AC Millivoltmeter, 10mV-300V in 12 ranges, Freq. 10Hz-1MHz ..... £75  
Elements for the above ..... £25

**MARCONI 893C** AF Power Meter, Sinad Measurement  
low distortion ..... Unused £100, Used £80  
**MARCONI 893B**, No Sinad ..... £30  
**MARCONI 2610** True RMS Voltmeter, Autorangeing,  
5Hz-25MHz ..... £195  
**GOULD J3B** Sine/Sq Osc., 10Hz-100kHz, low distortion ..... £75-£125  
**AVO 8 Mk. 6** in Every Ready case, with leads etc. .... £80  
Other AVOs from ..... £50  
**GOODWILL CVT427** Dual Ch AC Millivoltmeter, 10mV-300V in 12 ranges, Freq. 10Hz-1MHz ..... £100-£125  
**SOLARTRON 7150** DMM 6 1/2-digit Tru RMS-IEEE ..... £95-£150  
**SOLARTRON 7150 Plus** ..... £200

**HIGH QUALITY RACAL COUNTERS**  
**9904** Universal Timer Counter, 50MHz ..... £50  
**9916** Counter, 10Hz-520MHz ..... £75  
**9918** Counter, 10Hz-560MHz, 9-digit ..... £50  
**WAYNE KERR B424** Component Bridge ..... £125  
**RACAL/AIM 9343M** LCR Databridge, Digital Automeasurement of R, C, L, Q, D ..... £200  
**HUNTRON TRACKER** Model 1000 ..... £125  
**FLUKE 8050A** 4-5 Digit, 2A, True RMS ..... £75  
**FLUKE 8010A** 3-5 Digit, 10A ..... £50  
**FLUKE 8012A** 3-5 Digit, 2A ..... £40

**Portable Appliance Tester** ..... **£180**  
Megger Pat 2 ONLY

**H.P. 6012B** DC PSU 0-60V, 0-50A, 1000W ..... £1000  
**FARNELL AP6050** 1KV Autorangeing ..... £1000  
**FARNELL H60/50** 0-60V 0-50A ..... £750  
**FARNELL H60/25** 0-60V 0-25A ..... £400  
**Power Supply HPS3010**, 0-30V, 0-10A ..... £140  
**FARNELL** Dual PSU XA35-2T, 0-35V, 0-2A, Twice OMD L.C.D. Display ..... £180  
**FARNELL L30-2** 0-30V, 0-2A ..... £80  
**FARNELL L30-1** 0-30V, 0-1A ..... £60  
Many other Power Supplies available

**FARNELL DT12-14 OSCILLOSCOPE.**  
Dual trace, 12MHz TV, coupling, ONLY ..... **£75**

**FARNELL LF1 SINE/SQ OSCILLATOR.**  
ONLY ..... **£75**  
10Hz-1MHz.

## OSCILLOSCOPES

**TEKTRONIX TD530** dual trace, 200MHz, 1GS ..... Unused £1500  
**TEKTRONIX TD5320** dual trace, 100MHz, 50MS ..... £1200  
**TEKTRONIX TD510** dual trace, 50MHz, 200MS ..... £950  
**LECROY 9400A** dual trace, 175MHz, 5GS ..... £750  
**HITACHI VC523**, d/trace, 20MHz, 20MS, delay etc Unused £500  
**PHILIPS PM3092** 2+2-ch, 200MHz, delay etc, £800 as new £950  
**PHILIPS PM3092** 2+2-ch, 100MHz, delay etc, £700 as new £850  
**TEKTRONIX TAS465** dual trace, 100MHz, delay etc ..... £750  
**TEKTRONIX 2465B** 4-ch, 400MHz, delay cursors etc ..... £1500  
**TEKTRONIX 2465** 4-ch, 300MHz, delay cursors etc ..... £900  
**TEKTRONIX 468** Dig. Storage, dual trace, 100MHz, delay ..... £450  
**TEKTRONIX 466** Analogue Storage, dual trace, 100MHz ..... £250  
**TEKTRONIX 485** dual trace, 350MHz, delay sweep ..... £350  
**TEKTRONIX 475** dual trace, 200MHz, delay sweep ..... £350  
**TEKTRONIX 465B** dual trace, 100MHz, delay sweep ..... £325  
**TEKTRONIX 2215** dual trace, 60MHz, delay sweep ..... £250  
**PHILIPS PM3065** 2+1-ch, 100MHz, dual TB/delay autose ..... £375  
**PHILIPS PM3055** 2+1-ch, 60MHz, dual TB/delay autose ..... £275  
**PHILIPS PM3217** dual trace, 50MHz delay ..... £200-£250  
**GOULD OS1100** dual trace, 30MHz delay ..... £125  
**HAMEG HM303** dual trace, 35MHz component tester as new ..... £240  
**HAMEG HM303** dual trace, 30MHz component tester ..... £200  
Many other Oscilloscopes available

**MARCONI 2022E** Synth AM/FM Sig Gen 10kHz-1.01GHz L.C.D. display etc ..... £525-£750  
**H.P. 8657A** Synth sig gen, 100kHz-1040MHz ..... £2000  
**H.P. 8656B** Synth sig gen, 100kHz-990MHz ..... £1350  
**H.P. 8656A** Synth sig gen, 100kHz-990MHz ..... £995  
**R&S APN62** Synth, 1Hz-260kHz sig. gen., balanced/unbalanced output, L.C.D. display ..... £425  
**PHILIPS PM5328** sig gen, 100kHz-180MHz with 200kHz, freq. counter, IEEE ..... £550  
**RACAL 9081** Synth AM/FM sig gen, 5MHz-520MHz ..... £250  
**H.P. 3325A** Synth function gen, 21MHz ..... £600  
**MARCONI 6500** Amplitude Analyser ..... £1500  
**H.P. 4192A** Impedance Analyser ..... £5000  
**H.P. 8754A** LCR Meter, 10kHz-10MHz ..... £2750  
**H.P. 8903A** Distortion Analyser ..... £1000  
**WAYNE KERR 3245** Inductance Analyser ..... £2000  
**H.P. 8112A** Pulse Generator, 50MHz ..... £1250  
**MARCONI 2440** Frequency Counter, 20GHz ..... £1000  
**H.P. 3505B** Frequency Counter, 20GHz ..... £2000  
**H.P. 5424A** 10Hz-18GHz Frequency Counter ..... £800  
**H.P. 1650B** Logic Analyser, 80-channel ..... £1000  
**MARCONI 2035** Mod Meter, 500kHz-2GHz ..... £750

**H.P. 6063B** DC Electronic Load, 3-240V/0-10A, 250W ..... POA  
**H.P. 66312A** PSU, 0-20V/0-2A ..... £400  
**H.P. 66311B** PSU, 0-15V/0-3A ..... £400  
**H.P. 66309D** PSU Dual, 0-15, 0-3A/0-12, 0-1-5A ..... £750  
**H.P. 6632B** PSU, 0-20V/0-5A ..... £500  
**H.P. 6623A** PSU, triple output ranging from 0-7V 0-5A to 0-20V 0-4A ..... £850  
**H.P./AGILENT 34401A** DMM 6 1/2 digit ..... £400/£450  
**H.P. 3478A** DMM 5 1/2 digit ..... £275  
**FLUKE 45** DMM dual display ..... £400  
**KEITHLEY 2010** DMM 7 1/2 digit ..... £950  
**KEITHLEY 617** Programmable Electrometer ..... £1250  
**H.P. 6338B** Millivoltmeter ..... £1500  
**RACAL** Counter type 1999 2GHz ..... £500  
**H.P. Counter type 53131A** 3GHz ..... £850  
**H.P./AGILENT 33120A** Func. Gen/ARB, 100kHz-15MHz ..... £900/£1000  
**SONY/TEKTRONIX AFG320** Arbitrary Func. Gen ..... £1250  
**H.P. 8804A** Syn. Function Gen, DC-600kHz ..... £1000/£1250  
**BLACK STAR JUPITOR 2010** Func. Gen, 0-2Hz-2MHz with frequency counter ..... £140  
**H.P. 8116A** Pulse Generator, 1mH-50MHz ..... £1950  
**H.P. 8657B** Syn Sig. Gen, 0-1-2080MHz ..... £2500  
**CO-AXIAL SWITCH**, 1-5GHz ..... £140  
**IEEE CABLES** ..... £10

## SPECTRUM ANALYSERS

**H.P. 8561B** 50Hz-6.5GHz ..... £5000  
**H.P. 8560A** 50Hz-2.9GHz synthesised ..... £5000  
**H.P. 8594E** 9kHz-2.9GHz ..... £4500  
**H.P. 8591E** 1MHz-1.8GHz, 75 Ohm ..... £2750  
**H.P. 853A** with 8559A 100kHz-2GHz ..... £1750  
**H.P. 8558B** with Main Frame, 100kHz-1500MHz ..... £750  
**H.P. 3585A** 20Hz-40MHz ..... £2500  
**H.P. 3580A** 5Hz-50kHz ..... £600  
**ADVANTECH R431B** 10kHz-3.5GHz ..... £2750  
**EATON/AILTECH 757** 0.001-22GHz ..... £750  
**MARCONI 2382** 100Hz-400MHz, high resolution ..... £2000  
**MARCONI 2370** 30kHz-110MHz ..... from £500  
**H.P. 182** with 8557 10kHz-350MHz ..... £500  
**H.P. 141T SYSTEMS**  
**8553** 1kHz-110MHz ..... £500  
**8554** 500kHz-1250MHz ..... £750  
**8555** 10MHz-18GHz ..... £1000  
**H.P. 8443** Tracking Gen/Counter, 110MHz ..... £250  
**H.P. 8444** OPT 059 ..... £750  
**B&K 2033R** Signal Analyser ..... £550  
**H.P. 8754A** Network Analyser, 4MHz-1300MHz ..... £1250  
**H.P. 3557A** Network Analyser, 5Hz-200MHz ..... £3000  
**H.P. 3310A** Mod Domain Analyser Opt 001/003 ..... £3500  
**QNO SOKKO** OF300 Portable FFT Analyser ..... £1500  
**H.P. 8720C** Microwave Network Analyser, 50MHz-20GHz ..... £12,500

**RADIO COMMUNICATIONS TEST SETS**  
**MARCONI 2555/2555R** ..... From £1000  
**RHODE & SCHWARZ CMT** 0-1000MHz ..... £1500  
**SCHLUMBERGER 4040** ..... £750

## STEWART of READING

110 WYKEHAM ROAD, READING, BERKS. RG6 1PL  
Telephone: (0118) 9268041. Fax: (0118) 9351696  
[www.stewart-of-reading.co.uk](http://www.stewart-of-reading.co.uk)

Callers welcome 9am-5.30pm Monday to Friday (other times by arrangement)

**Used Equipment – GUARANTEED. Manuals supplied**  
This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for lists.  
Please check availability before ordering.  
CARRIAGE all units £16. VAT to be added to Total of Goods and Carriage



# ENERGY SAVING LAMPS

## LOWEST PRICES


### 2U



FROM  
**£2.49**

Energy used	Bright-ness	Dim H	D (mm)	RRP	Ultima Price	Type of Fitting
15w	75w	162	40	£4.99	<b>£2.49</b>	BC/ES
9w	45w	135	40	£4.99	<b>£2.49</b>	BC/ES

### 3U

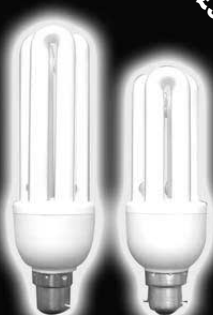

FROM  
**£3.99**

Energy used	Bright-ness	Dim H	D (mm)	RRP	Ultima Price	Type of Fitting
24w	120w	178	54	£7.99	<b>£3.99</b>	BC
18w	100w	158	54	£7.99	<b>£3.99</b>	BC

**10 Year Life**  
*Running at 3hrs a day.*

**5 x Brightness**  
*SaverLamps need only one fifth of the electricity to generate the same brightness as a traditional bulb.*

**80% Less Power**  
*Because they need less power than a traditional bulb, so you save 80% on your electricity costs.*

**Help The Environment**  
*use less electricity and do something to help preserve the world's resources.*



Type of Fitting: BC = Standard Bayonet, ES = Standard Screw, SBC = small bayonet, SES = small screw

Dim = Dimensions H = Height D = Diameter


### 4U



FROM  
**£4.99**

Energy used	Bright-ness	Dim H	D (mm)	RRP	Ultima Price	Type of Fitting
65w	325w	255	72	£19.99	<b>£9.99</b>	BC
30w	150w	178	54	£9.99	<b>£4.99</b>	BC

### FULL SPIRAL

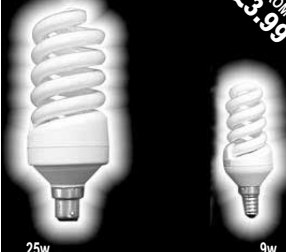

FROM  
**£3.99**

Energy used	Bright-ness	Dim H	D (mm)	RRP	Ultima Price	Type of Fitting
25w	125w	145	62	£7.99	<b>£3.99</b>	BC
20w	100w	130	62	£7.99	<b>£3.99</b>	BC
15w	75w	110	49	£7.99	<b>£3.99</b>	BC/ES
11w	60w	110	49	£7.99	<b>£3.99</b>	BC/ES
9w	45w	106	37	£8.99	<b>£4.50</b>	BC/SBC ES/SES

### LARGE SPIRAL



FROM  
**£15.99**

Energy used	Bright-ness	Dim H	D (mm)	RRP	Ultima Price	Type of Fitting
85w	425w	258	88	£29.99	<b>£15.99</b>	BC

### TRADITIONAL BULB



FROM  
**£2.99**

Energy used	Bright-ness	Dim H	D (mm)	RRP	Ultima Each	Type of Fitting
9w	45w	135	60	£5.99	<b>£2.99</b>	BC
13w	65w	150	65	£6.99	<b>£3.49</b>	BC

### CANDLE



FROM  
**£2.99**

Energy used	Bright-ness	Dim H	D (mm)	RRP	Ultima Price	Type of Fitting
9w	45w	142	41	£5.99	<b>£2.99</b>	BC/SBC ES/SES
7w	35w	142	41	£5.99	<b>£2.99</b>	BC/SBC ES/SES

### REFLECTOR



FROM  
**£3.99**

Energy used	Bright-ness	Dim H	D (mm)	RRP	Ultima Price	Type of Fitting
20w	100w	165	97	£9.99	<b>£4.99</b>	BC
13w	65w	112	63	£7.99	<b>£3.99</b>	BC

### LARGE GLOBAL



FROM  
**£4.99**

Energy used	Bright-ness	Dim H	D (mm)	RRP	Ultima Each	Type of Fitting
24w	100w	172	120	£8.99	<b>£4.99</b>	BC

#### HOW TO ORDER:

On the Web: Visit [www.ultimalamps.com](http://www.ultimalamps.com)

By Phone: Using your credit card or switch card number. Our lines are open 9am - 5.30pm, Monday to Friday.

By Fax: Fax your order through on 01279 821300 with full payment details.

By Post: You may post an order to the address below. We advise you not to send cash in the post. If you do, please send it by registered mail.

Payment Method: You may pay by cheque or postal order. We also accept payment by Access, Mastercard, Visa, Delta Card and Switch. Please note that we will add a 2% surcharge for processing credit card orders.

Post and Packing: Post and Packing is FREE on all orders over £100 (UK Mainland only - orders outside UK on request). We charge £5.95 P&P on all orders under £100. Dimensions are approximate and for guidance only. Please make cheques payable to Ultima Networks PLC.

Ultima Lamps, Akhter House, Perry Road, Harlow, Essex, CM18 7PN

Tel: 01279 821222 Fax: 01279 821300

Email: [sales@ultimalamps.com](mailto:sales@ultimalamps.com)

All Prices Include VAT

(Ultima Lamps is a division of Ultima Networks PLC)

[www.ultimalamps.com](http://www.ultimalamps.com)

## MAIL ORDER ONLY • CALLERS BY APPOINTMENT

### EPE PROJECT PICS

**Programmed PICs for \*EPE Projects**  
12C508/9 - £3.90; 16F627/8 - £4.90  
16C84/16F84/16C71 - £5.90  
16F876/877 - £10.00  
All inc. VAT and Postage  
(\*Some projects are copyright)

### EPE MICROCONTROLLER P.I. TREASURE HUNTER

The latest MAGENTA DESIGN - highly stable & sensitive - with I.C. control of all timing functions and advanced pulse separation techniques.

- High stability drift cancelling
- Easy to build & use
- No ground effect, works in seawater



- Detects gold, silver, ferrous & non-ferrous metals
- Efficient quartz controlled microcontroller pulse generation.
- Full kit with headphones & all hardware

**KIT 847 ..... £63.95**

### PIC PIPE DESCALER

- SIMPLE TO BUILD
- HIGH POWER OUTPUT
- AUDIO & VISUAL MONITORING
- SWEPT FREQUENCY

An affordable circuit which sweeps the incoming water supply with variable frequency electromagnetic signals. May reduce scale formation, dissolve existing scale and improve lathering ability by altering the way salts in the water behave. Kit includes case, P.C.B., coupling coil and all components. High coil current ensures maximum effect. L.E.D. monitor.



**KIT 868 ..... £22.95 POWER UNIT.....£3.99**

### MICRO PEST SCARER

Our latest design - The ultimate scarer for the garden. Uses special microchip to give random delay and pulse time. Easy to build reliable circuit. Keeps pets/pests away from newly sown areas, play areas, etc. uses power source from 9 to 24 volts.

- RANDOM PULSES
- HIGH POWER
- DUAL OPTION



Plug-in power supply £4.99

**KIT 867 ..... £19.99**

**KIT + SLAVE UNIT ..... £32.50**

### WINDICATOR

A novel wind speed indicator with LED readout. Kit comes complete with sensor cups, and weatherproof sensing head. Mains power unit £5.99 extra.

**KIT 856 ..... £28.00**

## ★ TENS UNIT ★

### DUAL OUTPUT TENS UNIT

As featured in March '97 issue.

Magenta have prepared a FULL KIT for this, excellent new project. All components, PCB, hardware and electrodes are included. Designed for simple assembly and testing and providing high level dual output drive.

**KIT 866. . Full kit including four electrodes £32.90**

Set of 4 spare electrodes £6.50

### 1000V & 500V INSULATION TESTER



Superb new design. Regulated output, efficient circuit. Dual-scale meter, compact case. Reads up to 200 Megohms.

Kit includes wound coil, cut-out case, meter scale, PCB & ALL components.

**KIT 848. .... £32.95**

## EPE TEACH-IN 2000

Full set of top quality NEW components for this educational series. All parts as specified by EPE. Kit includes breadboard, wire, croc clips, pins and all components for experiments, as listed in introduction to Part 1.

\*Batteries and tools not included.

**TEACH-IN 2000 -**


**KIT 879 £44.95**

**MULTIMETER £14.45**

### SPACEWRITER

An innovative and exciting project. Wave the wand through the air and your message appears. Programmable to hold any message up to 16 digits long. Comes pre-loaded with "MERRY XMAS". Kit includes PCB, all components & tube plus instructions for message loading.

**KIT 849 ..... £16.99**

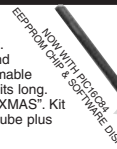

### 12V EPROM ERASER

A safe low cost eraser for up to 4 EPROMs at a time in less than 20 minutes. Operates from a 12V supply (400mA). Used extensively for mobile work - updating equipment in the field etc. Also in educational situations where mains supplies are not allowed. Safety interlock prevents contact with UV.

**KIT 790 ..... £29.90**

### SUPER BAT DETECTOR

1 WATT O/P, BUILT IN SPEAKER, COMPACT CASE 20kHz-140kHz NEW DESIGN WITH 40kHz MIC.

A new circuit using a 'full-bridge' audio amplifier i.c., internal speaker, and headphone/tape socket. The latest sensitive transducer, and 'double balanced mixer' give a stable, high performance superheterodyne design.


**KIT 861 ..... £24.99**

ALSO AVAILABLE Built & Tested... £39.99



### 68000 DEVELOPMENT TRAINING KIT

- NEW PCB DESIGN
- 8MHz 68000 16-BIT BUS
- MANUAL AND SOFTWARE
- 2 SERIAL PORTS
- PIT AND I/O PORT OPTIONS
- 12C PORT OPTIONS

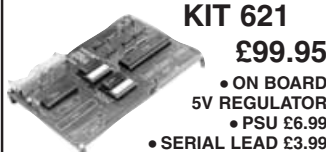

**KIT 621**

**£99.95**

- ON BOARD 5V REGULATOR
- PSU £6.99
- SERIAL LEAD £3.99

### Stepping Motors

MD100...Std 100 step...£9.99

MD200...200 step...£12.99

MD24...Large 200 step...£22.95



### MOSFET MkII VARIABLE BENCH POWER SUPPLY 0-25V 2-5A

Based on our Mk1 design and preserving all the features, but now with switching pre-regulator for much higher efficiency. Panel meters indicate Volts and Amps. Fully variable down to zero. Toroidal mains transformer. Kit includes punched and printed case and all parts. As featured in April 1994 EPE. An essential piece of equipment.



Kit No. 845 ..... £64.95

### ULTRASONIC PEST SCARER

Keep pets/pests away from newly sown areas, fruit, vegetable and flower beds, children's play areas, patios etc. This project produces intense pulses of ultrasound which deter visiting animals.

- KIT INCLUDES ALL COMPONENTS, PCB & CASE
- EFFICIENT 100V TRANSDUCER OUTPUT
- COMPLETELY INAUDIBLE TO HUMANS



- UP TO 4 METRES RANGE
- LOW CURRENT DRAIN

**KIT 812. .... £15.00**

### SIMPLE PIC PROGRAMMER

**KIT 857... £12.99**

Includes PIC16F84 chip disk, lead, plug, p.c.b., all components and instructions


Extra 16F84 chips £3.84 Power Supply £3.99



## MAGENTA BRAINBOT I & II

- Full kit with ALL hardware and electronics
- As featured in *EPE* Feb '03 – KIT 910
- Seeks light, beeps, avoids obstacles
- Spins and reverses when 'cornered'
- Uses 8-pin PIC
- ALSO KIT 911 – As 910 PLUS programmable from PC serial port – leads and software CD provided

**NEW**

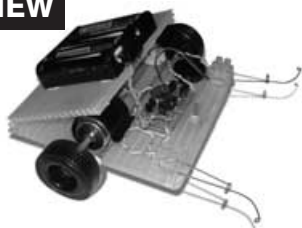

**KIT 910 £16.99    KIT 911 £24.99**

## PIC 16F84 MAINS POWER 4-CHANNEL CONTROLLER & LIGHT CHASER

- ZERO VOLT SWITCHING
- OPTO ISOLATED 5 Amp
- 12 KEYPAD CONTROL
- HARD-FIRED TRIACS
- WITH SOURCE CODE
- SPEED & DIMMING POT.
- EASILY PROGRAMMED

**Kit 855 £39.95**

## PIC 16F84 LCD DISPLAY DRIVER

INCLUDES 1-PIC16F84 WITH DEMO PROGRAM SOFTWARE DISK, PCB, INSTRUCTIONS AND 16-CHARACTER 2-LINE

**LCD DISPLAY**

**Kit 860 £19.99**

Power Supply £3.99

FULL PROGRAM SOURCE CODE SUPPLIED – DEVELOP YOUR OWN APPLICATION!


Another super PIC project from Magenta. Supplied with PCB, industry standard 2-LINE x 16-character display, data, all components, and software to include in your own programs. Ideal development base for meters, terminals, calculators, counters, timers – Just waiting for your application!

## 8-CHANNEL DATA LOGGER

As featured in Aug./Sept. '99 *EPE*. Full kit with Magenta redesigned PCB – LCD fits directly on board. Use as Data Logger or as a test bed for many other 16F877 projects. Kit includes programmed chip, 8 EEPROMs, PCB, case and all components.

**KIT 877 £49.95 inc. 8 x 256K EEPROMS**

**ICEBREAKER**  
□□□□□□□□□□

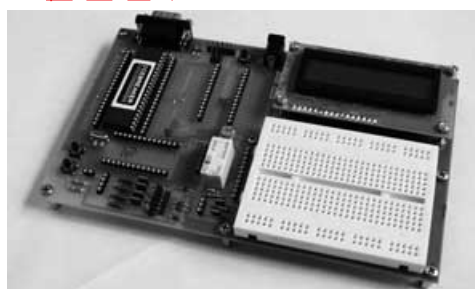

## PIC Real Time In-Circuit Emulator

- Icebreaker uses PIC16F877 in circuit debugger
- Links to Standard PC Serial Port (lead supplied)
- Windows™ (95+) Software included
- Works with MPASM and MPLAB Microchip software
- 16 x 2 L.C.D., Breadboard, Relay, I/O devices and patch leads supplied

As featured in March '00 *EPE*. Ideal for beginners AND advanced users. Programs can be written, assembled, downloaded into the microcontroller and run at full speed (up to 20MHz), or one step at a time.

Full emulation means that all I/O ports respond exactly and immediately, reading and driving external hardware.

Features include: Reset; Halt on external pulse; Set Breakpoint; Examine and Change registers, EEPROM and program memory; Load program, Single Step with display of Status, W register, Program counter, and user selected 'Watch Window' registers.

**KIT 900 ... £34.99**

POWER SUPPLY £3.99    STEPPING MOTOR 100 STEP £9.99

## EPE PIC TOOLKIT 3

**NEW**

- THE LATEST TOOLKIT BOARD – 8, 18, 28 AND 40-PIN CHIPS
- MAGENTA DESIGNED P.C.B. WITH COMPONENT LAYOUT AND EXTRAS
- L.C.D., BREADBOARD AND PIC CHIP INCLUDED
- ALL TOP QUALITY COMPONENTS AND SOFTWARE SUPPLIED

**KIT 880 ... £34.99 with 16F84 ... £39.99 with 16F877**

## PIC TOOLKIT V2

- SUPER UPGRADE FROM V1
- 18, 28 AND 40-PIN CHIPS
- READ, WRITE, ASSEMBLE & DISASSEMBLE PICS
- SIMPLE POWER SUPPLY OPTIONS 5V-20V
- ALL SWITCHING UNDER SOFTWARE CONTROL
- MAGENTA DESIGNED PCB HAS TERMINAL PINS AND OSCILLATOR CONNECTIONS FOR ALL CHIPS
- INCLUDES SOFTWARE AND PIC CHIP

**KIT 878 ... £22.99 with 16F84 ... £29.99 with 16F877**

## EPE PIC Tutorial

**At last! A Real, Practical, Hands-On Series**

- **Learn Programming from scratch using PIC16F84**
- **Start by lighting I.e.d.s and do 30 tutorials to Sound Generation, Data Display, and a Security System.**
- **PIC TUTOR Board with Switches, I.e.d.s, and on board programmer**

## PIC TUTOR BOARD KIT

Includes: PIC16F84 Chip, TOP Quality PCB printed with Component Layout and all components\* (\*not ZIF Socket or Displays). Included with the Magenta Kit is a disk with Test and Demonstration routines.

**KIT 870 .... £27.95, Built & Tested .... £42.95**

Optional: Power Supply – £3.99, ZIF Socket – £9.99

**LCD Display ..... £7.99    LED Display ..... £6.99**

Reprints Mar/Apr/May 98 – £3.00 set 3

## SUPER PIC PROGRAMMER

- READS, PROGRAMS, AND VERIFIES
- WINDOWS™ SOFTWARE
- PIC16C AND 16F – 6X, 7X, AND 8X
- USES ANY PC PARALLEL PORT
- USES STANDARD MICROCHIP
- HEX FILES
- OPTIONAL DISASSEMBLER SOFTWARE (EXTRA)
- PCB, LEAD, ALL COMPONENTS, TURNED-PIN SOCKETS FOR 18, 28, AND 40 PIN ICs

- SEND FOR DETAILED INFORMATION – A SUPERB PRODUCT AT AN UNBEATABLE LOW PRICE.

**Kit 862    £29.99**

Power Supply £3.99

**DISASSEMBLER SOFTWARE    £11.75**

## PIC STEPPING MOTOR DRIVER

INCLUDES PCB, PIC16F84 WITH DEMO PROGRAM, SOFTWARE DISC, INSTRUCTIONS AND MOTOR.

**Kit 863 £18.99**

FULL SOURCE CODE SUPPLIED ALSO USE FOR DRIVING OTHER POWER DEVICES e.g. SOLENOIDS

Another Magenta PIC project. Drives any 4-phase unipolar motor – up to 24V and 1A. Kit includes all components and 48 step motor. Chip is pre-programmed with demo software, then write your own, and re-program the same chip! Circuit accepts inputs from switches etc and drives motor in response. Also runs standard demo sequence from memory.

**MAGENTA**

All prices include VAT. Add £3.00 p&p. Next day £6.99

Tel: 01283 565435    Fax: 01283 546932    E-mail: sales@magenta2000.co.uk

# EVERYDAY PRACTICAL ELECTRONICS

THE No.1 MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

**VOL. 32 No. 6 JUNE 2003**

## Editorial Offices:

EVERYDAY PRACTICAL ELECTRONICS EDITORIAL  
WIMBORNE PUBLISHING LTD., 408 WIMBORNE ROAD EAST,  
FERNDOWN, DORSET BH22 9ND  
Phone: (01202) 873872. Fax: (01202) 874562.

Email: enquiries@epemag.wimborne.co.uk

Web Site: www.epemag.wimborne.co.uk

EPE Online (downloadable version of EPE): www.epemag.com

EPE Online Shop: www.epemag.wimborne.co.uk/shopdoor.htm

See notes on Readers' Technical Enquiries below – we regret lengthy technical enquiries cannot be answered over the telephone.

## Advertisement Offices:

EVERYDAY PRACTICAL ELECTRONICS ADVERTISEMENTS  
MILL LODGE, MILL LANE,

THORPE-LE-SOKEN, ESSEX CO16 0ED

Phone/Fax: (01255) 861161 Email: epeads@aol.com

## SOMETHING FOR NOTHING ...

When I was a young lad most enthusiasts' first experience of electronics was to build a radio set. Magazines like *Boys Own* would show constructional projects for crystal sets or one valve radios and later for simple transistor designs. In those days electronics was not the wide ranging hobby it is now, and until *Practical Electronics* was launched in 1964 hobbyists were served only by wireless magazines.

There was always something exciting about building your first radio and receiving stations from around the world – many of the early designs included a short-wave band. I well remember receiving the World Service broadcast from a transmitter near my home on a "set" consisting of a block of wood, a razor blade, lead from a pencil and a pair of ex-army headphones, that was really something for nothing.

In this issue Raymond Haigh starts a new series on *Radio Circuits* which we hope will recapture the excitement for some readers. There is even a crystal set to build and, over the course of the series, a wide range of other sets building up to a superhet design. Of course, there is no longer the incentive of saving money by making your own receiver that there once was – in those days a number of suppliers advertised kits for a wide range of radio sets – but construction is still very educational and that, teamed with the pride of having built it yourself, is part of what our hobby is all about.

## ... AND YOUR KICKS FOR FREE!

As I write, I note with some satisfaction how helpful our readers are to each other. Requests for information on our *Chat Zone* are quickly met with all sorts of help and advice from around the globe. It is great to see that this freely offered help is still part of our hobby. However, I also note that some people seem to be happy to use that assistance without as much as a "Thank You".

It would be sad if the advice were not so forthcoming in future because a certain section of readers simply take it for granted. A while ago an overseas reader asked about some highly unusual aspect of high power electronics and then started berating the *Chat Zone* because he had received no replies. He seemed to feel that we should have a range of experts in every field to provide instant assistance.

It is, of course, not quite like that, we are a hobbyist magazine run by enthusiasts and helped by fellow enthusiasts who are often willing to give their time and knowledge to help fellow readers. If you receive such help from another reader or even from a freelance *EPE* contributor, it costs nothing to say thanks – let us retain some old world courtesy, or instill it where it has waned.

*Mike Kenward*

## AVAILABILITY

Copies of *EPE* are available on subscription anywhere in the world (see opposite), from all UK newsagents (distributed by COMAG) and from the following electronic component retailers: Omni Electronics and Yobo Electronics (S. Africa). *EPE* can also be purchased from retail magazine outlets around the world. An Internet on-line version can be purchased and downloaded for just \$10.99US (approx £7) per year available from [www.epemag.com](http://www.epemag.com)

## SUBSCRIPTIONS

Subscriptions for delivery direct to any address in the UK: 6 months £15.50, 12 months £29.50, two years £54; Overseas: 6 months £18.50 standard air service or £27.50 express airmail, 12 months £35.50 standard air service or £53 express airmail, 24 months £66 standard air service or £101 express airmail.

Online subscriptions, for downloading the magazine via the Internet, \$10.99US (approx £7) for one year available from [www.epemag.com](http://www.epemag.com).

Cheques or bank drafts (in £ sterling only) payable to *Everyday Practical Electronics* and sent to EPE Subs. Dept., Wimborne Publishing Ltd, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872. Fax: 01202 874562. Email: subs@epemag.wimborne.co.uk. Also via the Web at: <http://www.epemag.wimborne.co.uk>. Subscriptions start with the next available issue. We accept MasterCard, Amex, Diners Club, Switch or Visa. (For past issues see the *Back Issues* page.)

## BINDERS

Binders to hold one volume (12 issues) are available from the above address. These are finished in blue p.v.c., printed with the magazine logo in gold on the spine. Price £6.95 plus £3.50 p&p (for overseas readers the postage is £6.00 to everywhere except Australia and Papua New Guinea which cost £10.50). Normally sent within seven days but please allow 28 days for delivery – more for overseas.

Payment in £ sterling only please. Visa, Amex, Diners Club, Switch and MasterCard accepted. Send, fax or phone your card number, card expiry date and card security code (the last 3 digits on or just under the signature strip), with your name, address etc. Or order on our secure server via our UK web site. Overseas customers – your credit card will be charged by the card provider in your local currency at the existing exchange rate.

Editor: MIKE KENWARD

Deputy Editor: DAVID BARRINGTON

Technical Editor: JOHN BECKER

Business Manager: DAVID J. LEAVER

Subscriptions: MARILYN GOLDBERG

Administration: FAY KENWARD

Editorial/Admin: (01202) 873872

Advertisement Manager:

PETER J. MEW, Frinton (01255) 861161

Advertisement Copy Controller:

PETER SHERIDAN, (01202) 873872

On-Line Editor: ALAN WINSTANLEY

EPE Online (Internet version) Editors:

CLIVE (MAX) MAXFIELD and ALVIN BROWN

## READERS' TECHNICAL ENQUIRIES

E-mail: techdept@epemag.wimborne.co.uk

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years old. Letters requiring a personal reply must be accompanied by a stamped self-addressed envelope or a self-addressed envelope and international reply coupons.

## PROJECTS AND CIRCUITS

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it.

A number of projects and circuits published in *EPE* employ voltages that can be lethal. You should not build, test, modify or renovate any item of mains powered equipment unless you fully understand the safety aspects involved and you use an RCD adaptor.

## COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers (see *Shoptalk*). We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

## ADVERTISEMENTS

Although the proprietors and staff of *EVERYDAY PRACTICAL ELECTRONICS* take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are bona fide, the magazine and its Publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or in inserts.

The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture.

## TRANSMITTERS/BUGS/TELEPHONE EQUIPMENT

We advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the UK. Readers should check the law before buying any transmitting or telephone equipment as a fine, confiscation of equipment and/or imprisonment can result from illegal use or ownership. The laws vary from country to country; readers should check local laws.





# FIDO PEDOMETER

MIKE BOYDEN



*Keeping track of how far you've walked!*

**T**REKKING guidebooks often refer to distances between minor landmarks for navigation purposes. This is not a handicap when navigating across countryside that is full of easily distinguished geographical or man-made features. However, when the author was trekking in the more remote locations of the French Pyrenees, estimating the distance walked was difficult and retracing steps became frustrating.

Fido was developed in an effort to look for navigational signs in roughly the expected location. It can record the distance traversed by a walker or runner and was extended to calculate average speed – a useful addition when planning how long it will take to get back to comfort!

A PIC16F84A microcontroller is employed and the unit can be set to work in miles or kilometres.

### WALKING THE WALK

Some background research revealed that estimation of the distance travelled by walkers (or runners) has presented engineers with some difficulty.

Arctic explorers measured movement by towing a “log” in the form of a rotating wheel that made connection with the ground from the rear of a sledge. The turns of the wheel were counted by a gear mechanism, which calculated and displayed the distance covered on a clock face. However, walkers and runners need to move freely, unencumbered with wheels and other contraptions.

Inertial guidance systems have for many years offered a “contactless” means of determining position. The theory is that the distance moved by a body can be determined if the acceleration of the body is accurately known in time. Gyroscopes (looking very much like the toys with which we are familiar) are widely used to detect acceleration. Aeroplanes and ships use these systems extensively.

The problem with using inertial systems is that measuring very small horizontal accelerations when a person is walking ( $1\text{mg}$  or  $1\cdot10^{-3}\text{g}$ ) over a long period of time (say 12 hours) leads to an unacceptable level of error (i.e. 25%). Also, the earth's acceleration ( $\text{g}$ ) needs to be

removed from the calculations, further increasing the complexity and potential for error. The term  $\text{g}$  refers to the acceleration exerted on an object at the surface of the earth, which is approximately  $9\cdot81\text{ms}^{-2}$ .

More recently, a mathematical link between the vertical acceleration of the human hip joint and stride length has been established. By combining microcontrollers and accelerometers using MEMS (Micro Electrical Mechanical Systems) technology – see *Teach-in 2002*, Aug '02 – commercial pedometers started to emerge.

The developments combined to reduce errors to about 8%, which is the sort of accuracy that commercial units now offer. However, the author considered the cost of using an accelerometer as rather excessive, as was purchasing a Global Positioning System (GPS) system.

It was then discovered that Army personnel are trained to take a compass

Table 1. Results of Stride Counting

Type of exercise	Gradient %	Strides (1 mile)
Walk (leisurely 3-5mph)	0	2280
Run (light 5-0mph)	0	1960
Walk (leisurely 3-5mph)	10	2310
Run (light 5-0mph)	10	1982

bearing and count the number of steps in a particular direction. Walking the same number of steps on a reciprocal bearing should return them to the same spot. The problem here is that the length of a stride can change, depending upon whether the subject is running, moving up or down a gradient, or simply tired. Some texts suggested that stride length could vary by as much as 40%, which would give unacceptable accumulative errors.

Nevertheless, in an effort to keep costs low, the literature was reviewed regarding the “stride counting” approach and a number of stride counting tests were made.

### GET WALKING

The treadmill machine at the author's local gym was used to count the number of strides to run (and walk) one mile. The results are listed in Table 1. The count was also noted for a variety of gradients (the treadmill incorporated a gradient adjustment) and various stages of tiredness (ranging from mildly hot, to “get a doctor”). Minor gradient changes did not appear to introduce major errors, but the type of motion (i.e. walking or running) had a significant influence on stride length.

It was concluded that providing a person's unique “stride constant” (strides per mile/kilometre) could be estimated and stored, then a microcontroller could use this as a basis of a distance monitor, without the need for complex accelerometers.

Users would have to accept that the readings for steep terrain or excessive tiredness would become increasingly inaccurate, and that each pedometer would need to be calibrated to the type of exercise and individual's stride length. Providing these limitations were accepted,



a unit offering about 10% accuracy was considered achievable and acceptable, given the simplicity of design.

## DEVELOPMENT

The next problem was to reliably detect and count strides. After a little experimentation it was found that two opposing tilt switches, S1 and S2, pointing downwards by about 10 degrees, could be made to track the cycle of a leg movement.

Referring to the full circuit diagram in Fig.1, the tilt switches are connected respectively to the RA0 and RA1 pins of a PIC16F84A on one side and to the 0V line on the other. The pins are biased normally-high via resistors R1 and R2, and i.e.d.s D1 and D2.

As illustrated in Fig.2, when the knee is raised the conductive fluid in switch S1 is forced momentarily onto its contacts, closing them, so applying logic 0 to pin RA0. Pin RA1 remains at logic 1. As the foot is placed down, both S1 and S2 open, and both RA0 and RA1 are set at logic 1. As the knee is raised in the last part of the stride then S1 opens and RA0 goes to logic 1, but S2 closes, with RA1 at logic 0.

The prototype was taken to the local gym for testing, where it was found by experimentation that the detection unit operated best when strapped to the left upper calf. Note that the software only allows the unit to function in this position.

The software verifies the correct switch closure sequence and also includes some time delays. These are necessary to reduce the sensitivity of the system and curtail the number of "bad reads" due to the equivalent of contact bounce.

For simplicity and cost effectiveness, a single 7-segment i.e.d. display was used for all of the display and control interfacing, using a cyclic technique to display the various factors. A sounder, WD1, is included to signal each valid step when in the Learn mode – this improved the setting-up procedure. The mode of operation is selected by means of a 3-way toggle switch, S3.

## DISTANCE AND TIME

The main computation undertaken by Fido requires distance and elapsed time to be known.

**Time:** Fido's clock rate is set by a 20ms interrupt generated by a TMR0 overflow. Although this would not be accurate enough for daily time keeping, it is accurate enough for this application. The 20ms "ticks" are counted and eventually used to increment a "6-minute", 16-bit timer-counter (Ttimehi, Ttimelo).

**Distance:** If Fido is to work in miles then the number of strides recorded to complete one mile is entered into Fido during the Learn mode. Once the calibration distance has been walked, a switch adjustment ensures that the number of strides (the stride constant) is stored in the PIC's non-volatile Data EEPROM. (The software is written to store the stride value for every stride that is taken after the first 255 strides.) The value placed into the EEPROM is calculated from:

$$\text{Stride Constant} = \text{Strides Counted} / \text{ten}$$

The Stride Constant is subtracted from the 16-bit stride counter (distlo, disthi) to see if 0.1 of a mile has been walked. If it

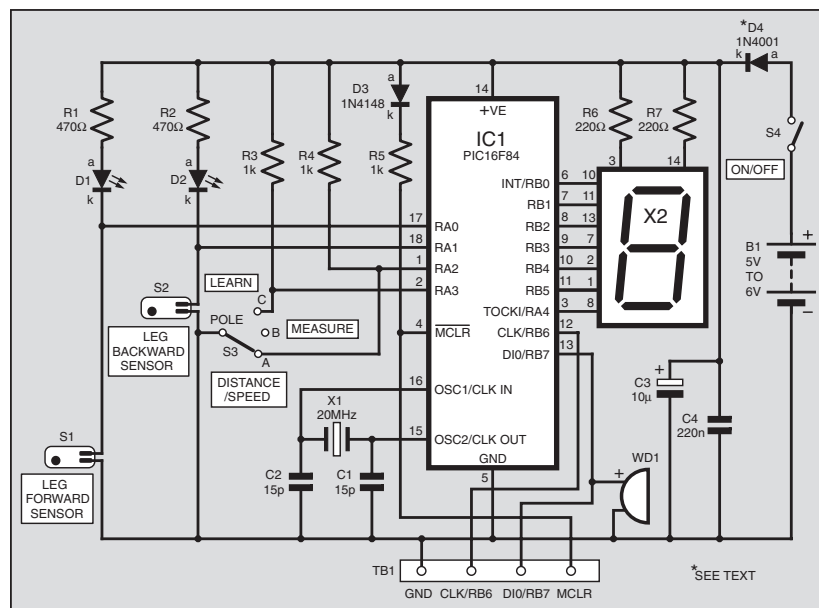


Fig.1. Complete circuit diagram for the Fido Pedometer.

has, then this is then used to increment a "0.1 mile", 16-bit Total Distance counter (Tdisthi, Tdistlo).

Distance is recorded and displayed by means of a number of incrementing decimal counters.

## CALCULATIONS

Average speed is calculated at each 6-minute interval and a "snapshot" of the Distance Counter is stored in Tdisthi1 and Tdistlo1. The average speed is then derived from:

$$\begin{aligned} \text{Average speed (miles/hour)} \\ &= 0.1 \text{ mile counter} / 6\text{-minute counter} \\ &\text{i.e.} \\ &(\text{Tdisthi1, Tdistlo1}) / (\text{Ttimehi, Ttimelo}) \end{aligned}$$

Hence the average speed displayed is the average since the time that Fido was switched on. If the walker stops for lunch, and Fido is left on, the average speed will be seen to steadily fall. If the average speed is required "per leg" of a journey, then simply record the distance together with average speed and turn off Fido, thereby resetting the unit in readiness for the next phase of your walk.

A "standard" library of 16-bit unsigned integer mathematical functions from Microchip's website ([www.microchip.com](http://www.microchip.com)) were used in this application. "Invalid" divisions (i.e. 1 / 0 or 2 / 3) are returned as 0, rather than the true mathematical results of infinity or a fraction. Mathematically, Fido has a maximum capability of approximately 6,500 miles and 270 days! A reset of the unit is forced if the distance exceeds 99.9 units, but the time has no restrictions.

## INHIBITING ERRORS

Although Fido computes and displays distance immediately, the first computed value of

speed is only available for display six minutes after turning Fido on. Distance and average speed values displayed in the first 0.5 miles should be treated with caution as the small reading errors represent a significant proportion of the initial measured values. The errors rapidly diminish as the time and distance measurements increase.

The measurement technique assumes that most of the movement is a genuine walking or running motion, hence the errors contributed by a few "stumbles" are greatly reduced when averaged against the number of strides that equate to a mile for individual walkers.

## RESOURCES

Software for this design is available on 3.5-inch disk (Disk 6) from the Editorial Office – a nominal handling charge applies (see the *EPE PCB Service* page). It is also available for free download from the *EPE* ftp site. The easiest way into this is via the home page [www.epemag.wimborne.co.uk](http://www.epemag.wimborne.co.uk). Click the top link saying ftp site (downloads), then take the path pub/PICS/Fido.

## CONSTRUCTION

Fido is constructed on a single printed circuit board (p.c.b.) whose full-size track layout and component positions are shown


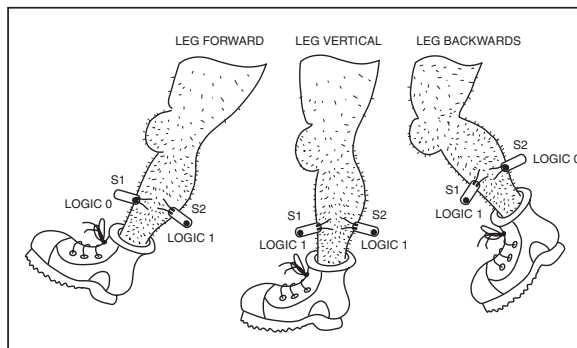


Fig.2. Fido's logic (with or without hairy legs!).

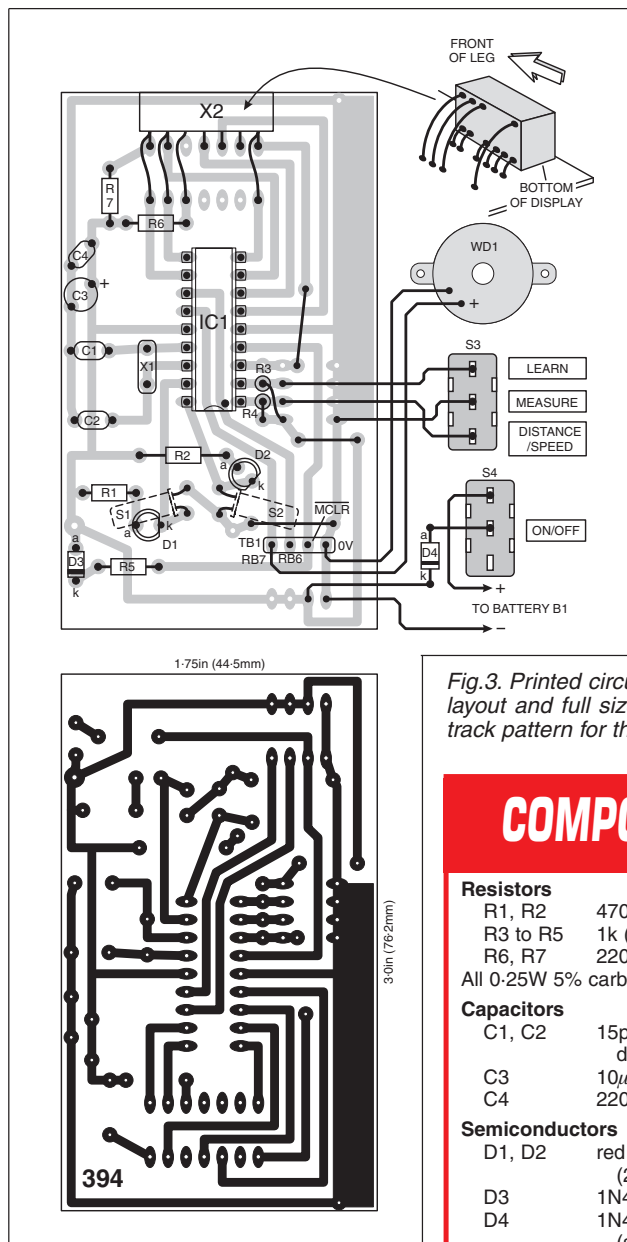



in Fig.3. This board is available from the *EPE PCB Service*, code 394.

Mount the components in order of increasing size. Correctly observe the polarity of the diodes and electrolytic capacitor C3. A socket must be used for IC1. Do not insert the PIC until the board has been completed and fully checked.

The 7-segment l.e.d. is not mounted flush with the board. Rather, to assist viewing when walking, it is mounted on its side. The decimal points are at the lower end of the display and these should point towards the rear of the calf when strapped to the left leg. The lower pins of the display are tightly turned into the p.c.b. Small rigid extension wires link the required upper pins to the p.c.b., see Fig.3.

Connector TB1 provides the programming connection points for those who wish to program their PIC *in situ*, but note that they are not in John Becker's "standard" TK3 order. Pin RB7 is also the pin to which the sounder WD1 is connected, but

Fig.3. Printed circuit board component layout and full size copper foil master track pattern for the Fido pedometer.

## COMPONENTS

### Resistors

R1, R2	470Ω (2 off)
R3 to R5	1k (3 off)
R6, R7	220Ω (2 off)
All 0.25W 5% carbon film	

### Capacitors

C1, C2	15p polystyrene or disc ceramic (2 off)
C3	10μ radial elect. 10V
C4	220n disc ceramic

### Semiconductors

D1, D2	red l.e.d. (low current) (2 off)
D3	1N4148 signal diode (see text)
D4	1N4001 rectifier diode (see text)
IC1	PIC16F84A microcontroller preprogrammed (see text)


### Miscellaneous

X1	20MHz crystal
X2	7-segment display, common anode
S1, S2	tilt switch (2 off)
S3	s.p.d.t. centre off toggle switch, spring biased one direction
S4	s.p.s.t. min. toggle switch
WD1	buzzer
B1	5V to 6V battery (4 x AAA), with holder and clips (see text)

Printed circuit board, available from the *EPE PCB Service*, code 394; slim-line plastic case (80mm x 62mm x 39mm); custom-made cloth pouch (see text); 18-pin d.i.l. socket; 14-pin d.i.l. socket; solder, etc.

Approx. Cost  
Guidance Only

**£16**  
excl. case & batts

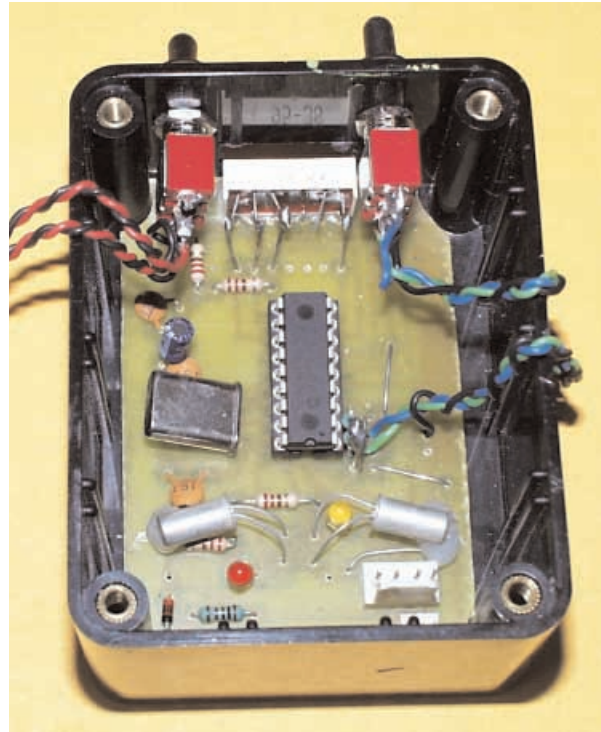

the sounder should be disconnected if/when on-board programming is to be performed.

Fido was mounted in a slim-line plastic case, measuring 80mm x 62mm x 39mm, with suitable holes cut for the l.e.d.s, 7-segment display and the switches. Allow room for the battery (see later). It may also be necessary to drill small holes to let the sounder be heard. To protect Fido from rain and mud, rubber dust covers are recommended for the switches and a small piece of clear plastic should cover the 7-segment display.

## SETTING UP

Ensure the tilt switches are angled pointing slightly downwards and both l.e.d.s, D1 and D2, are off. Ensure switch S3 is centred (off). Turn Fido on in the vertical position; the sounder will then signal that the timer function has started.

Sway Fido back and forth in a motion as if it were the bob of a pendulum (which effectively is what a leg is, i.e. pivoted at the hip). Each sway will flash, in turn, the horizontal bars of the 7-segment display.

The top, middle and lower bars will not necessarily flash in a perfectly smooth sequence when swayed – this is normal. When vertical, the centre bar will flash. The l.e.d.s D1 and D2 go on and off as appropriate when the tilt switches make and break their contacts.


Switching to Learn mode will make alignment easier, as each valid stride is signalled by a bleep, but be sure not to exceed 255 "test" steps, otherwise Fido will assume that a new stride constant is to be stored. Reset by turning off and back on again.

Note that the bleep will not always occur in exactly the same leg position. However, only one bleep should be heard per stride cycle. Adjust the tilt switch positions if necessary. Once Fido is "walking" reliably, open the box and secure the location of the tilt switches using hot melt glue.

Turning off power to the unit will reset to zero the distance and speed displays and calculations. If a new stride constant has



*Fido's "collar", worn around the left upper calf.*

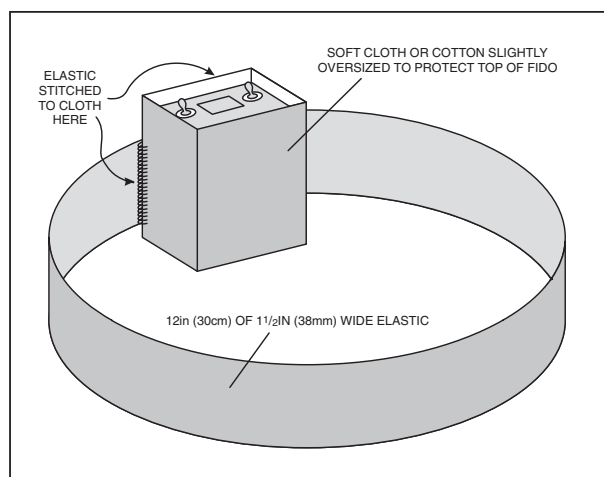

*Fig.4. Construction of Fido's "pouch and collar"!*

**Table 2. Mode Switch S3 Functions**

Position	Mode	Function	Display	Tone
A	Display	Display distance/average speed	P0-0 A0-0 ...	Silent
B	Measure	Measure distance speed	Descending bars	Every mile/km
C	Learn	Learn strides per mile/km	L and bars descending	< 255 strides 1 bleep > 255 strides 2 bleeps

been entered using Learn mode then this will be remembered despite power being turned off.

The unit can only be used on the left leg. Changing orientation would require changes to be made to the software, a matter on which no advice is offered.

The 7-segment display will not be readable from a normal standing position, so it is necessary to make a strap-on pouch to allow Fido to be lifted out and read when required. The author's arrangement is shown in Fig.4. The pouch is sewn to a loop of 50mm wide elastic. The walking boot is passed through the elastic hoop and Fido is slipped into the pouch at the top of the calf just below the knee joint.

Note that as the calf muscle is rounded, so Fido points slightly "inward" when viewed from above. This is normal, but check that Fido does not significantly shift from this position, especially when running.

## FIDO'S APPETITE

Part of the design criteria for Fido assumed that it might be used in rugged and remote locations, where constant battery changes would not be welcome. When walking, the prototype consumed an average of 27mA, but by using low current I.e.d.s and "flashing" the display whenever possible, this was reduced to an average of 13mA.

The plastic case is sized to house four AAA alkaline batteries rated at 1200mA/hr. No battery duration problems have been experienced in the prototype, despite constant testing over a period of two months.

It should be noted that the PIC16F84A has a maximum supply voltage limit of 5.5V, whereas four AAA cells will nominally deliver 6V. Consequently, it is recommended that a 1N4001 rectifier

diode should be inserted in the positive line between switch S4 and the p.c.b. to drop the voltage reaching the PIC by about 0.6V.

## TAKING FIDO FOR A WALK

When first switched on, if Fido is not upright the display will remain blank and the timing function will be disabled. When upright, the centre bar of the display will flash and a short bleep from the sounder will indicate that the unit is now functioning.

Slip Fido into its pouch situated on the left calf and walk with Mode switch S3 in position A (centre). As progress is made, each of the horizontal bars of the 7-segment display will flash as each stage of a valid walk cycle is detected. When stationary and vertical, the middle bar will flash at about 1Hz.

Next, Mode switch S3 can be tested. It is a 3-position (centre-off) toggle switch. Position A is "spring return loaded". Its functions are shown in Table 2.

### Display Mode (S3-A)

Only when Fido is in the vertical position (middle bar flickering) can switch position S3-A be "pulsed". This will trigger a display cycle on the single digit 7-segment display, showing progress (distance covered) and average speed.

If Fido has been calibrated in miles, the letter P (progress) is displayed first, followed by the miles units, then a decimal point (a dash) followed by tenths of a mile. After a short pause, the letter A (average speed) is displayed and the average speed in miles/hour is shown in the same format as distance. If the distance or speed exceeds 9.9 then the tens of miles digit will automatically appear.

Once a display cycle is completed, the unit will return to measure mode.

### Measure Mode (S3-B)

When switch position S3-B is selected (centre), Fido silently counts strides and displays each stage of a valid leg movement by flashing the top, middle and lower bars of the 7-segment display. Every mile (or kilometre) is signalled with a long bleep from the sounder.

### Learn Mode (S3-C)

Fido has been programed with a default value of stride constant (2280 strides/mile, level ground, walking), but it will probably be necessary to readjust this constant. To make the adjustment, Learn mode needs to be selected by setting the Mode switch to position S3-C.

A distance of one mile, or one kilometre, should now be walked or run. The display will show the normal "descending bars" indicating a valid stride, but this will be accompanied by a bleep and the letter L on the display.

To avoid the accidental selection of Learn mode (and hence entering incorrect data), Fido will only commence remembering the stride count after 255 strides have been completed. When more than 255 strides have been recorded, each stride will be followed by two bleeps to indicate that Fido is now recording a "live" stride constant value.

Once the standard distance has been covered, switch to normal walk mode (Measure – S3-B) and walk a few paces. Check the descending bars are visible again and no bleep is present. Switch Fido off, wait a couple of seconds to let capacitor C3 discharge, and then switch back on. Henceforth only the new stride constant will be used (until such time as you might choose to change it, in the same way as just described).

If possible, "train" Fido in the type of terrain in which it will be used. A "standard



mile" can be determined by driving a car down a safe road (i.e. also suitable for pedestrians) for one mile (or 0.62 miles for kilometres), as shown on the car's mileometer. Walk back to the start of the mile with Fido set to Learn mode. Save the new stride constant, restart Fido and then walk back to the car.

The display may show 0.9 miles when coincident with the position of the car. Walk until it shows 1.0 miles, which should be an indication of the error and should be no more than 10%, say 170 yards. Getting standard distances in rough country can be more difficult and perhaps Ordnance survey maps can be of assistance here.

Both a gym treadmill and the above procedure have been used for calibrating the prototype. Tests showed an accuracy to within 10% for distances greater than 1.0 miles.

The conversion between miles and kilometres is:

Miles to kilometres multiply by 1.609

Kilometres to miles multiply by 0.621

## FURTHER IDEAS


Fido can potentially record any repetitive leg movement providing the set-up and calibration are adjusted. Experiments are currently underway to adapt Fido to

measure the "stroke rate" and performance profile of club standard rowers.
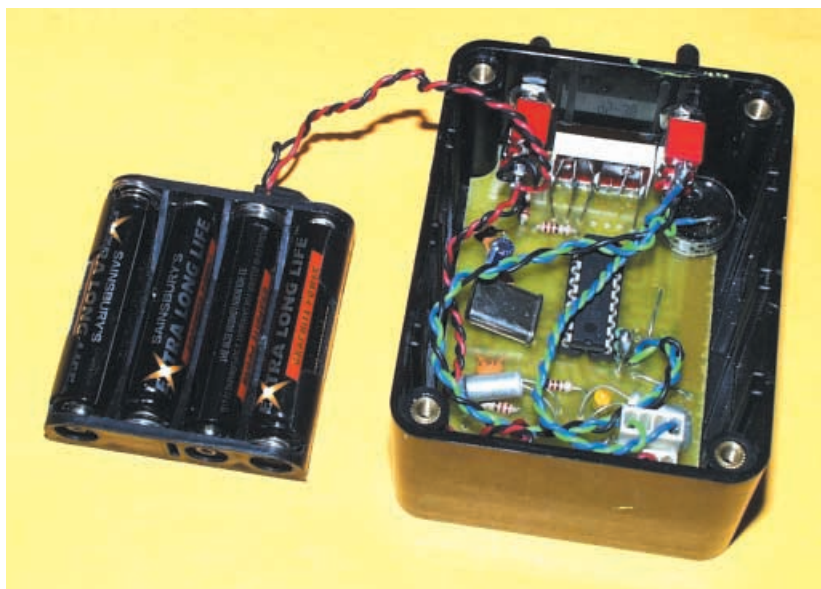
## FURTHER READING

Although this design is simply PIC-based, readers may be interested to read

about the ADXL202 accelerometer device, in particular *Using the ADXL202 in Pedometer Applications*, Harvey Weinberg, via [www.Parallex.com](http://www.Parallex.com). ADXL202 device information is available from [www.Analog.com](http://www.Analog.com). □



# SHOP TALK

with David Barrington

## PICronos L.E.D. Wall Clock

The first observation one makes when scanning down the parts list for the *PICronos L.E.D. Wall Clock* is that quite a cash saving can be made if readers approach some of our components advertisers and do a bit of "arm-twisting" and negotiate a special "bulk discount" on the ultrabright l.e.d.s. If you order 200, as the author did, they should certainly be able to offer you a good price, and possibly include different colours as well.

It is important that constructors keep to the specified semiconductor devices for the Clock. The L293DN 16-pin Half-H driver chip (also referred to as a stepper motor driver i.c.) was purchased from **Rapid Electronics** (☎ 01206 751166 or [www.rapidelectronics.co.uk](http://www.rapidelectronics.co.uk)), code 82-0192. The "D" denotes it is a 16-pin device. Do not use other L293 device types as they may not have the same characteristics – for instance, the L293E has 20 pins and cannot be used. (Check out the Texas web site at: [www.ti.com](http://www.ti.com).)

The 7-stage Darlington line driver type ULN2004A was also ordered from the above company, code 82-0622. It is also listed by **RS Components** (☎ 01536 444079 or [rswww.com](http://rswww.com), credit card only – a p&p charge will be made), code 652-825. RS also supplied the rail-to-rail LMC6484 quad op.amp, code 310-925.

For those readers unable to program their own PICs, a ready-programmed PIC16F877-4 microcontroller can be purchased from **Magenta Electronics** (☎ 01283 565435 or [www.magenta2000.co.uk](http://www.magenta2000.co.uk)) for the inclusive price of £10 each (overseas add £1 p&p). The software is available on a 3.5in. PC-compatible disk (Disk 6) from the *EPE Editorial Office* for the sum of £3 each (UK), to cover admin costs (for overseas charges see page 434). It is also available for free download from the *EPE* ftp site, which is most easily accessed via the click-link option on the home page when you enter the main web site at [www.epemag.wimborne.co.uk](http://www.epemag.wimborne.co.uk). On entry to the ftp site take the path [pub/PICs/PICronos](ftp://pub/PICs/PICronos).

The large circular printed circuit board for the Clock is available from the *EPE PCB Service*, code 395 (see page 434).

## Fido Pedometer

Apart from the PIC microcontroller and associated software, only the tilt switches called for in the *Fido Pedometer* project are likely to cause any real concern.

Due to the robust treatment of Fido, when taken for "walkies", and the dangerous toxic nature of mercury, we feel readers should make every endeavour to keep well clear of using mercury-filled tilt switches. Instead, we recommend readers use one of the hermetically sealed non-mercury types. A suitable switch is "currently listed" by **Maplin** (☎ 0870 2263 6000 or [www.maplin.co.uk](http://www.maplin.co.uk)), code DP50E.

The above company also supplied the sub-miniature centre-off, biased one way, toggle switch (code FH02C) and a suitable waterproof toggle switch cover (two needed – code JR79L). The plastic box is left to individual choice.

For those readers unable to program their own PICs, a ready-programmed PIC16F84A microcontroller can be purchased from **Magenta Electronics** (☎ 01283 565435 or [www.magenta2000.co.uk](http://www.magenta2000.co.uk)) for the inclusive price of £5.90 each (overseas add £1 p&p). The software is available on a 3.5in. PC-compatible disk (Disk 6) from the *EPE Editorial Office* for the sum of £3 each (UK), to cover admin costs (for overseas charges see page 434). It is also available for free download from the *EPE* ftp site, which is most easily accessed via the click-link option on the home page when you enter the main web site at [www.epemag.wimborne.co.uk](http://www.epemag.wimborne.co.uk). On entry to the ftp site take the path [pub/PICs/FidoPed](ftp://pub/PICs/FidoPed).

The printed circuit board is available from the *EPE PCB Service*, code 394 (see page 434). The 7-segment common anode display should be in abundant supply, but you will need to check the pinout arrangement before making a purchase.

## Back-To-Basics 5 – Mini Theremin/Twilight Switch

The only item that readers will experience problems finding for the *Mini Theremin*, one of this month's *Back-To-Basics* projects, is the specified Toko RD7 i.f. transformer, which is usually used in radio receivers.

Having had problems in the recent past trying to locate sources for Toko coils, it is fortuitous that the author (Raymond Haigh) of the new *Practical Radio Circuits* series has given us the names of two stockists. They are: **JAB Electronic Components**, Dept EPE, PO Box 5774, Birmingham, B44 8JP (☎ 0121 682 7045 or [www.jabdog.com](http://www.jabdog.com) – they appear to only deal with mail orders) and **Sycom**, Dept EPE, PO Box 148, Leatherhead, Surrey, KT22 9YW (☎ 01372 372587 or [www.sycomcomp.co.uk](http://www.sycomcomp.co.uk)). We also understand from Raymond that the main UK Toko supplier is **Coils-UK** (☎ 01753 549502 or [www.coils-uk.com](http://www.coils-uk.com)), but that they are only into "bulk orders".

All the semiconductor devices for both of this month's projects should be widely stocked by our components advertisers. They should also carry the ORP12 light-dependent resistor or its derivative used in the concluding *Twilight Switch*.

## Practical Radio Circuits – 1

No difficulties should be encountered in obtaining components for the *Practical Radio Circuits* series of projects and any that could possibly cause concern will be highlighted each month.

We "kick-off" the series with a simple *Crystal Set Radio*, a *TRF Receiver* and a single transistor *Headphone Amplifier*. The *Crystal Set* and *TRF Receiver* both use the same polythene dielectric tuning capacitor and ferrite rod coil.

The tuning capacitor will normally be found listed as a miniature "transistor radio" type and is currently stocked by **ESR Components** (☎ 0191 251 4363 or [www.esr.co.uk](http://www.esr.co.uk)), code 896-110 and **Sherwood Electronics** (see ad. on page 440), code CT9. The ferrite rod for the aerial/tuning coil should be easy to come by, it is certainly listed by Sherwood (code FR1) and we note **WCN Supplies** (☎ 023 8066 0700) are offering a 140mm x 10mm rod, with a coil (unwanted).

For the 26s.w.g. enamelled copper wire, the author obtained a 50g (20z) reel from **JAB Electronic Components** (☎ 0121 682 7045 or [www.jabdog.com](http://www.jabdog.com)). We also understand **J. Birkett Supplies** (☎ 01522 520767) stock 50g reels. Most suppliers only sell "large" reels.

The MK484 radio i.c. is stocked by **ESR Components** (see above) and **Rapid Electronics** (☎ 01206 751166 or [www.rapidelectronics.co.uk](http://www.rapidelectronics.co.uk)), code 82-1026. Any point-contact germanium diode should prove suitable for the detector in the *Crystal Set*, e.g. the OA47, OA90 and OA91, and any silicon signal diode can be used for D1 and D2 in the *TRF Receiver*, e.g. 1N4148, 1N914, 1N916.

The two small printed circuit boards are obtainable from the *EPE PCB Service*, codes 392 (TRF Rec.) and 393 (Headphone), see page 434.


## PLEASE TAKE NOTE

### Toolkit TK3

(Oct/Nov '01)  
Version V1.42 of the TK3 programming software is now on our ftp site. It has had the following facilities added:

- Recognition of Macro functions
- Use of LOCAL in the context of Macro addresses in relation to HIGH and LOW functions
- Recognition of IFDEF and ENDIF functions
- Calculator for PIC Baud rate register values

# PIC Training & Development System

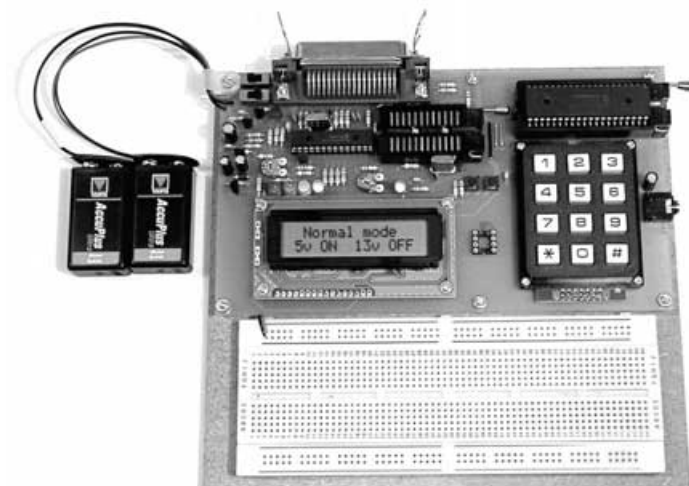

## Programming PICs the Easy Way

Programming PICs the Easy Way is the title of a new 208 page book by Peter Brunning which is now included in our PIC Training & Development System. This new book provides a very fast start for any newcomer to PIC programming who needs to rapidly get to the situation where he or she can write their own programmes. This book starts with four very simple experiments where the programmes are written out in full detail so that the basic programming concepts are understood. In the rest of the book each chapter sets a specific task which creates a real life PIC controlled circuit. The complexity of the programming for these projects is hidden away in ready made subroutines. So although the reader is working in PIC assembly language it is used as if it were a high level language. This has the great advantage of allowing a newcomer to create their own complex programmes in the shortest time with the minimum amount of typing, while retaining all the advantages of working in PIC assembly language.

Projects:- Traffic Lights Controller, Simple Text Messages, Using the Keypad, Creating a Siren Sound, Realistic Dice Machine, Freezer Thaw Warning Device, Voltage Measurement and Temperature Measurement.

For readers with very little electronics experience appendix E introduces resistors, capacitors, diodes, transistors, MOSFETs and logic circuits.

The software suite has been updated to include the library routines and a system which allows break points to be placed in the programme in the actual PIC so that hardware problems can be more easily located.

Our PIC training and development system now consists of our universal mid range PIC programmer, a 208 page easy programming book, a 306 page book covering the PIC16F84, a 262 page book introducing the PIC16F877 family, and a suite of programmes to run on a PC. Two ZIF sockets and an 8 pin socket allow most mid range 8, 18, 28 and 40 pin PICs to be programmed. The plugboard is wired with a 5 volt supply. The software is an integrated system comprising a text editor, assembler disassembler, simulator and programming software. The programming is performed at normal 5 volts and then verified with plus and minus 10% applied to ensure that the device is programmed with a good margin and not poised on the edge of failure. The DC version requires a 15 to 20 volt supply with a 2.1mm plug which is not included (UK plugtop supply £8.95). The battery version requires two PP3 batteries which are not included.

### Order Code P404:-

- Universal mid range PIC programmer module
- + Book Programming PICs the Easy Way
- + Book Experimenting with PIC Microcontrollers
- + Book Experimenting with the PIC16F877 (2nd edition)
- + Universal mid range PIC software suite
- + PIC16F84, 16F628 and 16F872 test PICs .....£179.91
- UK Postage (2 day) and insurance .....£ 9.00
- (Europe postage & Insurance ... £16.50. Rest of world . £32.50)

### Order Code P405:-

- Universal mid range PIC programmer module
- + Book Programming PICs the Easy Way
- + Universal mid range PIC software suite
- + PIC16F628 and PIC16F872 test PICs .....£129.91
- UK Postage and insurance .....£ 7.50

## Experimenting with PIC Micros

This book introduces the PIC16F84 and PIC16C711. We begin with four simple experiments, which are the same as in the easy programming book but this time using the PIC16F84. Then we study the basic principles of PIC programming, learn about the 8 bit timer, how to drive the liquid crystal display, create a real time clock, experiment with the watchdog timer, sleep mode, beeps and music, including a rendition of Beethoven's *Für Elise*. Finally there are two projects to work through, using the PIC16F84 to create a sinewave generator and investigating the power taken by domestic appliances. In the space of 24 experiments, two projects and 56 exercises the book works through from absolute beginner to experienced engineer level.

The best way to get the PIC programming language into your memory is to laboriously type every programme out in full so there are no short cuts in this book. However, we do understand that problems crop up where a typing error causes too much heart ache. If you do get stuck visit our web site, follow the instructions and we will email you the correct text.

## Ordering Information


Telephone with Visa, Mastercard or Switch, or send cheque/PO to have your order immediately processed. Despatch is usually within 2 days of order being received unless we are out of stock. All prices include VAT if applicable. Postage must be added to all orders. Please state DC or battery version. If not stated battery version will be assumed.

## Hardware required

Our PIC Training and Development System uses DOS based software which will run on any modern PC with a 386 processor or better. It is optimised for use with Windows 98. For other Windows systems the software should be run directly from DOS. Our website contains full information about Windows XP which also applies in general terms to Windows 2000 and Windows NT.

Please visit our website for full information:-

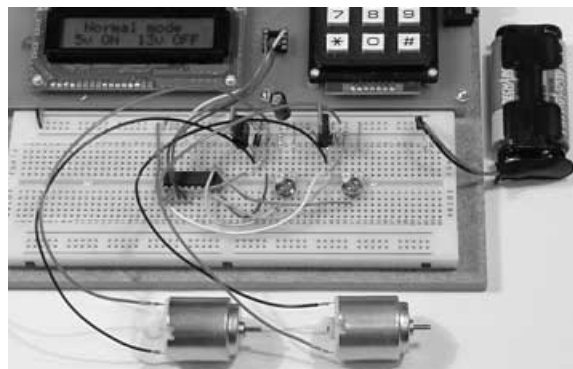**[www.brunningsoftware.co.uk](http://www.brunningsoftware.co.uk)**



## Experimenting with the PIC16F877

This book starts with the simplest of experiments to give us a basic understanding of the PIC16F877 family. Then we look at the 16 bit timer, efficient storage and display of text messages, simple frequency counter, use a keypad for numbers, letters and security codes, and examine the 10 bit A/D converter.

The 2nd edition has two new chapters. The PIC16F627 is introduced as a low cost PIC16F84. We use the PIC16F627 as a step up switching regulator, and to control the speed of a DC motor with maximum torque still available. Then we study how to use a PIC to switch mains power using an optoisolated triac driving a high current triac.

Mail order address:

**Brunning Software** 138 The Street, Little Clacton, Clacton-on-sea,  
Essex, CO16 9LS. Tel 01255 862308



## Powerline Comms – Boon or Bogey?

Broadband delivered over mains wiring? Andy Emmerson investigates

**I**F you thought PLC stands for public limited company, you'd be right. But to some it means power line communications as well, also known as PLT (power line telecommunications). Although some electricity companies see PLC as an ideal way of providing Internet service down your power feed (and making mega money at the same time), others consider the idea nothing short of abominable. So what's all the fuss about?

The notion is very simple. The copper cables that supply mains electricity to your home could deliver bandwidth by the bucketload as well to provide low cost broadband connections for Internetters frustrated by its lacking availability in their neck of the woods. With governments banging the broadband drum and users yearning for low-cost bandwidth, it's hardly surprising that power companies scent money in this opportunity.

Hardware vendors are equally keen to assist the electricity industry apply leverage to its existing assets and proclaim the effectiveness of their solutions most eloquently. The technology is cost-effective, it needs no new wires and everyone wants it. Or so you might believe.

### WHAT IS PLC?

Communicating over electricity mains uses the existing supply (110V, 230V, etc.) wiring to carry information as well as energy. This concept can be applied to local area networking (using internal wiring within the home or workplace) or for access to the public network (over the feeders that connect consumers' premises to the local substation).

As a commercial proposition, it is the latter opportunity that is exercising the minds of the power companies. With the delays and uncertainties of unbundling the European and US local loops and the stagnation surrounding broadband fixed wireless access, powerline technology is attracting considerable attention as a local access technology.

Before detailing the underlying technology, first we need to see what's fuelling this feeding frenzy. Power generation and distribution is a highly competitive business and utilities would dearly like to tap into new revenue streams.

A key imponderable remains, however, and it could prove a major stumbling block. The issue is electromagnetic compatibility (EMC); power lines carrying data signals are likely to radiate, interfering with broadcast signals. Bean counters make little of the issue and vendors argue that interference problems can be overcome. Others are less confident and are putting their faith in existing regulations against undesirable transmissions.

Debate has been mainly theoretical but with tests underway now, many bodies will be observing the results. If these are successful and interference can be contained, major deployment of the technology is forecast to follow.

### WHAT'S ON OFFER

Commercial applications for powerline communication include high-speed Internet access, entertainment distribution, voice telephony and fax using Voice over Internet Protocol (VoIP), building automation, meter reading and remote surveillance for building security and healthcare.

Data rates are not spectacular, however. Although products available currently work at up to 2Mbit/s, once several users are sharing the same data stream these speeds will drop significantly. Higher speeds are promised in future, though, and the vendor that spoke of individual network connections of 2.5Gbit/s has still not provided substantiation of this claim after 18 months.

A data concentrator installed at the neighbourhood substation is the transfer point for data streams between the local supply mains and the main telecommunications trunk network. The mains-voltage distribution network carries the data between here and consumers' homes or offices, where an adapter breaks out the voice and data signals and feeds them by coaxial cable to the user's PC, telephone and other applications. In general the maximum distance between transformer and consumer is up to half a mile.

Carrier frequencies for transmitting this data lie in the region 9kHz to 30MHz, the same part of the spectrum as used for a variety of radio communications. Implementations use a variety of spread spectrum and fast frequency hopping techniques, with either frequency division or amplitude modulation.

Power lines are a harsh environment for data transmission; impulsive noise and voltage spikes from electrical appliances, switching operations and distant lightning strikes can wipe out low-level signals. Modulation levels can be increased but then signals begin to leak out; radiation from street lamps during trials in Manchester gave rise to concerns over data security as well as fuelling opposition to further pollution of the airwaves. Powerline communications are anathema to broadcasters and listeners, not to mention government, amateur and CB users of the radio spectrum.

But is it legal? Or better stated, does it matter? Legitimate users of the radio spectrum think so. Radio Netherlands has warned that interference levels, even to reception of strong domestic signals, will be so high that the whole concept will have

to be re-thought. Otherwise many urban dwellers will lose the opportunity to listen to foreign radio stations on AM radio.

The Radio Society of Great Britain has also voiced its concern, noting that German approval for powerline communication systems, strongly opposed by radio users in that country, allow higher levels of emission than those cited in the UK as a "worst case" for acceptable interference. It concludes there is a European agenda to provide cheap wideband data systems and that the technical arguments for preservation of the h.f. spectrum appear to be ignored.

However, given the recent success of legal appeals under human rights legislation, it is likely that any significant interference to citizens' ability to listen to authorised broadcast stations would be found unconstitutional and would lead to effective action against the "jammers".

Just think back to the early 1980s and the hijacking of the airwaves for citizens' band radio, the largest manifestation of mass lawbreaking the country has ever seen. Rather than prosecute the malefactors, the supine government of the day saw fit to legalise the use of the 27MHz band for CB use, forcing the existing users of the frequency to swallow the cost of buying new equipment on different frequencies. If the British government gives in that easily to individuals, how likely is it to resist private companies with vested interests?

### STILL INTERESTED?

Scottish Hydro-Electric is due to begin full-scale commercial trials this summer of its broadband service over power lines, naming Stonehaven in Scotland and "a town in Hampshire". Pricing for triallists is stated to be around £25-£30 a month, although this was not finalised at the time of writing.

Don't hold your breath for powerline communications to reach your home by the end of the year though; the company may have legal action on its hands if the system causes interference. It cannot be forgotten either that high-profile trials in Britain and Germany by suppliers such as Nortel/Norweb, Siemens and Rhine-Westphalian Electricity have failed on account of regulatory issues and slow sales.

The truth is that powerline communication faces an uncertain future. Superficially attractive, its deployment may turn out to be unviable and technically problematic. A report from UBS Warburg and the Smith Group argues that it will come so late that it will "miss the boat" and by the time manufacturers have equipment that meets EMC regulations, the rollout of ADSL will be at an advanced stage. This may be unduly optimistic for ADSL but only time can tell.

## **June 2003 – Special PIC Supplement**

This special 16-page supplement is available for free download from the EPE Online website.

All you have to do is bounce over to [www.epemag.com](http://www.epemag.com) and click on the “Library” link in the main navigation.



### FOUNDER OF TI DIES

**T**HE British-born founder of Texas Instruments, Sir Cecil Green, died on 11 April 2003 aged 102 in a hospital at La Jolla, California. He had pneumonia.

He was the last of the four founders and a philanthropist who donated more than \$200 million to education and medical institutions around the world.

On 6 Dec 1941 he joined Eugene McDermott, J. Erik Jonsson and H. Bates Peacock to purchase Dallas-based Geophysical Service Inc., which performed seismic explorations for petroleum. During WW2, GSI branched into other areas, including the manufacture of submarine-detection devices and airborne radar systems.

In 1951 the company changed its name to Texas Instruments. In 1952 TI entered the semiconductor business by licensing Shockley's work at Bell Labs, putting it at the front of the chip business. Green discovered that foreign competitors were far smarter at adopting TI's innovations than US competitors. He is quoted as having said "Our aggressiveness, in effect, set the Japanese up in business".

Cecil Howard Green was born near Manchester, England, emigrated as a child to Canada, then San Francisco. He was awarded an honorary knighthood in 1991. He leaves no immediate survivors.

For more information browse [www.theregister.co.uk/content/3/30282.html](http://www.theregister.co.uk/content/3/30282.html) and [www.washingtonpost.com/wp-dyn/articles/A1993-2003Apr13.html](http://www.washingtonpost.com/wp-dyn/articles/A1993-2003Apr13.html).

### RACE FOR EPSOM

SUNDAY 22 June 2003 is the starting date-line for the Radio and Electronics Fair to be held at Epsom Grandstand, Surrey, from 10am to 5pm. After the success of the last rally in 2002, the organisers have been encouraged to stage another. The Fair has become the number one event for the region.

It is a one day event and will consist of private and trade stalls with added attractions throughout the day, amongst which will be a Bring and Buy sale. Also, on behalf of the RSGB, a National Construction Contest will be held, with a trophy. Morse testing facilities will be available as well. There will also be a display of military vehicles by VMARS (Vintage and Amateur Radio Society), plus a WW2 operations room talking station!

Refreshments are available, and further entertainment will be provided by Ken Mackintosh and his 17-member band.

Booking contact: Brian Cannon G8DIU, 38 Sandringham Road, Worcester Park, Surrey KT4 8UJ. Tel/fax 01737 279108. Email: [Brian.Cannon@btinternet.com](mailto:Brian.Cannon@btinternet.com).

### PICO CAT

AS you are no doubt aware, Pico specialises in the field of virtual instruments for data acquisition. They say that they have always been recognised for providing innovative low-cost alternatives to traditional test equipment and data acquisition products.

For many years Pico have generously supported *EPE*'s innovative readers by awarding prizes to the best *Ingenuity Unlimited* designs each year. They also supported our recent *Teach-In 2002* series. Teachers will be interested to know that Pico place a heavy emphasis on scopes and loggers for Education.

We thoroughly recommend that you get a copy of Pico's latest catalogue – over 40 pages of full-colour glossy A4 – detailing their entire range of products and accessories.

For further information contact Pico Technology Ltd., Dept. EPE, The Mill House, Cambridge Street, St Neots, Cambs PE19 1QB. Tel: 01480 396395. Fax: 01480 396296. Email: [sales@picotech.com](mailto:sales@picotech.com). Web: [www.picotech.com](http://www.picotech.com).

### WCN BARGAINS

"100's of bargains inside" proclaims WCN Supplies' latest catalogue, issue 17. In its 44 A4-sized pages there is a vast array of products on offer, ranging from batteries, connectors and fans, through buggies and paintball (yes indeed!), passive and active electronic components, to meters and tools.

To get your copy of this catalogue, contact WCN Supplies, Dept EPE, The Old Grain Store, Rear of 62 Rumbidge Street, Totton, Southampton SO40 9DS.

Tel/Fax: 023 8066 0700.

Email: [info@wcnsupplies.fsnet.co.uk](mailto:info@wcnsupplies.fsnet.co.uk).

Web: [www.wcnsupplies.com](http://www.wcnsupplies.com).

### Controlling Magic

Barry Fox

MODERN TV, recorder and satellite set top boxes are routinely updated with new operating software sent over the air or by phone line in the small hours without the owner knowing it. New features appear in the morning as if by magic. But the remote control often cannot control them.

Thomson (owner of RCA) has the answer. Thomson will now provide remotes that have an infra-red sensor eye as well as the usual IR transmitter; and the set-top box will have an infra-red transmitter as well as the usual sensor. After the set top box has been updated, instructions appear on screen telling the owner to point the remote at the box and wait a few seconds while it loads new control codes into its memory. The remote then matches the set-top box again.

### EPE Benefits EOCS

DON Bray, Hon Editor of the Electronics Organ Constructors Society has written to thank us for Editorial mention. We are indeed pleased to help publicise the EOCS, and have been doing so from time to time for many years.

He says that the EOCS has acquired several new members recently and at least one joined as result of our last mention. He also says that the EOCS magazine shows that there is a considerable interest in PIC programming, which of course we know full well!

For more information about the EOCS, contact Trevor Hawkins, Hon Secretary, EOCS, 23 Blenheim Road, St Albans, Herts AL1 4NS. Tel: 01727 857344.

### DATA LOGGING METER

WAVETEK Meterman Test Tools latest DMM 38XR range offers optional real-time data logging by PC. The 38XR is a true r.m.s. meter which measures volts, amps and ohms, as well as temperature, capacitance, frequency and 4-20mA loop current percentage.

The clear 10,000 count display with 0.25% accuracy includes an analogue bargraph. Features include buttons for Min/Max/Avg, Data Hold, Peak Hold and Relative functions, as well as a neon backlight for use in dim environments.

The meter can be used for data acquisition using any standard PC running Windows. The software stores data for retrieval and further analysis, including interfacing with Excel.

The Meterman 38XR is offered at a suggested retail price of £99.

For more information browse [www.metermantesttools.com](http://www.metermantesttools.com) or email [info@metermantesttools.com](mailto:info@metermantesttools.com).



# PRACTICAL RADIO CIRCUITS

RAYMOND HAIGH



## Part 1: Introduction, Simple Receivers and a Headphone Amp.

*Dispelling the mysteries of radio. This new series features a variety of practical circuits for the set builder and experimenter.*

**T**owards the end of the 19th century, sending a radio signal a few hundred yards was considered a major achievement. At the close of the 20th, man was communicating with space probes at the outermost edge of the solar system.

No other area of science and technology has affected the lives of people more completely. And because it is so commonplace and affordable, it is accepted without a second thought. The millions who enjoy it, use it, even those whose lives depend upon it, often have little more than a vague notion of how it works.

This series of articles will view the technology in a historical perspective and try to dispel its mysteries. The main purpose, however, is to present a variety of practical circuits for set builders and experimenters. And, with economy in mind, basic components and assemblies are repeated in different receivers.

### MAKING WAVES

Radio uses electromagnetic waves to transport speech, music and data over vast distances at the speed of light.

The electromagnetic waves are generated by making an electric current oscillate at frequencies ranging from 10kHz (ten thousand Hertz) to more than 100GHz (one-hundred thousand million Hertz).

The lowest frequencies are used for submarine communications because of their ability to penetrate water to a considerable depth: the highest mainly for satellite communications. Most radio listeners are served by the portion of the spectrum extending from 150kHz to 110MHz.

Frequency of oscillation is measured in Hertz in honour of Heinrich Rudolf Hertz, the

physicist who first demonstrated the existence of electromagnetic waves in 1886.

Before the valve era, radio frequency oscillations were generated by using an electrical discharge to shock-excite a tuned circuit (H. Hertz and G. Marconi), by the negative resistance of an electric arc

(V. Poulsen), and by mechanical alternators (E. Alexanderson). Semiconductors now play an increasing role, but valves are still used in high-power transmitters.

As their name suggests, the waves comprise an electric and a magnetic field which are aligned at right angles to one another. The electric field is formed by the rapid voltage fluctuations (oscillations) in the aerial. Current fluctuations create the magnetic field.

### HITCHING A RIDE

Electromagnetic waves cannot, by themselves, convey any information. They are essentially **radio frequency carriers**, and arrangements have to be made for the audio frequency speech and music signals to hitch a ride. This is done by modulating the radio frequency carrier with the audio frequency signals.

If the amplitude of the carrier is varied in sympathy with the signal, the process is known as **amplitude modulation** (a.m.), and typical waveforms are depicted in Fig.1.1. Varying the carrier frequency is, of course, known as **frequency modulation** (f.m.).

Marconi's Morse signals were transmitted by simply switching the carrier on and off. It was R. A. Fessenden who, in 1906, used a carbon microphone (said to be water cooled) to directly modulate the radio frequency (50kHz) output of an alternator and be the first to transmit speech and music.

### PROPAGATION

The oscillations produced by the transmitter are fed to an aerial system in order to radiate the electromagnetic energy. The lower the frequency the longer the wavelength and the bigger the aerial.

Aerial designs vary, but the dipole adopted by Hertz in 1886 is still deployed at high, very high

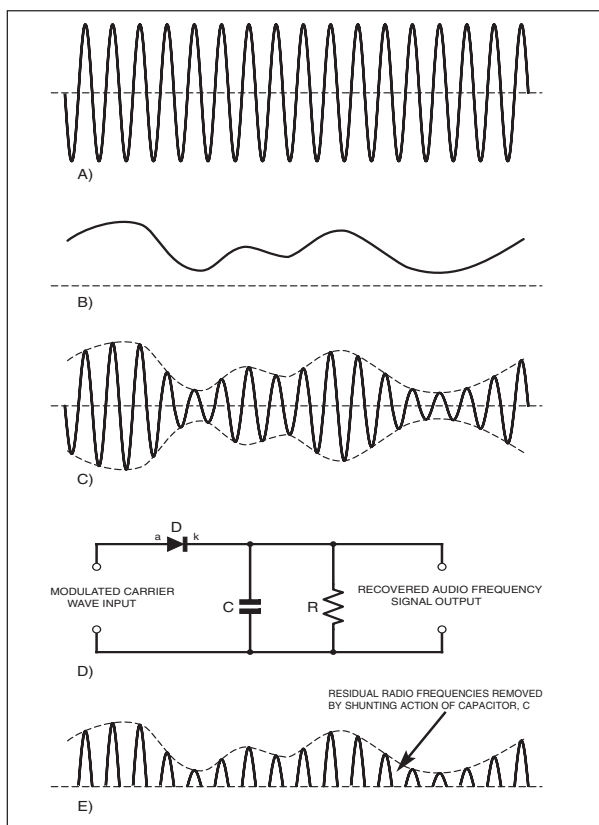


Fig.1.1. Modulation and detection: (A) Radio frequency carrier wave. (B) Audio frequency signal. (C) Carrier wave modulated by audio signal. Average value of imposed audio signal voltage is zero. (D) Diode detector, D, working into load resistor, R, rectifies the modulated carrier wave. Reservoir capacitor, C, removes residual radio frequencies and enables the audio frequency output voltage to approach its peak value. (E) Recovered audio frequency signal.

and ultra high frequencies. The elevated wire and earth arrangement used by Marconi in the 1890's is still used for the radiation of low and medium frequencies.

Transmitter powers range from the miserly one or two watts, radiated by amateurs who specialize in low power communication, to the two-million watts output from some medium wave broadcast transmitters.

Radiation from the transmitter reaches the receiver by either the ground wave (line of sight or diffraction around the earth's curvature), or the sky wave (reflected between the ionosphere and the surface of the earth. Propagation path is frequency dependant: by ground wave up to 500kHz, then gradually shifting to sky wave until, above 30MHz, the waves are no longer reflected back by the ionosphere and escape out into space.

Solar radiation has a profound effect on the charged particles which make up the ionosphere, and propagation conditions vary between night and day, seasonally, and according to the eleven-year sunspot cycle.

## RECEPTION

Reception involves three essential functions: picking up the energy radiated by transmitters, selecting one station from all the rest, and extracting the modulation from the carrier wave in order to make the transmitted speech or music audible to the listener.

### Signal Pick Up

Receiving aerials respond to either the electric or the magnetic field radiated by the transmitter. Sets that use telescopic rod or wire aerials pick up the electric field. Receivers that have loop aerials, i.e., a coil wound on a frame or a ferrite rod, respond to the magnetic field.

Portable receivers usually incorporate both: long and medium waves (150kHz to 1.6MHz) are covered by a loop with a ferrite rod core, and the v.h.f. f.m. band (88MHz to 108MHz) and short-wave bands by a telescopic aerial.

### Station Selection

In order to select one station from the thousands that are spread across the radio frequency spectrum, the receiver has to be tuned to the carrier frequency of the transmitter.

Sir Oliver Lodge was stressing the importance of tuning, a condition he called "syntony", as early as 1889, and he patented his system in 1897. This is one of the most fundamental patents in radio, and his method is still universally adopted.

Lodge's invention exploits the way an inductor (coil) and capacitor combination resonate at a particular frequency. If the capacitor is connected in parallel with the inductor (see Fig.1.2a) the circuit presents a high impedance at its resonant frequency and a lower impedance at all others.

Connecting the capacitor in series with the inductor (Fig.1.2b) results in a low impedance at resonance and a higher impedance at other frequencies. If the inductor or the capacitor (usually the capacitor) is made variable, it is possible to tune the circuit across a range of frequencies.

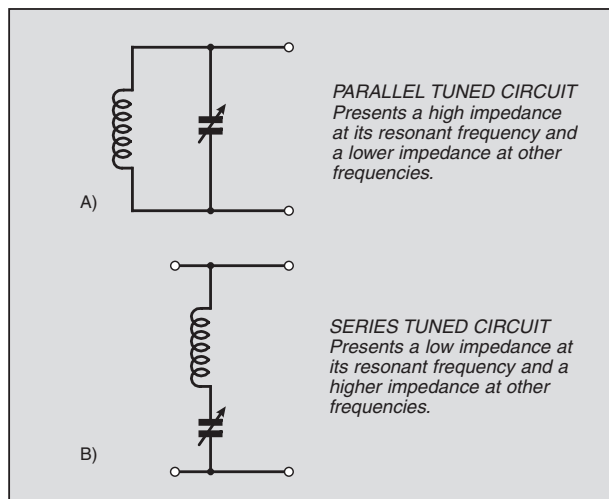


Fig.1.2. Basic tuned circuits. Combining an inductor (coil) and a capacitor produces a circuit which resonates at one particular frequency. The resonant frequency can be varied by changing the amount of inductance or capacitance (usually the latter). The tuning of all radio receivers and transmitters depends upon this phenomenon.

## IMPORTANT EVENTS

**1831**

In published papers and a letter deposited with the Royal Society (opened in 1937), Michael Faraday tentatively proposes electromagnetic wave theory.

**1864**

James Clerk Maxwell's mathematical analysis of Faraday's work published in his paper: *A Dynamical Theory of the Electro-magnetic Field*.

**1888**

Heinrich Rudolf Hertz uses a crude spark transmitter and receiver to demonstrate the existence of electromagnetic waves.

**1889**

Sir Oliver Lodge lectures on the need to tune the transmitter to receiver, a condition he called "syntony".

**1893**

Sir Oliver Lodge uses an invention of Edouard Branley's as a sensitive detector of electromagnetic waves. (The coherer).

**1901**

Guglielmo Marconi transmits radio signals across the Atlantic.

**1904**

Sir John Ambrose Fleming patents the diode valve.

**1906**

Dr Reginald Fessenden modulates a carrier wave and broadcasts speech and music. Dr Lee de Forest makes a patent application for his triode valve, the first electronic amplifying device.

**1913**

Major Edwin Howard Armstrong invents the regenerative receiver.

**1918**

Armstrong invents the superheterodyne receiver.

**1921**

Armstrong invents the super regenerative receiver and W. G. Cady uses quartz crystals to stabilize oscillators.

**1933**

Armstrong demonstrates his system of frequency modulated radio transmission.

**1947**

John Bardeen, Walter Brattain and Dr William Shockley develop the transistor at the Bell Telephone Laboratories.

Sharpness of tuning depends mainly on resistive and other losses in the inductor or coil: the lower these losses the sharper the tuning. Resistive and dielectric losses in the capacitor also affect performance, but, with modern tuning components, these are usually so small they can be ignored.

The ability of the coil to resonate sharply, i.e., be more selective, is known as its "Q" factor: the sharper the resonance the higher the Q.

Resonant tuned circuits magnify signal voltages, a phenomenon that is crucial to radio reception. If a signal of the same frequency as the resonant frequency of the tuned circuit is applied to the coil/capacitor combination, its voltage will be increased in proportion to the Q of the coil. With a Q of 100, a 1mV signal will be magnified to 100mV or 0.1V. We will be returning to this later.

## Demodulation

With amplitude modulated signals (a.m.) the process of recovering the modulation is essentially one of rectification. In Fig.1.1d, diode, D, rectifies the incoming radio frequency carrier wave and capacitor, C, shunts residual radio frequencies to ground (earth) leaving only the audio frequency modulation. Capacitor, C, also exhibits a reservoir action enabling the audio frequency voltage to approach its peak value.

The diode and, indeed, any other a.m. demodulator, is called a *detector*, a hang-over from the earliest days of radio when glass tubes filled with metal filings were used to simply detect the presence of electromagnetic waves.

In 1889, whilst working on the protection of telegraph equipment from lightning, Sir Oliver Lodge noticed that metal surfaces, separated by a minute air gap, would fuse when an electrical discharge occurred close by. He used the phenomenon to detect electromagnetic waves, and called devices of this kind *coherers*.

About this time, Edouard Branley discovered that a spark in the vicinity of a mass of metal particles lowered their resistance. Lodge found this arrangement to be more sensitive and, in 1893, adapted it for use as a detector.

Subsequently, J. A. Fleming's diode valve, patented in 1904, and crude semiconductor devices, were used as rectifiers in order to demodulate signals.



# CRYSTAL SET RADIO

A modern-day "museum piece" receiver

## THE CAT'S WHISKER

The most popular of the semiconductor detectors was the "crystal" or "cat's whisker" which consisted of a short length of springy brass wire touching a crystal of galena (lead sulphide). Adjustment of the point of contact was critical, but these crystal detectors could be more sensitive than Fleming's diode valve. They were much less expensive.

The modern equivalent of the crystal detector is the point contact germanium diode. Here, a gold-plated wire contacts a wafer of germanium, the assembly being enclosed within a glass tube. These diodes are still used to demodulate the signals in most domestic a.m. radios.

## CRYSTAL SET

The simplest receiver, known as a *Crystal Set*, consists of nothing more than a coil, tuning capacitor, diode detector, and a pair of earphones.

A typical circuit diagram for a Crystal Set Radio is given in Fig.1.3, where inductor or coil L1 is tuned by variable capacitor VC1 to the transmitter frequency. Diode D1 demodulates the signal, which is fed straight to the earphones. There is no amplification.


A long (at least 20 metres), high (7 metres or more) aerial and a good earth (a buried biscuit tin or a metre of copper pipe driven into damp ground) are required in order to ensure audible headphone reception. The earphones originally used with these receivers had an impedance of around 4000 ohms and were very sensitive (and heavy and uncomfortable). They are no longer available, but a crystal earpiece, which relies on the piezoelectric effect, will give acceptable results. Low impedance "Walkman" type earphones are *NOT* suitable.

## DRAWBACKS

Quite apart from the absence of amplification, two factors seriously limit the performance of crystal receivers.

Germanium diodes become increasingly reluctant to conduct as the applied voltage falls below 0.2V, and this makes the receiver insensitive to weak signals. Silicon diodes have a threshold of around 0.6V, and are, therefore, unsuitable for circuits of this kind.

The earphone loading imposes heavy damping on the tuned circuit, reducing its  $Q$  and, hence, its selectivity, i.e. its ability to separate signals. With such low selectivity insensitivity can be a blessing, and crystal sets are normally only capable of receiving a single, strong transmission on the long and medium wavebands. (They will sometimes receive more than one if a shortwave coil is fitted).

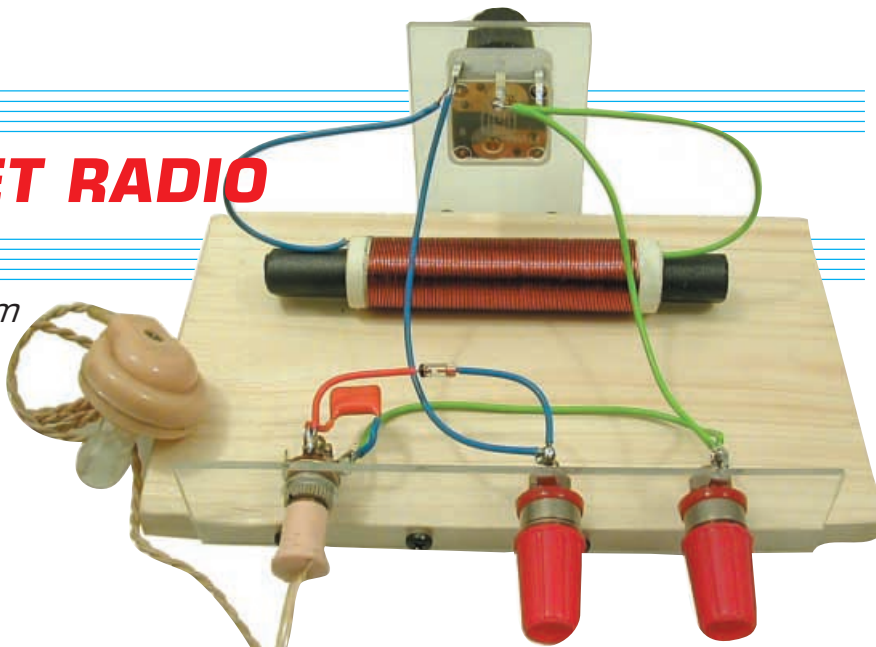

The author's Crystal Set "knock-up" on a wooden baseboard. This uses two screw terminals for the Aerial and Earth wire connections instead of croc. clips.

The aerial and diode can be connected toappings on the tuning coil in order to reduce damping, but the improvement in selectivity is usually at the expense of audio output.

When valves cost a week's wages and had to be powered by large dry batteries and lead/acid accumulators, the construction of simple receivers of this kind could be justified. With high performance transistors now costing only a few pence or cents, crystal sets are now regarded as "nostalgic pieces".

Some readers may, however, wish to build one out of curiosity, or for the novelty of having a receiver that does not require a power supply. Moreover, the components required are all used in more complex receivers to be described later.

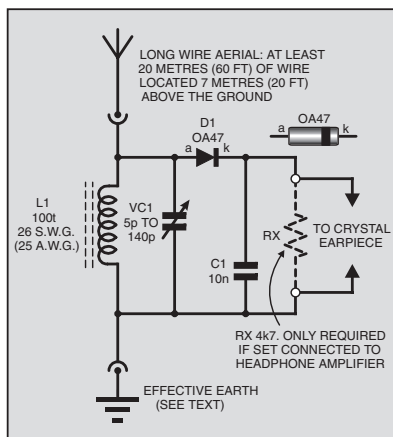


Fig.1.3. This simplest of radio receivers uses a germanium diode as the "cat's whisker" crystal detector.

## CIRCUIT DETAILS

Ferrite loop aerial L1 and polythene dielectric variable capacitor VC1 form the tuned circuit. Point contact germanium diode D1 demodulates the signal; capacitor C1 bypasses residual r.f. (radio frequencies) to earth and also exhibits a reservoir action, enabling the a.f. (audio frequency) output to approach its peak value. The

recovered audio signal is fed directly to a crystal earpiece.

Signal voltages induced in the ferrite loop aerial by the radiated magnetic field are much too weak to produce an output from the detector, and the component is used here simply as a tuning coil. The ferrite core does, however, reduce the number of turns required for the coil winding, thereby reducing its resistance and increasing its  $Q$  factor.

## COMPONENTS

### CRYSTAL SET

#### Resistor

RX 4k7 0.25W 5% (only required if set is connected to amplifier)

#### Capacitors

C1 10n disc ceramic.  
VC1 5p to 140p (minimum) polythene dielectric variable capacitor (see text)

#### Semiconductors

D1 0A47 germanium diode

#### Miscellaneous

L1 ferrite rod, 100mm (4in.) × 9mm/10mm (3/8in.) dia., with coil (see text)

Crystal earpiece and jack socket to suit.; plastic control knob; plastic insulated flexible cable for aerial wire, downlead and earth connection, 30 metres (100 ft) minimum; buried biscuit tin or 1 metre (3ft) of copper pipe for earth system; 50gm (2oz) reel of 26s.w.g. (25a.w.g.) enamelled copper wire, for tuning coil; card and glue for coil former; multistrand connecting wire; crocodile clips or terminals (2 off), for aerial and earth lead connection; solder etc.

Approx. Cost  
Guidance Only

£4

excl. earpiece & wire

## CONSTRUCTION

The circuit is simple enough to be assembled on the work bench, and a printed circuit board layout is not given. The components and the various interwiring connections are illustrated in Fig.1.4.

## COIL DETAILS

Full construction and winding details for the ferrite tuning/aerial coil L1 are shown in Fig.1.5. The coil is made from 26s.w.g. (25a.w.g.) enamelled copper wire, close wound on a cardboard former. This same ferrite tuning coil forms the loop aerial in the following TRF Receiver.

The r.f. bypass capacitor C1 can, in practice, be omitted with no noticeable reduction

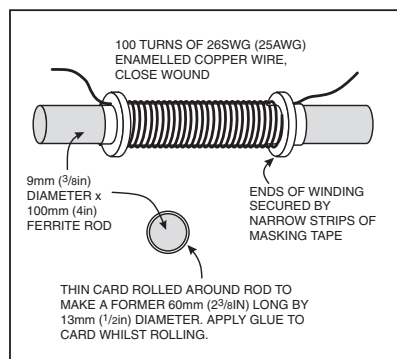


Fig.1.5. Construction and winding details for the ferrite rod tuning/aerial coil L1. This loop aerial is also used in the TRF Receiver.

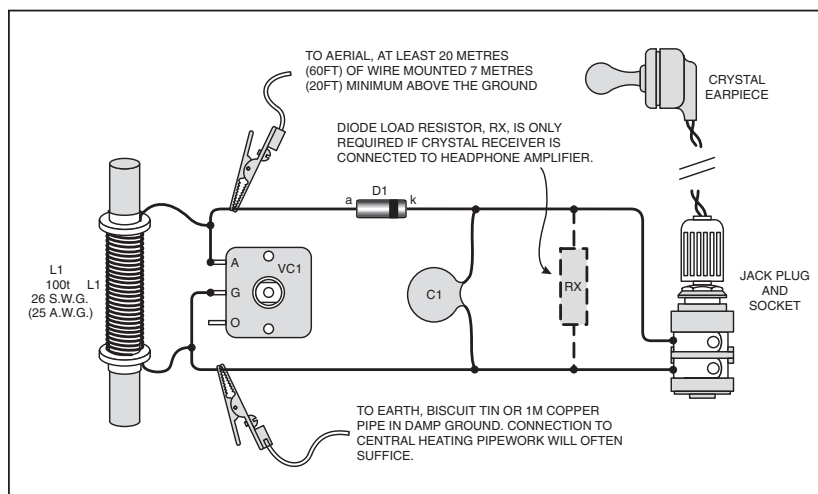


Fig.1.4. The components and various interwiring connections for the simple crystal set. This circuit is easily "lashed-up" on the workbench and no circuit board layout is given. The author's demonstration set is shown in the heading photograph.

in performance. However, if the set is to be connected to either the headphone amplifier (Fig.1.10) or speaker amplifier described next month, this component, together with diode load resistor, RX, must be included.

## AMPLIFICATION

Audio frequency amplification *after* the diode detector will permit the use of low impedance Walkman type earphones or even loudspeaker operation. It will do

nothing, however, to overcome the diode's insensitivity to weak signals. For this we must have radio frequency amplification of the signals picked up by the aerial *before* they reach the detector. (The standard circuit for a transistor portable receiver has three stages of radio frequency amplification ahead of the diode).

# MK484 TRF RECEIVER

Uses a single i.c. radio chip and a transistor

## TRF RECEIVER

Receivers with tuned circuits and amplification, at signal frequency, ahead of the detector stage were known, during the valve era, as tuned radio frequency, or t.r.f., receivers.

This arrangement was adopted by Ferranti when they designed their popular ZN414 radio i.c. Introduced in 1972, the chip relied upon a then new manufacturing technique developed by Bell Laboratories and known as collector diffusion isolation.

No bigger than a single transistor, and requiring a power supply of only 1.5V, the device enabled truly miniature receivers to be built, one of which was featured on the BBC TV science programme, *Tomorrow's World*. The chip is still produced, but in a plastic package instead of the original metal case and with the type number **MK484**.

## INTERNAL ARRANGEMENT

The chip's internal architecture, in block form, is depicted in Fig.1.6. The very high impedance input stage minimizes damping on the tuned circuit, enabling it to maintain a high *Q* factor and, consequently, reasonable selectivity. This is followed by three stages of radio frequency amplification ahead of a two transistor detector or demodulator.

Chip characteristics and pinout details are also listed with the block diagram Fig.1.6. Internal capacitors impose the low frequency operating limit, and the performance of the transistors determines the tail-off at high frequencies.

### MK484 Specification . . .

Supply Voltage (via external load resistor)	1.1V to 1.8V
Current Drain (affected by signal level)	0.3mA to 0.5mA
Frequency range (peaks at 1MHz)	150kHz to 3MHz
Input Impedance	1.5 megohms
Output Impedance	500 ohms
Sensitivity	better than 100µV
Power Gain	70dB
Internal Component Count:	
	10 Transistors
	15 Resistors
	4 Capacitors

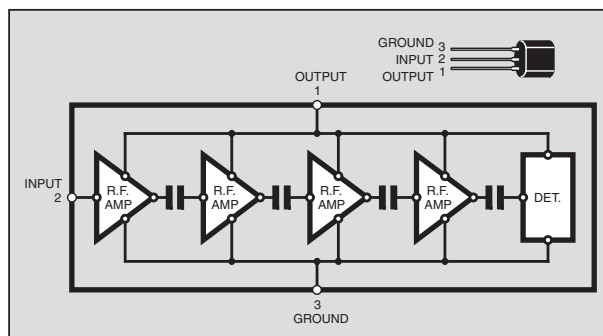


Fig.1.6. Block diagram showing the internal arrangement of the MK484 radio i.c.

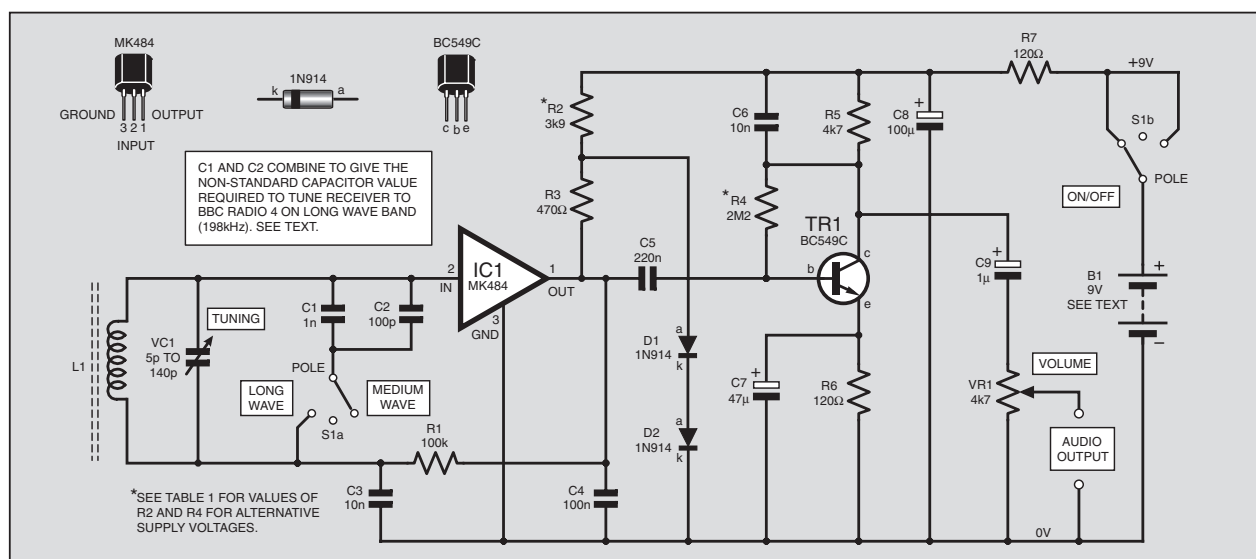


Fig.1.7. Complete circuit diagram for the MK484 TRF Receiver.

## TRF CIRCUIT

The circuit diagram for a simple TRF Receiver using the MK484 i.c. is given in Fig.1.7. Inductor or coil L1 is "tuned" by variable capacitor VC1, from roughly 550kHz to 1.7MHz, i.e., over the medium wave band.

Provision is made for toggle switch S1a to connect an additional capacitor across L1 to tune it to a lower frequency long wave station. For *BBC Radio 4* on 198kHz, a non-standard component is required, and this is made up from capacitors C1 and C2.

Tuning coil L1 is wound on a ferrite rod in order to form a loop aerial which, as we have seen, responds to the magnetic fields radiated by transmitters. The high permeability ferrite material concentrates the lines of magnetic force, and the signal developed across the coil is equal to that picked up by an air-cored loop of around 200mm (8in.) diameter. The threshold sensitivity of IC1 is better than 100μV, and this is sufficient for the reception of strong signals via the loop.

## SELECTIVITY

Current drawn by IC1 increases as signal strength increases, and the gain of the MK484 is supply voltage dependant. Connecting all of the stages to the supply via the audio load resistor R3 produces a measure of automatic gain control (a.g.c.). (Increased current demand at high signal levels increases the voltage drop across the load resistor thereby reducing the gain of the chip.) IC1 input pin 2 is biased via resistor R1, and r.f. bypass capacitors C3 and C4 ensure stability.

The value of the audio load resistor (sometimes called the a.g.c. resistor) R3 can range from 470 ohms to 1000 ohms. Selectivity is better when the value is kept low: gain is greater when the value is high. Most readers will need all the selectivity they can get and a 470 ohm resistor is used in this circuit.

Optimum supply voltage with a 470 ohm load is around 1.2V: more than this can cause instability problems, less will reduce gain. The voltage delivered by a fresh dry cell can be as high as 1.7V and the chain of silicon diodes, D1 and D2,

each of which begins to conduct at a 0.6V threshold, holds the supply at the correct potential.

Some readers will no doubt wish to use the circuit with different supply voltages, and the value of dropping resistor R2 should be altered to avoid excessive current drain. Table 1.1 gives suitable values for this resistor for various battery voltages.

## AUDIO OUTPUT

The output from IC1 pin1 is low, so the audio amplifier stage, TR1, is included to increase it to a useable level. The signal from IC1 pin 1 is applied to TR1 base (b) via d.c. blocking capacitor C5, and the output is developed across collector (c) load resistor R5.

Emitter (e) bias is provided by resistor R6 which is bypassed by capacitor C7. Base bias is derived via resistor R4. Connecting

Table 1.1: MK484 TRF Receiver  
(Values of resistors R2 and R4 for different supply voltages)

Voltage	R2	R4
1.5V	100Ω	180k
3V	1k	1M
4.5V	1k8	2M2
6V	2k2	2M2
9V	3k9	2M2

this resistor to the collector rather than the supply rail provides a measure of negative feedback, stabilizing the stage against temperature and transistor gain variations. The value of this resistor has to be optimized for different supply voltages, and appropriate values are given in Table 1.1.

## COMPONENTS

Approx. Cost  
Guidance Only  
excl. case, earpiece, wire & batt.

£10

### TRF RECEIVER

#### Resistors

R1	100k
R2	3k9 see Table 1.1
R3	470Ω
R4	2M2 see Table 1.1
R5	4k7
R6, R7	120Ω (2 off)

All 0.25W 5% carbon film

#### Potentiometers

VR1	4k7 rotary carbon, log.
-----	-------------------------

#### Capacitors

C1	1n polystyrene (see text)
C2	100p polystyrene or "low k" ceramic (see text)
C3, C6,	10n disc ceramic (2 off)
C4	100n disc ceramic
C5	220n disc ceramic
C7	47μ radial elect. 16V
C8	100μ radial elect. 16V
C9	1μ radial elect. 16V
VC1	5p to 140p (minimum) polythene dielectric variable capacitor

#### Semiconductors

D1, D2	1N914 silicon signal diodes (2 off)
TR1	BC549C <i>n</i> p <i>n</i> small signal transistor
IC1	MK484 radio i.c.

#### Miscellaneous

S1	d.p.d.t. centre-off toggle switch
L1	ferrite loop aerial: 100mm (4in.) × 9mm/10mm (3/8in.) dia. ferrite rod with coil (see text)

Printed circuit board available from the *EPE PCB Service*, code 392; plastic case, size and type to choice; plastic control knob (2 off); 50gm (2oz) reel of 26s.w.g. (25a.w.g.) enamelled copper wire, for tuning coil; card and glue for coil former; crystal earpiece and jack socket to suit; multistrand connecting wire; 9V battery, clips and holder; p.c.b. stand-off pillars; mounting nuts and bolts; solder pins; solder etc.



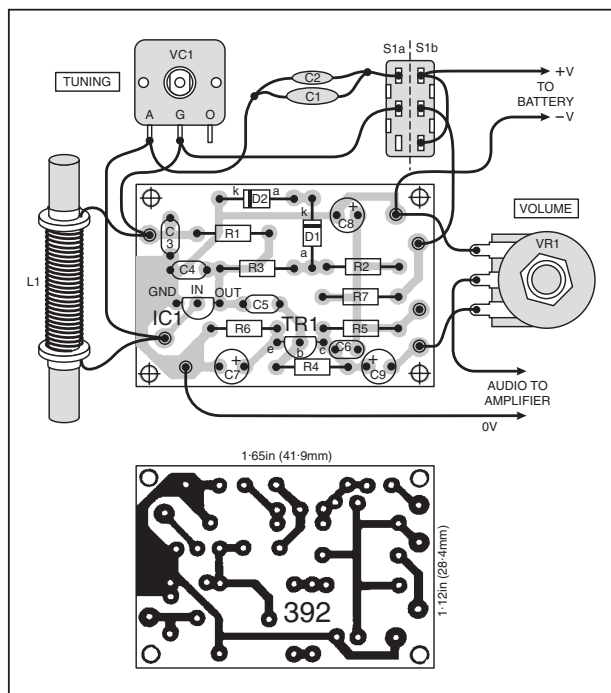


Fig.1.8. Printed circuit board component layout, interwiring to off-board components and full-size underside board copper track master.

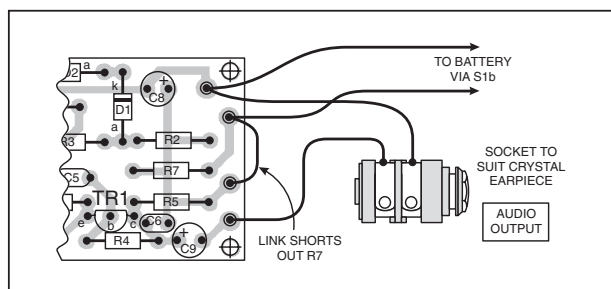


Fig.1.9. Connecting a crystal earpiece, via socket, directly to the p.c.b. in place of the Volume control. Note the "shorting" link wire.

Headphone and loudspeaker amplifiers will, in most cases, be connected across the same battery power supply, and resistor R7 and capacitor C8 decouple the tuner circuit in order to prevent instability. Bypass capacitor C6 connected across collector load R5 is also included to avoid instability. Audio output is taken from the collector of transistor TR1 and connected to the Volume control VR1, via d.c. blocking capacitor C9.

A crystal earpiece can be connected in place of the volume control but the output, especially when weaker signals are being received, will be barely adequate. With this arrangement there is no need for resistor R7, and provision is made, on the printed circuit board, for it to be shorted out (see Fig.1.9).

## CONSTRUCTION

If you have not already made up the "tuning coil" for the Crystal Set, construction of the TRF Receiver should commence with the winding of the ferrite loop aerial as detailed earlier in Fig.5 and as follows. Wind thin card (a postcard is ideal) around a 100mm (4in.) length of 9mm (3/8in.) diameter ferrite rod until an

overall diameter of 13mm (1/2in.) is achieved. Apply adhesive as the card is wound on.

Coil L1 consists of 100 turns of 26s.w.g. (25a.w.g.) enamelled copper wire close wound, i.e. with turns touching. Secure the start and finish of the winding with thin strips of masking tape wound tightly around the former. The task of producing a neat coil can be eased by slightly spacing the turns as they are wound on and repeatedly pushing them together with the thumb as the winding proceeds.

The inductance of this loop winding is higher than normal in order to ensure full Medium Wave coverage with the specified tuning capacitor (medium wave loops usually comprise about sixty turns on a 9mm (3/8in.) dia. rod). Longer rods, which will increase signal pick-up, may be used if a larger receiver can be tolerated.

Use rubber bands, strips of card or wood or plastic blocks to secure ferrite loop aerials. Do not use metal mounts as these can form a shorted turn and dramatically reduce efficiency.

## VARIABLE CAPACITORS

(Polythene dielectric type)

Some retailers supply extenders for the stubby spindle. If an extender has to be fabricated, use a 6mm diameter tubular stand-off bolted to the central hole in the spindle (bolt is usually 2mm). Grip the capacitor spindle when tightening bolt. **Do not tighten against internal end stop.**




Secure capacitors to bracket or front panel with two bolts driven into threaded holes in its front plate. **Bolts (usually 2mm) must not extend through the thickness of the front plate.**

Twin-gang capacitor lead-outs are usually thin metal strips. Moving vanes (the strip often marked 'G') should be connected to ground or the 0V rail. Strips for the fixed vanes, normally used to tune the aerial and oscillator circuits in a superhet receiver, are often marked "A" and "O". One or both should be connected to the "hot" end of the simple receiver's tuning coil.

Internal trimmers should be set to minimum capacitance when a variable is used with simple receivers. Twin-gang polyvaricons have two trimmers. Four-gang units have four trimmers.

For complete coverage of the medium wave band with this ferrite loop aerial, the variable capacitor should have a 5pF minimum capacitance and a maximum capacitance of at least 140pF. The aerial tuning section of most polythene dielectric variables, as used in transistor portables, should be suitable.

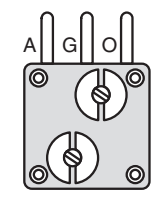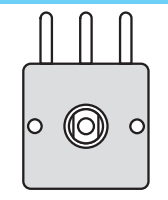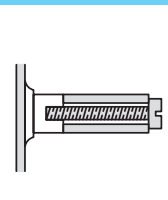If necessary, both sections (aerial and oscillator) can be connected in parallel to ensure the necessary maximum capacitance. This will, however, double the minimum capacitance and slightly curtail coverage at the high frequency end of the band.



## RECEIVER BOARD


Most of the TRF Receiver components are assembled on a small printed circuit board (p.c.b.). The topside component layout, off-board interwiring and a full-size underside copper foil master are shown in Fig.1.8. This board is available from the EPE PCB Service, code 392. How to connect an earpiece directly to the Receiver p.c.b. is illustrated in Fig.1.9.

Insert and solder in position the resistors and capacitors first and the semiconductors last. The 3-pin MK484 radio i.c. must be mounted close to the board to prevent instability: leave just sufficient lead length for the application of a miniature crocodile clip as a heat shunt whilst soldering.

Take care to remove all traces of the enamel from the ends of the coil winding in order to ensure a good connection. Solder pins, inserted at the lead-out points, will simplify the task of off-board wiring.
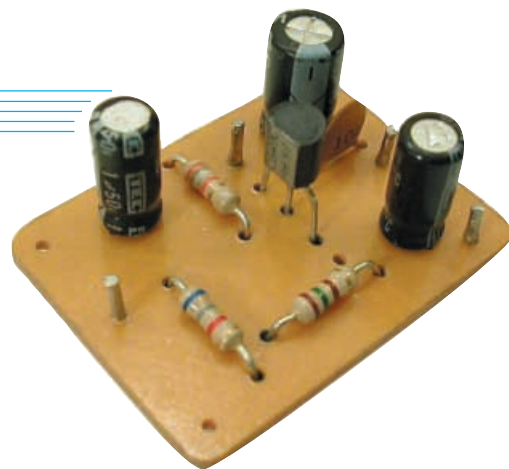
# HEADPHONE AMPLIFIER

*Add-on amplifier for personal listening*



## COMPONENTS

### HEADPHONE AMPLIFIER

#### Resistors

R1	39k
R2	5k8
R3	150Ω

See  
**SHOP**  
TALK  
page

#### Capacitors

C1	1μ radial elect. 16V
C2	100n disc ceramic
C3	47μ radial elect. 16V
C4	100μ radial elect. 16V

#### Semiconductors

TR1	BC549C npn small signal transistor
-----	------------------------------------

#### Miscellaneous

S1	d.p.d.t. centre-off toggle switch (see text)
----	--

Printed circuit board available from the *EPE PCB Service*, code 393; jack socket to suit 'phones; multistrand connecting wire; 9V battery, clips and holder; p.c.b. stand-off pillars; solder pins; solder etc.

**Approx. Cost**  
**Guidance Only**

**£6**  
excl. 'phones

The single transistor Headphone Amplifier circuit illustrated in Fig.1.10, will ensure an acceptable output via Walkman type 'phones. The audio input signal is coupled to the base of transistor TR1 via d.c. blocking capacitor C1. Base bias resistors R1 and R2, fix the standing collector current at around 4mA. Emitter bias is provided by R3, which is bypassed by C3.

Walkman type 'phones form transistor TR1's collector load, both earpieces being wired in series to produce an impedance of 64 ohms. Bypass capacitor C2 acts as a high frequency shunt across the 'phone leads. This measure avoids instability problems and is particularly necessary when the amplifier is used with some of the more sensitive receivers to be described later in the series.

Bypass capacitor C4 ensures stability when tuner and amplifier stages are powered by the same battery, particularly when battery impedance rises as it becomes exhausted. On/off control, S1b, is one half of a two-pole, centre-off, toggle switch.

## CONSTRUCTION.

All parts, except the 'phone socket and battery, are assembled on a small p.c.b. and the component layout, off-board wiring and full-size copper foil master are given in Fig.1.11. This board is available from the *EPE PCB Service*, code 393.

Follow the assembly sequence suggested for the TRF radio board. Again, solder pins at the lead-out points will ease the task of off-board wiring.

Wiring the output to the tip and centre ring on the jack socket will result in the series connection of the earpieces and produce a nominal 64 ohm load for transistor TR1.

## SPOT CHECKS

Check the two p.c.b.s for poor soldered joints and bridged tracks. Check the orientation of electrolytic capacitors and semiconductors.

Make sure the off-board wiring has been correctly routed and, if all is in order, connect the battery power supply.

Current consumption of the tuner/amp with a 9V supply and resistors R2 and R4 as specified in Table 1.1 should be approximately 2.5mA.

Readers who are keen to minimize battery drain could reduce bias resistor, R2, in Fig.1.10, to 4.7kΩ or less. This

will lower the standing current drawn by the Headphone Amplifier at the expense of maximum undistorted output.

The add-on amplifier stage will permit low-impedance Walkman type 'phones to be used with the Crystal Set (Fig.3). A Volume control is unnecessary: simply connect a 4700 ohm resistor (RX) to act as a diode load in place of the 'phones, and link receiver to amplifier via d.c. blocking capacitor, C1.

## PERFORMANCE

Performance of the MK484 TRF Receiver and Headphone Amplifier combination is far superior to the simple Crystal Set. The MK484 is, moreover, sufficiently sensitive to operate from a ferrite-cored loop and an external wire aerial and earth are not required.

Selectivity is barely adequate, and very powerful signals tend to spread across the dial. Rotating the ferrite loop aerial to null out the offending station will, however, usually effect a cure. (Loop aerials are directional and signal pick-up falls to a minimum when the axis of the coil is pointing towards the transmitter).

Although the circuit will permit the clear reception of a number of stations, sensitivity is not sufficient for the reception of weak signals. A simple add-on circuit, which will transform the performance of the receiver and make it as selective and sensitive as a commercial super-het, will be described next month.

Next month's article will also include an amplifier for readers who want loudspeaker operation, and a design for another simple, but high performance, medium and long wave receiver using individual transistors.

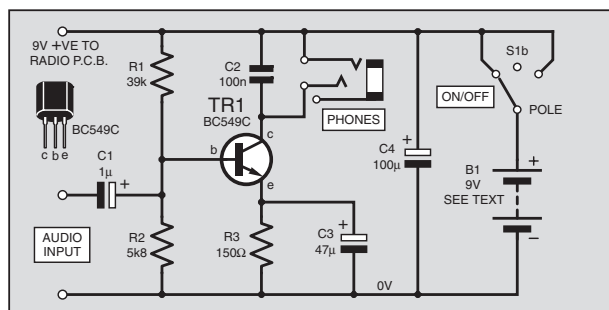


Fig.1.10. Circuit diagram for a single transistor Headphone Amplifier.


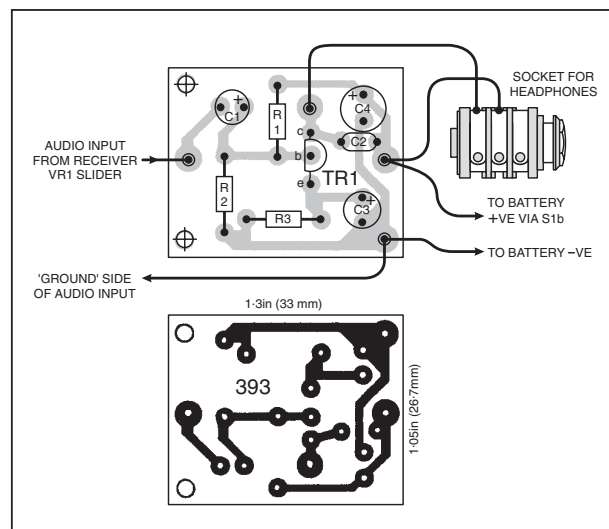


Fig.1.11. Headphone Amplifier printed circuit board component layout, wiring details and full-size copper foil master.

# CIRCUIT SURGERY

ALAN WINSTANLEY  
and IAN BELL

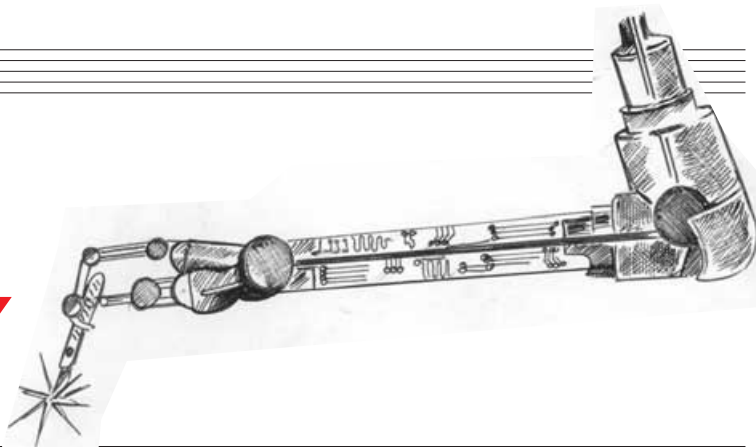

*We round off our three-part mini series showing beginners how to read circuit diagrams.*

IN the April and May issues we outlined the technique that every electronics enthusiast needs in order to be able to read a circuit diagram. We looked at basic schematic symbols for passive and semiconductor devices, and we also showed you how to compare transistor and diode symbols against their physical counterparts.

We round off this mini guide with a look at integrated circuits and last but not least, methods of depicting power rail connections. Earth, bus, ground, chassis – what do all these terms mean? Read on!

## A Chip Off The Block

These days, integrated circuits (i.c.s) are fundamental to the majority of *EPE* constructional projects, but even the most sophisticated of microcontroller device, such as the popular PICmicro family that are used in almost all of our micro projects, can be drawn in our circuit schematics very simply as a box!

Almost every i.c. package, with the exception of voltage regulator i.c.s and some specialist devices, contains at least eight pins: a modern microprocessor for a PC contains many hundreds of pins – and millions of miniature transistors inside! Circuit diagrams typically show just a simple box outline together with a pin number.

As an example of how i.c.s are shown in schematic diagrams, the 555 timer is shown in Symbol File-4 of Fig.1. Notice how the pin's functions are also labelled (often using shorthand that is puzzling to the inexperienced constructor), but on more complex circuit diagrams there may not be room to show this information. If we want to know what's actually inside the device, we could refer to a manufacturer's data sheet, but for many purposes it's all right just to treat the device as a building block.

Our very simple "circuit diagram" of Fig.1, April '03 p263, holds true for


depicting the use of integrated circuits. Each i.c. pin has a unique number, and we draw solid lines showing how each pin is wired to the rest of the circuitry. Sometimes, if a pin is to be left unconnected, you may see the letters "n.c." for "no connection" used. Otherwise, the pin may not be shown at all.

In the case of, for example, logic gates, it is common to separate out the individual gates and label them individually. A good example was shown in Fig.1, May '03 p334 – it shows two logic i.c.s (IC2, IC4) and a separate NAND logic gate that is part of a 74LS00 i.c.; hence the NAND gate's pins are numbered to correspond with the dual-in-line package numbering scheme. Note, however, that the NAND chip's essential power supply rails were not included (see later).


Pinout data for chips can be obtained by searching manufacturers' web sites including Philips Semiconductors ([www-eu.semiconductors.philips.com](http://www-eu.semiconductors.philips.com)) and Texas Instruments ([www.ti.com](http://www.ti.com)).

### SYMBOL FILE-4


DIMPLE NOTCH

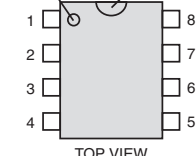

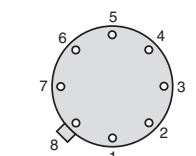
A DIMPLE AND/OR NOTCH DEPICTS PIN 1 OF A DUAL-IN-LINE I.C.



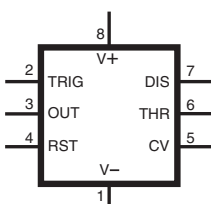TOP VIEW  
E.G. LM567H  
NATIONAL SEMICONDUCTOR



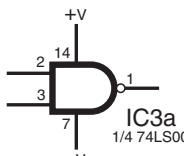HOW A 555 TIMER I.C. IS SHOWN IN CIRCUIT DIAGRAM. NOTE THE PIN NUMBERING LABELS AND FUNCTIONS.



AN INDIVIDUAL NAND GATE SHOWING PINOUTS, AND (OPTIONAL) POWER RAILS

## Identity Parade

As for identifying which way round an i.c. is connected, note that all dual-in-line (d.i.l.) chips follow a standard scheme, but unlike pinouts for transistors or l.e.d.s (which are always viewed from below), we show an **aerial view** of integrated circuits. The location of pin 1 can always be derived from a notch or a circular mark (or both) moulded into the i.c. package, and the rest of the pin numbers follow a standard pattern from there.

In some cases, alternative packages are used including TO5 metal can i.c.s, and it is best to consult manufacturer's datasheets to confirm the pinout details. There are other types of flat-pack i.c. available in industry that use complex multi-pin surface mount techniques, which won't be discussed further here.

## Board the Bus

As you may imagine, when there are many i.c.s in a circuit schematic then the interwiring can become highly complicated, to the point that it becomes pointless trying to draw every line. When data

Fig.1. A comparison of integrated circuit (i.c.) styles and pinout information in circuit diagrams.



has to be shifted or output by i.c.s, the data is transported by a "bus" – if the data is 8 or 16 bits wide or more, then in order to avoid drawing a rat's nest of lines in a circuit diagram, a wider line may be drawn, with pinout information being derived from the schematic as shown in Fig.2, which was part of our 6502 Micro Lab microprocessor trainer published in 1993. The pins of the microprocessor feed into a bus, the other end of which feeds into individual pins of the target component. Like-named pins are connected on each i.c.

## Power Play

This brings us to the final aspect of drawing circuit diagrams and the methods depicting the *power rails*. These days, a computer-aided design (CAD) package is often used to simulate circuits on-screen and also to produce schematics and p.c.b.s.

The CAD program already "knows" the pinouts of each device drawn into the circuit diagram. The designer can therefore

draft a diagram to depict how the components should be wired together, which creates a *netlist* (computerised p.c.b. data describing which components are connected where).

Using the netlist, p.c.b. software can then route a p.c.b. foil design, because the program also "knows" the *physical shape and pinout* of each device used. Unfortunately for us, the power supply details are often hidden in the background when circuits are drawn with CAD packages. The software knows the power connections needed for each i.c., so it does not show them in the schematic.

However, in the drawings used in *EPE*, supply rails are always shown clearly, and we include the power supply rails for individual logic gates etc. as well; usually, one gate is shown wired across the power supply (e.g. the NAND gate in Symbol-File 4 shows the power rails for the entire 74LS00 chip – all four gates being powered through this connection).

## Down to Earth

The automatic assumption of power supply rails can also be seen in more basic circuit diagrams, and it can cause an awful lot of confusion for beginners. The author recalls how, as a young enthusiast, he was fascinated by American text books on hobby electronics, but it was very strange to see how even the most trivial battery circuit appeared to be connected to earth (called "ground" in the USA and elsewhere). Why would a battery circuit need to be earthed?

In order to avoid cluttering circuit diagrams with "unnecessary" lines, one of the power supply rails (almost always 0V) can be omitted, and instead a ground symbol is used. In Fig.3 an example circuit uses the earth symbol to show how those components are actually to be connected to 0V. In automotive circuit diagrams, the chassis of the vehicle is usually wired to the negative battery terminal, and it is very common to therefore use ground or chassis symbols throughout the circuit to depict a chassis connection. Strictly speaking, a chassis symbol is used to show a *physical connection* to the metal frame of an apparatus or a vehicle, whilst a ground symbol is used to denote a common connection (usually a 0V rail). A.R.W.

- The component photos used in this mini series are included on the author's CD-ROM *Electronic Components Photos Vol. 1* available from *EPE*. It is ideal to help with presentations, catalogues, tutorials, projects etc. – see the *EPE Electronics CD-ROM* advertisement and order form elsewhere in this issue.

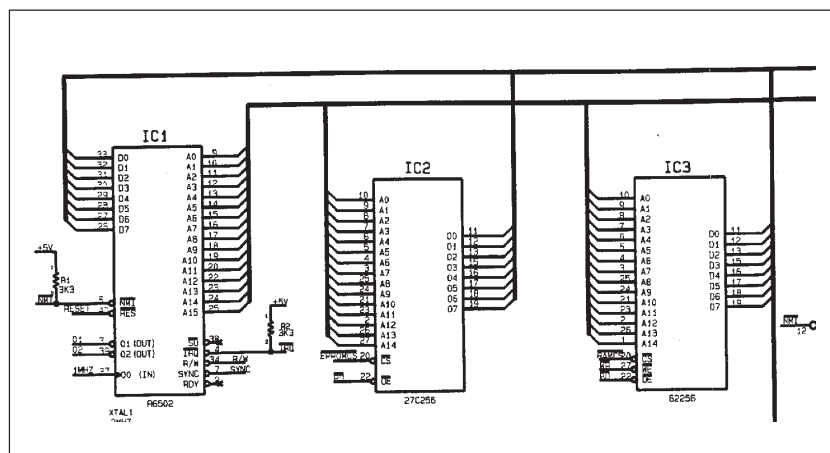


Fig.2. A typical example of how complex data buses might be shown on schematic diagrams.



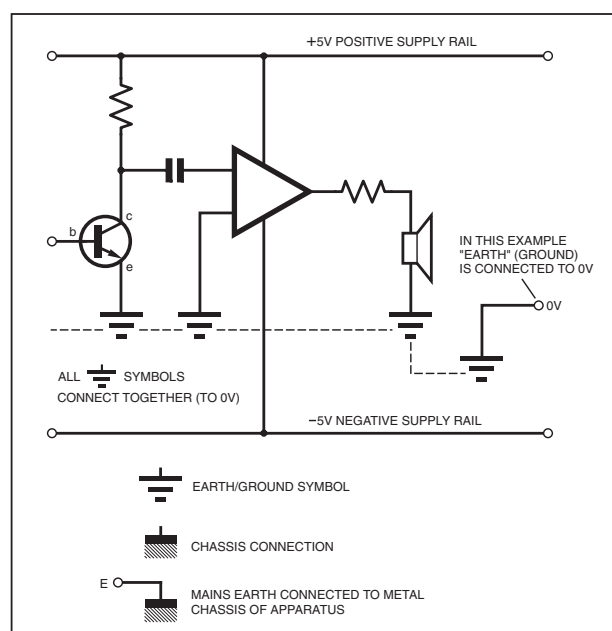



Fig.3. The use of ground and chassis symbols helps to avoid cluttering circuit diagrams with unnecessary lines.

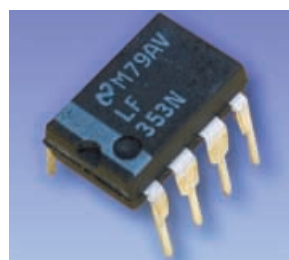

8-pin i.c. (d.i.l.) package.

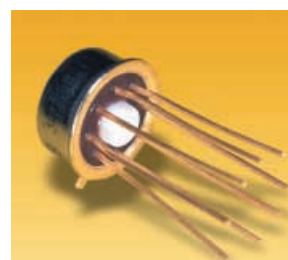

TO5 metal can package i.c.

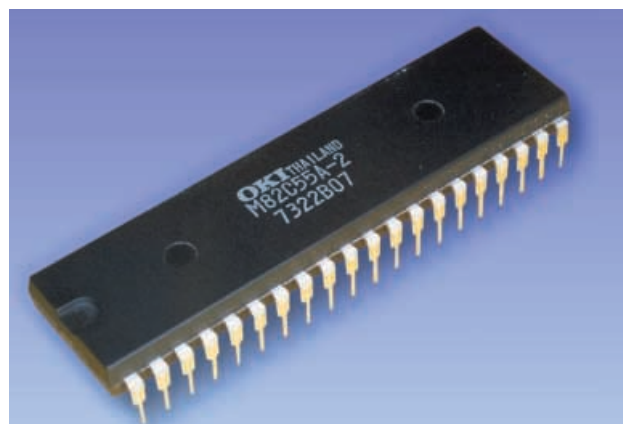

40-pin dual-in-line (d.i.l.) plastic package i.c.

# BACK TO BASICS



**BART TREPAK**

**Part Five**

*Illustrating how useful circuits can be designed simply using transistors.*

## MINI THEREMIN

**D**ESPITE their obvious uses in amplifying the sound of conventional acoustic musical instruments, transistors have had a great impact in terms of the actual generation of musical notes and rhythms.

This is especially true since integrated circuits (which are comprised of many transistors) were first introduced, enabling instruments such as electronic organs and synthesisers to be produced. These can produce sounds which mimic conventional instruments and are played selecting the required notes by pressing switches normally arranged as a piano keyboard.

In such instruments, each note may be generated by its own oscillator, or by a master oscillator and many divider stages to obtain the lower notes. Notes are then processed by filters and envelope shapers which tailor the waveform to produce the required sound, and fed to an amplifier and loudspeaker.

### THEREMIN

One instrument that differs radically from keyboard instruments is the Theremin, named after its inventor Leon Theremin. A Theremin produces the notes

in a completely different way and does not even require the musician to touch the instrument to play it!

All the notes are produced using the interaction of just two oscillators and the instrument can only play one note at a time. As well as the standard musical tones, all other frequencies in between can also be produced, gliding between them in response to hand movements.

This provides some interesting sounds but also makes the instrument quite difficult to play. This is even more true of the simplified version described here – professional Theremins also have a control enabling the signal to be muted by the performer so that the notes do not have to glide from one pitch to the next.

### BEAT FREQUENCY

The operation of a Theremin is based on two high frequency tuned circuit oscillators running at almost identical frequencies. This type of oscillator was discussed in the *Metal Detector* project in Part Two of this series (March '03).

Referring to the circuit diagram shown in Fig.30, the oscillators are based around transistors TR1 and TR2. Note that in this

case, however, the two oscillators use an inductive tap to generate the feedback, which is applied to the transistor bases via capacitors C1 and C3.

The first oscillator frequency is variable and the second is fixed. The frequency of oscillation depends on the values of the inductors and their tuning capacitors C2 and C4. In the case of the variable oscillator around TR1, it is also governed by the additional capacitance of the player's hand close to a metal plate or aerial. The inductance values are adjustable so that the frequencies of both oscillators can be tuned as required.

As the hand is moved closer to the plate, this capacitance increases causing a corresponding decrease in the frequency of the oscillator. The changes in capacitance are minute, however, resulting in only very small changes in frequency.

### MIXED SOUNDS

The outputs of two oscillators are mixed, resulting in both sum and difference frequencies. If the two basic frequencies are close enough, the resultant beat frequencies will be in the audio range. The interesting thing is that although the original frequencies are high and well above the audio range, a small change in one of them produces a large change in the audio beat frequency producing a very sensitive instrument with a wide pitch range.

The outputs from the oscillators are coupled by resistors R3 and R4 to capacitor C5 and into the mixer stage around TR3.

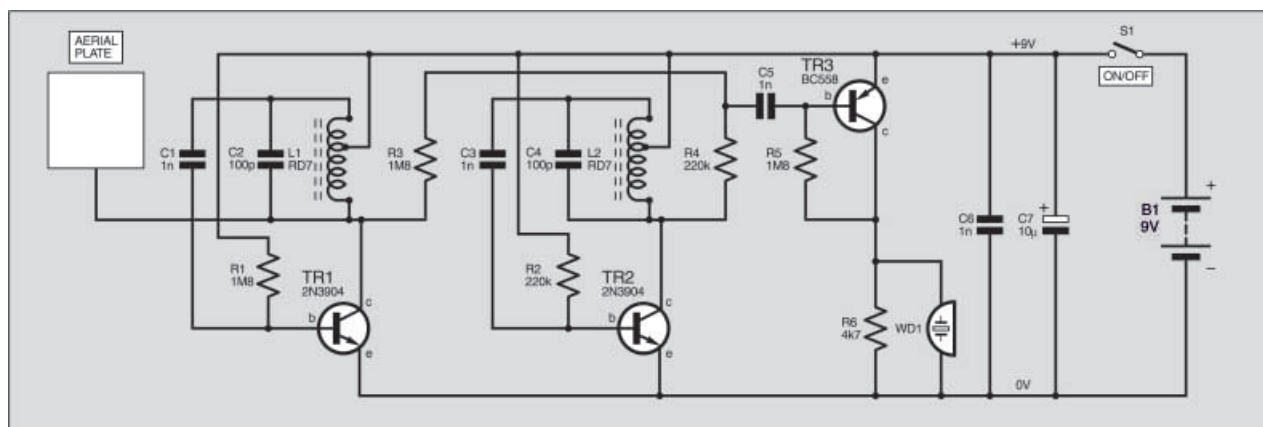


Fig.30. Complete circuit diagram for the Mini Theremin.

# COMPONENTS

## Resistors

R1, R3, R5 1M8 (3 off)  
R2, R4 220k (2 off)  
R6 4k7  
All 0.25W 5% carbon film

## Capacitors

C1, C3, C5, C6 1n disc ceramic, 2.5mm pitch (4 off)  
C2, C4 100p disc ceramic, 2.5mm pitch (2 off)  
C7 10 $\mu$  radial elect. 16V

## Semiconductors

TR1, TR2 2N3904 npn transistor (2 off)  
TR3 BC558 pnp transistor

## Miscellaneous

L1, L2 Toko RD7 inductor (2 off)  
S1 s.p.s.t. min. toggle switch  
WD1 piezo sounder

Stripboard, 19 holes x 8 strips; PP3 battery and clip; plastic case to suit; copper-clad p.c.b. laminate or aluminium plate, approx. 40mm x 50mm (see text); connecting wire; solder, etc.

Approx. Cost  
Guidance Only

**£6**  
excl. case & batt.

See  
**SHOP  
TALK**  
page


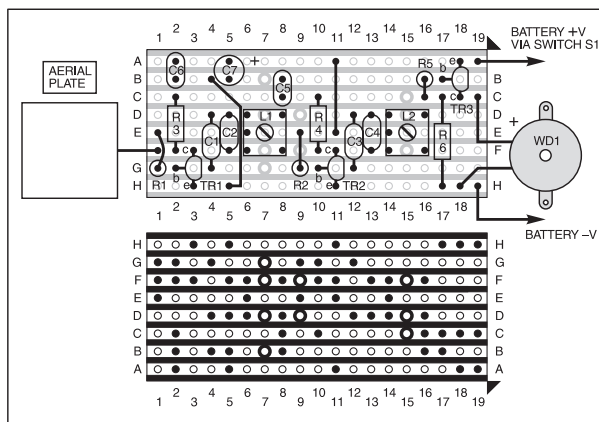


Fig.31. Stripboard component layout, interwiring and details of breaks required in the underside copper tracks.

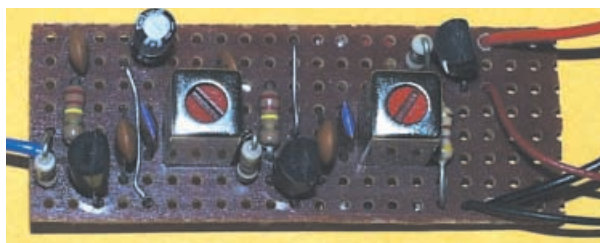

Component layout on the completed circuit board.

The resistors have relatively high values to prevent the oscillators from interacting undesirably and locking together. The mixer also amplifies the resultant frequencies and drives the piezo transducer WD1.

Frequencies above the audio range are largely attenuated by the capacitance of the transducer, leaving only the audio tone beat frequency. However, if the output is to be connected to an external amplifier in place of WD1, a 2200pF capacitor should be connected in parallel with resistor R6 as the signal could otherwise cause interference in radio equipment.

The circuit is powered by a 9V battery, supplied via switch S1. Capacitors C6 and C7 are included to ensure a low impedance supply at both low and high frequencies. The current consumption is about 1mA.

## CONSTRUCTION

The complete circuit is built on a small piece of stripboard having 19 holes x 8 strips, as shown in Fig.31. Before starting construction, the tracks should be cut in the places indicated using a 2.5mm drill, or the special tool available for this.

Two wire links are also required and these can be made from discarded component leads. As with all projects in this series, the layout applies to the specified transistors and if substitutes are used, care should be taken as pinouts may differ.

Inductors L1 and L2 are small i.f. (intermediate frequency) transformers normally used in radio receivers and the types specified do not have integral capacitors. The cans have solder lugs enabling these to be soldered to fix them, although in this application the lugs do not fit into the pitch of the stripboard so they are simply bent up underneath the component before it is mounted.

WD1 is a piezo sounder (not to be confused with a piezo buzzer which contains an integral drive circuit) and this may be connected either way around.

The "tuning" plate should consist of a small piece of aluminium or copper-clad p.c.b. laminate, measuring about 40mm x 50mm, connected to the circuit by a short wire. Alternatively, this can take the form of a short aerial 10cm to 15cm long connected to the same point on the circuit.

If the unit is to be mounted in a box, a plastic case with a battery compartment would be most suitable.


## TUNING

When finished, the circuit must be tuned for correct operation by adjusting the inductor cores so that both oscillators are working at around the same frequency.

Only use a plastic blade for adjusting the cores – a metal tool could damage them.

It is best to set one core to about its mid-position and adjust the other until a whistle is heard from the sounder. Bringing your hand near the sensor plate will then result in a lower pitch sound. Alternatively the circuit may be adjusted beyond this point so that the frequency rises as your hand approaches the sensor.

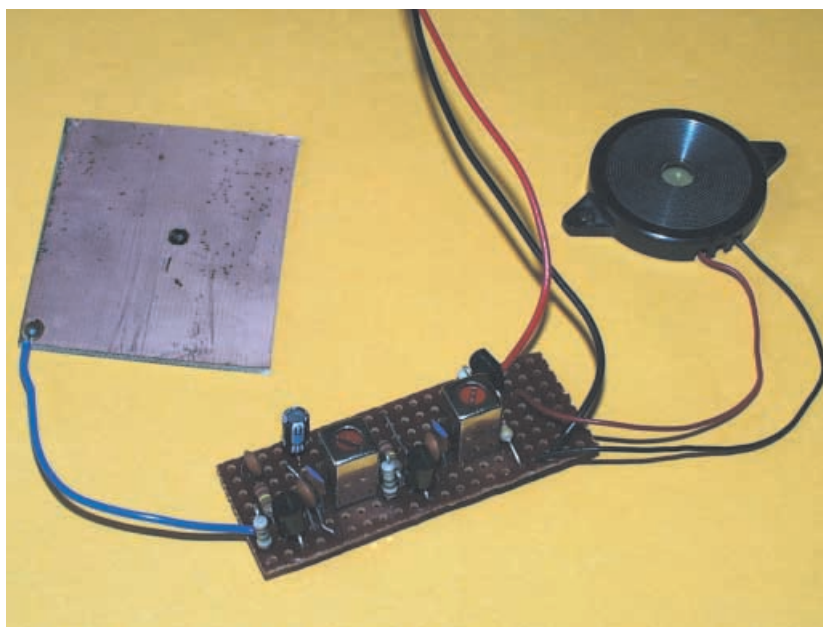Apart from its undoubted(?) musical applications, the unit could find uses as a rudimentary proximity alarm to detect the presence of people or animals, although the stability of this simple circuit is not ideal for such applications.



Finished Mini Theremin showing wiring to the "tuning" plate and piezoelectric sounder. The tuning plate is an off-cut from a piece of copper-clad board.



# TWILIGHT SWITCH

**T**HIS circuit is designed to switch on a low-power lamp when it gets dark and switch it off again at sunrise. It could, for example, be used as a burglar deterrent to give the impression that a house is occupied, or to light a path or porch during the hours of darkness.

With a slight modification, it could also be used as a medicine cupboard alarm to give a warning when it has been opened or, by changing the sensor, as a temperature controller (thermostat).

on TR1's base, causing both transistors to switch off rapidly. With TR2 off, TR3 also switches off, as does l.e.d. D1.

With falling light levels, the l.d.r. resistance increases and the voltage at TR1's emitter rises. However, since TR2 is off, the threshold voltage will now be determined only by R4 and R5 (about 3V with the component values given). The input level will therefore have to rise above this value before TR1 can switch on and the circuit revert to its former state with all three transistors on.

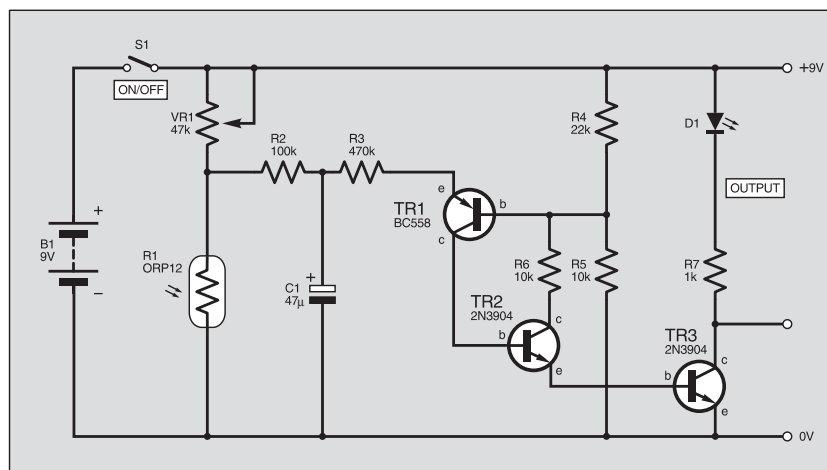


Fig.32. Circuit diagram for the light sensitive Twilight Switch.

## CIRCUIT DETAILS

Referring to the circuit diagram in Fig.32, light dependent resistor (l.d.r.) R1 is used as the light sensor. In bright conditions, its resistance is around 2k $\Omega$  rising to over 20k $\Omega$  in low light and over 1M $\Omega$  in darkness.

Transistors TR1 and TR2 form a complementary Schmitt trigger circuit that has two switching thresholds. Assuming both TR1 and TR2 are on, resistors R4 and R5 are connected across the power supply as a potential divider. They set the voltage applied to the base of TR1 at just under 3V, assuming a 9V supply.

With the l.d.r. in darkness, the voltage at its junction with preset VR1 will be above that on TR1's base. The sensor voltage is applied to TR1's emitter via resistors R2 and R3. Capacitor C1 smooths out fluctuations in light intensity during daylight conditions, such as caused by shadows moving across the l.d.r., or illumination by car headlights at night.

## LIGHT LEVELS

During darkness, the voltage from the l.d.r. will be sufficient to cause transistor TR3 to be turned on via TR1 and TR2. As a result, l.e.d. D1 is switched on, via ballast resistor R7.

As the light level increases, the resistance of the l.d.r. falls so that the input voltage to the circuit also falls. Once it falls below 2V, TR1 begins to switch off. This causes TR2 to switch off raising the voltage

It will be seen that there is a difference between the brightness levels at which the circuit switches on and off. This property is called hysteresis and is useful as it gives the circuit a "snap" action, switching on and off rapidly even if the input is changing slowly. It also prevents the lamp switching on and off as the thresholds are approached. Note that altering the value of R6 will vary the hysteresis.

## MAINS OPTION

Transistor TR3's collector load, comprising l.e.d. D1 and R7, could be replaced by, or used in conjunction with, an opto-isolated triac or a relay to switch on a mains lamp, as shown in Fig.33b and Fig.33c.

Note that the mains voltage existing at the output of both these circuits is dangerous and these two options should only be built under competent supervision. Suitable insulation, earthing and fuse arrangements must be provided.

The opto-triac type MOC3020 can handle output currents up to 100mA, i.e. a maximum of 23W of 230V a.c. mains power. The typical maximum size of mains driven lamp that can be used with it is thus approximately 15W.

With relay control, the maximum lamp power is limited only by the rating of the relay contacts.

A problem that could be encountered if a mains lamp is fitted is that of the circuit oscillating. When the light level falls, the light will switch on and the ambient brightness will increase causing the lamp to switch off again. The large hysteresis should help to prevent this but it is important that the sensor is positioned so that it cannot "see" the light from the lamp.

## COMPONENTS

### Resistors

R1	ORP12 light dependent resistor
R2	100k
R3	470k
R4	22k
R5, R6	10k (2 off)
R7	1k

All 0.25W 5% carbon film

### Capacitor

C1	47 $\mu$ radial elect. 16V
----	----------------------------

### Semiconductors

D1	red l.e.d.
TR1	BC558 pnp transistor
TR2, TR3	2N3904 npn transistor (2 off)

### Miscellaneous

S1	s.p.s.t. min. toggle switch
VR1	47k skeleton preset potentiometer
WD1	piezo buzzer

Stripboard, 14 holes x 7 strips; PP3 battery and clip; case to suit (see text); relay (optional), 12V coil with mains contacts, opto-triac (optional) MOC3020 or MOC3040, 12V Buzzer (optional); connecting wire; solder, etc.

Approx. Cost  
Guidance Only

excl. case, relay, opto-triac & batt.

**£6**

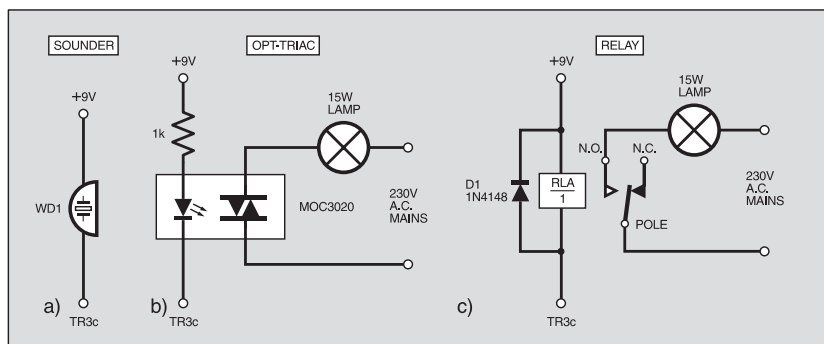


Fig.33. Circuit details for alternative output options.


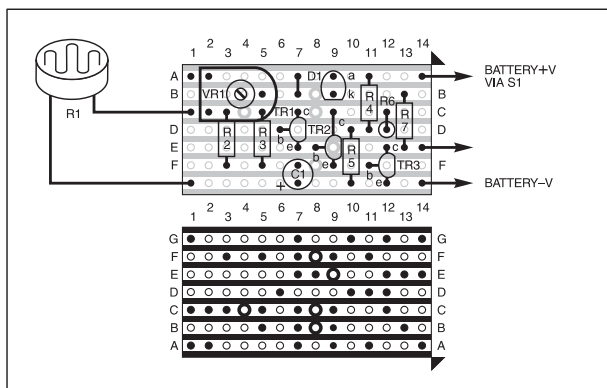


Fig.34. Component layout, wiring and copper break details.

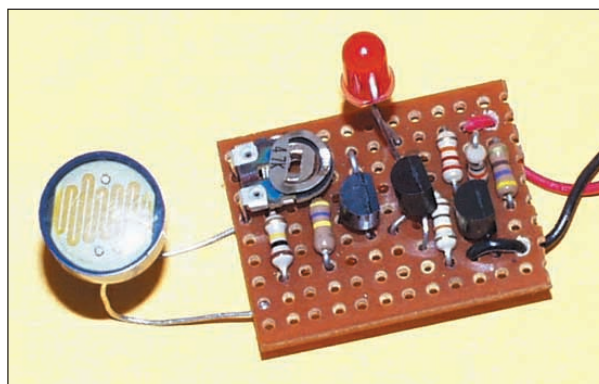

Completed prototype Twilight Switch.

## OTHER OPTIONS

A simple thermostat could be built by replacing the l.d.r. with an n.t.c. thermistor (negative temperature coefficient – resistance falls with increases in temperature). Depending on the resistance of the type used, the value of VR1 may need to be altered.

By connecting a buzzer across l.e.d. D1 and R7, and transposing the l.d.r. and preset VR1, a simple medicine cupboard alarm can be made. In this case TR3 will switch on when the ambient light level increases (i.e. when the cupboard door is opened) and switch off when it is dark.

The response delay can be removed if required by omitting capacitor C1.

## CONSTRUCTION

The circuit may be built on a piece of stripboard measuring 14 holes by 7 strips

as shown in Fig.34. Before assembling and soldering the components on the board, the tracks should be cut in the places indicated by means of a 2.5mm drill or the tool available for this purpose.

Take care to ensure that the transistors, l.e.d. and electrolytic capacitor C1 are inserted the correct way around. There is also one link required which can be made from a piece of discarded resistor lead.

It is also important to connect the buzzer (if used) correctly. These components often have the polarity indicated by the lead with red being positive. Note that a unit with an internal oscillator is required.

The l.d.r. (or thermistor) is not polarity sensitive and may be connected either way around.

The mains switching options **must NOT** be built on the stripboard but as a separate

unit and connected to the control circuit by suitable leads. To ensure safety with the mains switching option, the complete circuit must be mounted in an earthed metal case with a suitable mains input plug and outlet socket for the lamp. A fuse and fuseholder should be included, rated to suit the lamp used.

Do not adjust the circuit with the mains connected or operate the unit with the box open. If the circuit is used to control a mains lamp, the l.e.d. will be superfluous but may be retained.

Setting up consists of adjusting preset VR1 so that the circuit switches at the required light level. This may be simulated by shielding the l.d.r. and adjusting VR1 accordingly and is best done before C1 is soldered into the circuit so that the unit responds immediately to changes in light levels. □

# TRcontrol Solutions

Innovative Products Imaginative Solutions




I<sup>2</sup>C and Serial LCD Modules

Embedded Internet Solutions



Rapid Development Micro-Controllers

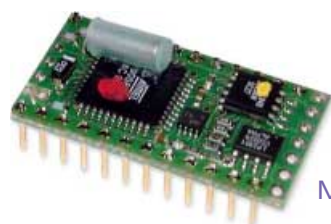

Visit our site [www.trcontrolsolutions.com](http://www.trcontrolsolutions.com) or Phone us on 020 8823 9230

# TOTALROBOTS

Robotics, Control & Electronics Technology

BEAM Robots



Programmable Mobile Robots

Robot Arms



Visit our site [www.totalrobots.com](http://www.totalrobots.com) or Phone us on 020 8823 9220

# New Technology Update

*Adding silicon to Li-Ion battery electrodes improves charge level performance.  
Ian Poole reports.*

**B**ATTERY technology is an increasingly important part of today's electronics scene. It was not many years ago when Nickel Cadmium cells were the only rechargeable types on the market. By today's standards they were inefficient in terms of energy storage density. Additionally the cadmium they contained made them difficult to dispose of in an environmentally friendly manner.

Since then technology has moved on significantly. Nickel Metal Hydride cells arrived. These cells provided an improvement in performance, but probably more important they were more environmentally friendly. However, a significant leap in performance has been made by the introduction of Lithium Ion or Li-Ion cells. This technology offers a significant improvement in performance, enabling much higher levels of charge to be stored in a given volume or battery weight.

Even these new cells, though, are undergoing further development to improve their performance. Developments at the Sandia Labs in California promise to give improvements of up to 400% according to Jim Wang, Manager of the Analytical Materials Science Department at Sandia.

## Li-Ion Cells

Like many other types of cell, Lithium Ion cells consist of a positive electrode, a negative electrode and a separator. The cathode or positive electrode consists of lithium metal oxide. The other metal in this oxide may be a variety of metals. One that is often used is cobalt. The anode or negative electrode is made from activated carbon. Between these two electrodes there is a physical separator to ensure that the two electrodes do not touch, and it also acts as an electrolyte to provide a conduction path between the electrodes.

In the charge-discharge cycle a complicated chemical reaction occurs where the lithium in the positive electrode is ionised during the charge process, ions moving to the other electrode. During the discharge part of the cycle, ions move to the positive electrode and return it to its original structure.

Lithium-Ion cells offer many advantages over previous types of cell. They have a long cycle life, and they offer approximately two and a half times the energy density of Nickel Cadmium. When compared to Nickel Metal Hydride, they offer approximately twice the energy density. Their voltage is higher than the other two technologies. At 3-6 volts it is three times that of the other commonly used

forms of cell. This is a major advantage in many applications where the 1-2 volts provided by both Nickel Cadmium and Nickel Metal Hydride is normally too low. Additionally the self discharge characteristic of these cells is very low. However, one of the major advantages is that they offer a competitive cost when compared to the other technologies.

Their major disadvantage is that they must not be electrically stressed. Overcharging them destroys them very quickly. To overcome this, battery management systems are always employed with these cells.

## Improvements

The developments that have been undertaken at Sandia not only promise more powerful batteries, but also ones that last longer. It is found that when Li-Ion batteries are cycled through a charge-discharge cycle they lose a small amount of capacity each time.

To overcome this problem, Sandia have added silicon to the anode structure. The silicon on its own offers more than 10 times the capacity potential of graphite, but is hampered by a rapid capacity loss during the battery cycling phase. When small particles of silicon are combined within a graphite matrix, however, the large capacities are retained.

The silicon on its own is not suitable for constructing anodes and therefore a mix of the two materials is used. The marriage of silicon and graphite may improve the specific capabilities of commercial graphite anode materials up to 400%, said Jim Wang.

The silicon graphite composites can be produced using a simple milling process. This is a standard production methodology that is common within industry. This means that it is relatively easy to implement and no new processes or handling techniques are required.

In a conventional cell, one lithium ion is absorbed between each six carbon atoms. In the new cell technology each silicon atom holds four lithium ions. This is a 24-fold increase in capacity per atom.

There are a number of problems to be overcome. The silicon anode needs a very large surface area. In addition to this it must be physically able to cope with the doubling in size that the silicon undergoes when it absorbs that vast amount of lithium.

Both these problems have been overcome by using small silicon particles in a matrix of graphite. This allows the silicon to present a sufficiently high surface area

whilst also still being able to expand without distorting the overall anode assembly.

## Development Process

In reaching its conclusions about the new material's performance, Wang and other researchers at Sandia took a methodical approach that spanned three years. First they produced composite powders with varying silicon-to-carbon ratios and microstructures. Then they produced electrodes from the resultant powders and evaluated their performance by electrochemical measurements. They then examined structural changes in the electrodes during cycling to understand the lithium transfer mechanism and materials phase changes to further improve the new material.

According to Greg Roberts, a Post Doctoral team member at Sandia, the research and development focused on the replacement of graphite electrodes in rechargeable lithium batteries and this has taken many forms over the years. He explained that possible replacement candidates included non-graphitic carbons, inter-metallics, oxides, nitrides, and composites.

While each material has unique advantages and disadvantages that need to be considered when designing a battery for a specific application, Roberts said the silicon/graphite electrode materials are promising for applications that require high capacities delivered at low-to-moderate rates.

Sandia researchers acknowledge that there are some potential problems with the new material. The complete elimination of fading of long-term cycling capacity in the silicon-based electrodes may not be possible, though it is possible that it can be minimised by the design of the carbon-silicon composite microstructure.

The research team are confident that the silicon/graphite electrode materials have opened the door for future breakthroughs. "We believe that only other silicon-containing electrode materials can compete with the large capacities that our silicon/graphite composites have demonstrated," Wang said.

## Impact

It is anticipated that the discovery will have wide-ranging impact on a variety of consumer and defence applications as the use of Li-Ion batteries is now widespread and there is always a great demand for increased battery life. Mobile phone and laptop computer users will welcome any improvements in battery life.



We can supply back issues of *EPE* by post, most issues from the past three years are available. An *EPE* index for the last five years is also available at [www.epemag.wimborne.co.uk](http://www.epemag.wimborne.co.uk) or see order form below. Alternatively, indexes are published in the December issue for that year. Where we are unable to provide a back issue a photocopy of any *one article* (or *one part* of a series) can be purchased for the same price. Issues from Nov. 98 are available on CD-ROM – see next page – and issues from the last six months are also available to download from [www.epemag.com](http://www.epemag.com).

## DID YOU MISS THESE?

### FEB '02

**PROJECTS** • PIC Spectrum Analyser • Guitar Practice Amp • HT Power Supply • Versatile Current Monitor.

**FEATURES** • Teach-In 2002 – Part 4 • Ingenuity Unlimited • Russian Space Shuttle Revisited • Circuit Surgery • Interface • New Technology Update • Net Work – The Internet Page.



### MAR '02

**PROJECTS** • MK484 Shortwave Radio • PIC Virus Zapper • RH Meter • PIC Mini-Enigma.

**FEATURES** • Teach-In 2002 – Part 5 • Ingenuity Unlimited • Programming PIC Interrupts-1 • Circuit Surgery • Practically Speaking • New Technology Update • Net Work – The Internet Page.

### APR '02

**PROJECTS** • Electric Guitar Tuner • PIC Controlled Intruder Alarm • Solar Charge and Go • Manual Stepper Motor Controller.

**FEATURES** • Teach-In 2002 – Part 6 • Interface • Programming PIC Interrupts-2 • Circuit Surgery • Ingenuity Unlimited • New Technology Update • Net Work – The Internet Page • **FREE** Giant Op.Amp Data Chart.

### MAY '02

**PROJECTS** • PIC Big-Digit Display • Simple Audio Circuits – 1 • Freezer Alarm • Washing Ready Indicator.

**FEATURES** • Teach-In 2002 – Part 7 • Ingenuity Unlimited • Practically Speaking • New Technology Update • Circuit Surgery • Net Work – The Internet Page.

### JUNE '02

**PROJECTS** • Biopic Heartbeat Monitor • Frequency Standard Generator • Simple Audio Circuits – 2 • World Lamp.

**FEATURES** • Teach-In 2002 – Part 8 • Interface • New Technology Update • Circuit Surgery • Ingenuity Unlimited • Net Work – The Internet Page.

### JULY '02

**PROJECTS** • EPE StyloPIC • Infra-Red Autoswitch • Simple Audio Circuits – 3 • Rotary Combination Lock.

**FEATURES** • Teach-In 2002 – Part 9 • Practically Speaking • Using The PIC's PCLATH Command • Ingenuity Unlimited • Circuit Surgery • New Technology Update • Net Work – The Internet Page.

### AUG '02

#### Photocopies only

**PROJECTS** • PIC World Clock • Pickpocket Alarm • Big-Ears Buggy • Simple Audio Circuits – 4.

**FEATURES** • Teach-In 2002 – Part 10 • Using Square Roots with PICs • Ingenuity Unlimited • Evolutionary Electronics • Interface • Circuit Surgery • Net Work – The Internet Page.

### SEPT '02

#### Photocopies only

**PROJECTS** • Freebird Glider Control • Portable Telephone Tester • *EPE* Morse Code Reader • Vinyl to CD Preamp.

**FEATURES** • Circuit Surgery • New Technology Update • Practically Speaking • Net Work • Flowcode for PICmicro • Logic Gate Inverter Oscillators • Net Work – The Internet Page.

### OCT '02

#### Photocopies only

**PROJECTS** • *EPE* Bounty Treasure Hunter • IC Tester • Headset Communicator • PIC-Pocket Battleships.

**FEATURES** • Circuit Surgery • New Technology Update • Logic Gate Inverter Oscillators – 2 • Interface • Network – The Internet Page • Using TK3 With Windows XP and 2000.

### NOV '02

#### Photocopies only

**PROJECTS** • *EPE* Hybrid Computer – 1 • Tuning Fork and Metronome • Transient Tracker • PICAXE Projects-1 (Egg Timer – Dice Machine – Quiz Game Monitor).

**FEATURES** • Practically Speaking • Ingenuity Unlimited • Circuit Surgery • New Technology Update • Net Work – The Internet Page.

### DEC '02

**PROJECTS** • Versatile PIC Flasher • *EPE* Hybrid Computer – 2 • Door Defender • PICAXE Projects – 2 (Temperature Sensor – Voltage Sensor – VU Indicator).

**FEATURES** • Electronic Paper • Alternative Uses for Transistors • Interface • Circuit Surgery • New Technology Update • Ingenuity Unlimited • Net Work – The Internet Page • 2002 Annual Index.

### JAN '03

**PROJECTS** • *EPE* Minder • F.M. Frequency Surfer • Wind Speed Meter • PICAXE Projects-3 (Chaser Lights).

**FEATURES** • Who Really Invented The Transistor • TechnoTalk • Circuit Surgery • Practically Speaking • New Technology Update • Computer GOTOS • Ingenuity Unlimited • Net Work – The Internet Page.



### FEB '03

**PROJECTS** • Wind Tunnel • Brainbot Buggy • Back To Basics-1 (Hearing Aid, Audio Power Amplifier) • Tesla High Voltage Transformer.

**FEATURES** • In The Bag • Techno Talk • Circuit Surgery • New Technology Update • Interface • Ingenuity Unlimited • Net Work – The Internet Page.



### MAR '03

**PROJECTS** • Wind-Up Torch Mk II • 200kHz Function Generator • Driver Alert • Back-To-Basics-2 (Metal Detector, Simple Timer).

**FEATURES** • Ingenuity Unlimited • Practically Speaking • Techno Talk • New Technology Update • Circuit Surgery • Peak LCR Component Analyser Review • Net Work – The Internet Page.

### APR '03

**PROJECTS** • Atmospherics Monitor • Intelligent Garden Lights Controller • Back-To-Basics-3 (Touch Light, Plant Watering Reminder) • Earth Resistivity Logger-Part 1.

**FEATURES** • Ingenuity Unlimited • Techno Talk • New Technology Update • Circuit Surgery • Interface • Network – The Internet Page • **SPECIAL SUPPLEMENT** – *EPE* PIC Tutorial V2-Part 1.

### MAY '03

**PROJECTS** • Super Motion Sensor • Earth Resistivity Logger – Part 2 • Door Chime • Back-To-Basics-4 (Live Wire Detector, Medium Wave Radio).

**FEATURES** • Ingenuity Unlimited • Techno Talk • Practically Speaking • Circuit Surgery • Net Work – The Internet Page • **SPECIAL SUPPLEMENT** – *EPE* PIC Tutorial V2 – Part 2.

## BACK ISSUES ONLY £3.50 each inc. UK p&p.

Overseas prices £4 each surface mail, £5.50 each airmail.

We can also supply issues from earlier years: 1998 (except Jan. to May, July, Sept., Nov., Dec.), 1999 (except Aug., Dec.), 2000 (except Feb.), 2001 (except May, Sept., Oct.), 2002 (except Aug. to Nov.) Where we do not have an issue a photocopy of any *one article* or *one part* of a series can be provided at the same price.

### ORDER FORM – BACK ISSUES – PHOTOCOPIES – INDEXES

- ☐ Send back issues dated .....
- ☐ Send photocopies of (article title and issue date) .....
- ☐ Send copies of last five years indexes (£3.50 for five inc. p&p – Overseas £4 surface, £5.50 airmail)

Name .....

Address .....

.....Tel: .....

☐ I enclose cheque/P.O./bank draft to the value of £ .....

☐ Please charge my Visa/Mastercard/Amex/Diners Club/Switch £ ..... Switch Issue No. ....

Card No. ....

Card Expiry Date ..... Card Security Code ..... (The last 3 digits on or just under the signature strip)

SEND TO: Everyday Practical Electronics, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown, Dorset BH22 9ND.

Tel: 01202 873872. Fax: 01202 874562.

E-mail: [orders@epemag.wimborne.co.uk](mailto:orders@epemag.wimborne.co.uk) On-line Shop: [www.epemag.wimborne.co.uk/shopdoor.htm](http://www.epemag.wimborne.co.uk/shopdoor.htm)

Payments must be in £ sterling – cheque or bank draft drawn on a UK bank. Normally supplied within seven days of receipt of order.

Send a copy of this form, or order by letter if you do not wish to cut your issue.


M06/03
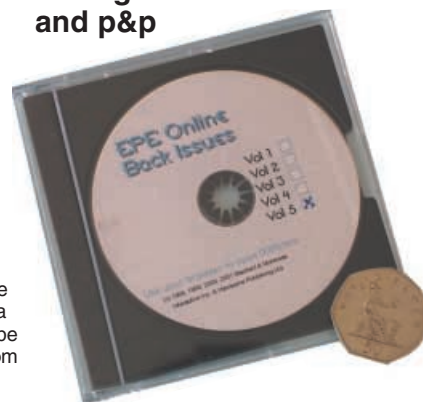
# STORE YOUR BACK ISSUES ON MINI CD-ROMS



**VOL 8  
NOW AVAILABLE**

**ONLY  
£14.45** each  
including VAT  
and p&p



A great way to buy *EPE* Back Issues – our mini CD-ROMs contain back issues from our *EPE Online* website plus bonus articles, all the relevant PIC software and web links. Note: no free gifts are included. All this for just £14.45 each including postage and packing.

## **VOL 1 CONTENTS**

BACK ISSUES – November 1998 to June 1999

## **VOL 2 CONTENTS**

BACK ISSUES – July 1999 to December 1999

## **VOL 3 CONTENTS**

BACK ISSUES – January 2000 to June 2000

## **VOL 4 CONTENTS**

BACK ISSUES – July 2000 to Dec. 2000

## **VOL 5 CONTENTS**

BACK ISSUES – January 2001 to June 2001

## **VOL 6 CONTENTS**

BACK ISSUES – July 2001 to December 2001

## **VOL 7 CONTENTS**

BACK ISSUES – Jan 2002 to June 2002

## **VOL 8 CONTENTS**

BACK ISSUES – July 2002 to December 2002

## **WHAT IS INCLUDED**

All volumes include the full editorial content of every listed issue, plus all the available **PIC Project Codes** for the PIC projects published in those issues.

**Note** that no advertisements are included in Volumes 1 and 2; from Volume 5 onwards the available relevant software for *Interface* articles is also included.

## **EXTRA ARTICLES – ON ALL VOLUMES**

**BASIC SOLDERING GUIDE** – Alan Winstanley's internationally acclaimed fully illustrated guide. **UNDERSTANDING PASSIVE COMPONENTS** – Introduction to the basic principles of passive components. **HOW TO USE INTELLIGENT L.C.D.s**, By Julian Ilett – An utterly practical guide to interfacing and programming intelligent liquid crystal display modules. **PhyzyB COMPUTERS BONUS ARTICLE 1** – Signed and Unsigned Binary Numbers. By Clive "Max" Maxfield and Alvin Brown. **PhyzyB COMPUTERS BONUS ARTICLE 2** – Creating an Event Counter. By Clive "Max" Maxfield and Alvin Brown. **INTERGRAPH COMPUTER SYSTEMS 3D GRAPHICS** – A chapter from Intergraph's book that explains computer graphics technology in an interesting and understandable way with full colour graphics.

**EXTRA ARTICLE ON VOL 1 & 2. THE LIFE & WORKS OF KONRAD ZUSE** – a brilliant pioneer in the evolution of computers. A bonus article on his life and work written by his eldest son, including many previously unpublished photographs.

NOTE: These mini CD-ROMs are suitable for use on any PC with a CD-ROM drive. They require Adobe Acrobat Reader (available free from the Internet – [www.adobe.com/acrobat](http://www.adobe.com/acrobat))

## **Order on-line from**

[www.epemag.wimborne.co.uk/shopdoor.htm](http://www.epemag.wimborne.co.uk/shopdoor.htm)

or [www.epemag.com](http://www.epemag.com) (USA \$ prices)

or by phone, Fax, E-mail or Post

## **BACK ISSUES MINI CD-ROM ORDER FORM**

Please send me ..... (quantity) BACK ISSUES CD-ROM **VOL 1**  
Please send me ..... (quantity) BACK ISSUES CD-ROM **VOL 2**  
Please send me ..... (quantity) BACK ISSUES CD-ROM **VOL 3**  
Please send me ..... (quantity) BACK ISSUES CD-ROM **VOL 4**  
Please send me ..... (quantity) BACK ISSUES CD-ROM **VOL 5**  
Please send me ..... (quantity) BACK ISSUES CD-ROM **VOL 6**  
Please send me ..... (quantity) BACK ISSUES CD-ROM **VOL 7**  
Please send me ..... (quantity) BACK ISSUES CD-ROM **VOL 8**

**Price £14.45 each** – includes postage to anywhere in the world.

Name .....

Address .....

..... Post Code .....

☐ I enclose cheque/P.O./bank draft to the value of £ .....

☐ Please charge my Visa/Mastercard/Amex/Diners Club/Switch

£ .....

Card No. ....

Card Security Code ..... (The last 3 digits on or just under the signature strip)

Expiry Date ..... Switch Issue No. ....

SEND TO: **Everyday Practical Electronics,  
Wimborne Publishing Ltd.,**

**408 Wimborne Road East, Ferndown, Dorset BH22 9ND.**

Tel: 01202 873872. Fax: 01202 874562.

E-mail: [orders@epemag.wimborne.co.uk](mailto:orders@epemag.wimborne.co.uk)

Payments must be by card or in £ Sterling – cheque or bank draft drawn on a UK bank.

Normally supplied within seven days of receipt of order.

Send a copy of this form, or order by letter if you do not wish to cut your issue.

# INTERFACE

## Robert Penfold



### MSCOMM VOLTAGE LEVELS, AND BATCH COUNTING

**C**ONTROL of and reading from the serial port handshake lines has been covered in recent *Interface* articles. The software side of things is reasonably straightforward using the MSCOMM ActiveX control, and interfacing circuits to the handshake lines is also reasonably simple.

The only slight complication in the hardware is the use of nominal signal voltages of  $\pm 12\text{V}$  for all RS232C lines including the handshake types. In most cases it is possible to drive RS232C inputs from ordinary 5V logic levels provided short cables of no more than two metres or so are used.

There is no guarantee that it will work reliably with all RS232C ports, but it always seems to. There is no risk of anything being damaged, so there is no harm in trying. If it fails to work, the port must be driven at the proper signal voltages via line drivers.

#### Stepping Down

Driving ordinary logic inputs from an RS232C output is a different matter. The signal voltages are nominally plus and minus 12V, but can be somewhat higher in practice. The output potentials do fall significantly under heavy loading, and the output current is limited to about 20mA. Even so, drive voltages well outside the limits for most logic chips are produced.

Stating that normal logic inputs should not be driven from serial port outputs will sometimes bring a response or two from readers who say they have tried it and it works. A few logic devices are designed to have compatibility with serial outputs as well as standard 5V logic types, and it is obviously all right to use these with RS232C ports.

Some logic chips might actually work when driven direct from a serial port, with their input protection circuits clipping the inputs at safe levels. However, relying on protection circuits to prevent a project from being zapped is not really an approach that can be recommended. The long-term reliability of such an arrangement is far from certain.

Although it might actually work with some chips, it will destroy others or cause them to malfunction. Trying to directly drive expensive chips would be foolhardy and probably costly as well. It is much better to use line receivers that provide the necessary voltage reductions.

There are special line receiver chips available, but a simple common emitter switching circuit such as the one shown in Fig.1 will usually suffice. It has to be borne in mind that there is an inversion through this circuit, and through any normal line driver and receiver circuits. This should not cause any major problems, and where necessary it is just a matter of writing the software to take the inversion into account.

The MAX202 chip is a good choice if line drivers are required. This chip operates from a single 5V supply from which it generates supplies of  $\pm 10\text{V}$  using a simple switching power supply.

As can be seen from the circuit of Fig.2, no inductors are required. The supplies

are generated using four capacitors and electronic switches in essentially the same arrangements used with the popular ICL7660 supply chip. Capacitors C2 to C5 must be high quality components such as tantalum types. Two line drivers are provided, together with two line receivers.

#### Count On It

One of the most common requests from readers used to be circuits for what is generally termed batch counting. In other words, a counter of the type that is used for counting products as they roll off the end of a production line. This type of thing has many other uses, such as lap counting for model racing cars and counting the number of pages produced by a printer. MSCOMM makes it easy to count transitions on the serial port handshake inputs, as it can generate an event on each one.

The difficult part of batch counting is finding a means of reliably detecting objects as they pass. Generating a basic signal is often quite straightforward, but spurious pulses tend to be a problem. These are more or less guaranteed to appear with simple mechanical sensing via a microswitch due to contact bounce. For one reason or another, spurious pulses often occur with other types of sensing such as optical and magnetic types. A grossly excessive count is produced unless these pulses are filtered out.

A monostable circuit is one of the most simple but effective methods of removing switching glitches. A simple "switch-debouncing" circuit, based on a 555 timer, is shown in Fig.3. A low-power version of the 555 is specified, but the circuit will work just as well with the standard device, albeit with a higher current consumption.

The circuit uses the timer chip (IC1) in the standard monostable mode, and it is triggered when switch S1 closes. In practice S1 is a microswitch that is activated by each object as it passes by.

The timing components are resistor R1 and capacitor C2. These set the pulse duration at just under 250 milliseconds, but other pulse times can be obtained by altering the value of capacitor C2. The pulse duration is proportional to the value of this component.

Spurious pulses might trigger the circuit and produce extra output pulses if the pulse duration is too short.

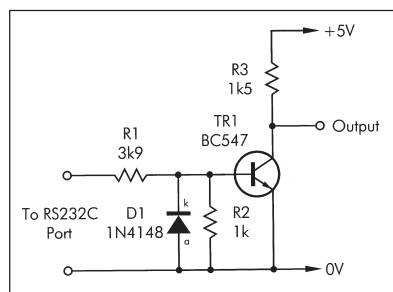


Fig.1. A simple but effective line receiver circuit.

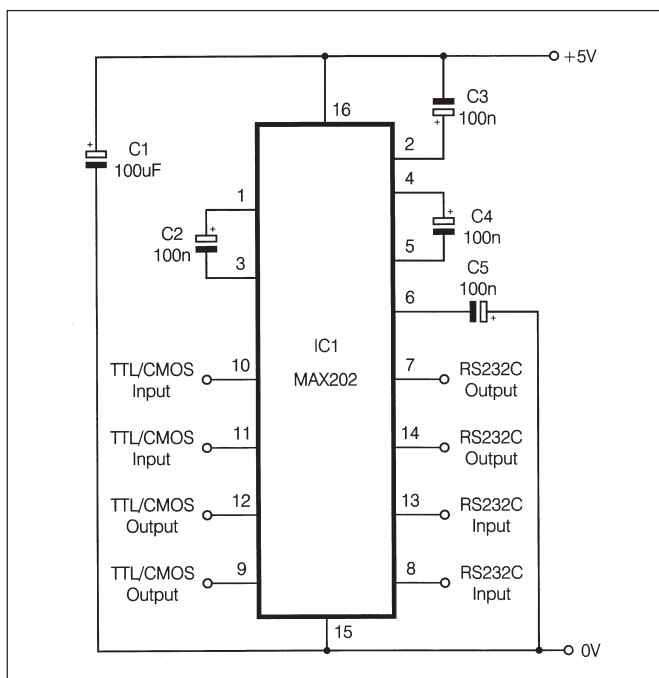


Fig.2. The Maxim MAX202 RS232 transceiver chip provides two proper line drivers and receivers.



Objects might slip though uncounted if the pulse duration is too long. It often requires some experimentation in order to find a suitable pulse length.

## Optical Count

Mechanical sensors are cheap and reliable but are not well suited to all applications. The usual alternative is some sort of optical sensor and Fig.4 shows a typical circuit diagram for a simple light sensor circuit; this is essentially the same circuit as Fig.3. As before, a monostable based on a 555 timer is used to remove any glitches and produce a "clean" output pulse.

The circuit is triggered by a potential divider circuit that has resistor R2 and preset potentiometer VR1 as the upper arm and the collector-to-emitter resistance of phototransistor TR1 as the lower arm. Under standby conditions the sensor is in relatively dark conditions and it therefore exhibits a high resistance.

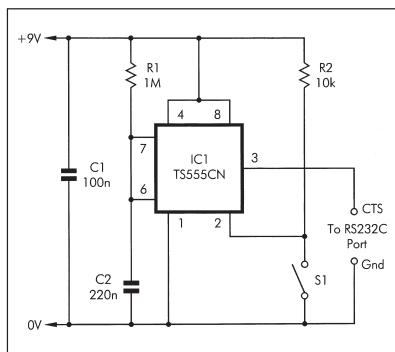


Fig.3. A monostable is a simple but effective means of switch debouncing.

Consequently, the voltage fed to pin 2 of IC1 is well above the trigger threshold, which is one third of the supply voltage. A suitably large increase in the light level received by TR1 results in a large fall in its collector-to-emitter resistance, and the voltage fed to pin 2 of IC1 then falls below the trigger level, instigating the output pulse at IC1 pin 3.

Preset VR1 enables the sensitivity of the circuit to be varied, with lower values giving higher light threshold levels. TR1 can be practically any phototransistor, and inexpensive types should be perfectly suitable. Note that Fig.4 correctly shows no connection to the base (b) terminal of TR1. The circuit will also work quite well using most light-dependent resistors (l.d.r.s), including the ORP12 and near equivalents.

## On Reflection

One way of using this type of sensor is to have a light source positioned next to

TR1 so that light is reflected from the counted objects and back onto TR1. This will only work properly if the objects being counted are suitably reflective. The alternative is to have the light source directed at TR1, with the objects blocking the light as they pass. With this second method the two arms of the potential divider circuit should be swapped, so that the voltage falls below the trigger level when TR1 is in dark conditions.

In some cases it will be possible to use the ambient light as the light source. In a lap counter for a model racetrack for example, TR1 could be mounted in the track and aimed upwards. The model car would then cast a shadow over TR1 each time it passed over it, and with preset VR1 at a suitable setting this should produce reliable triggering. A bit of trial and error will be needed in order to find a suitable setting for VR1, but there will

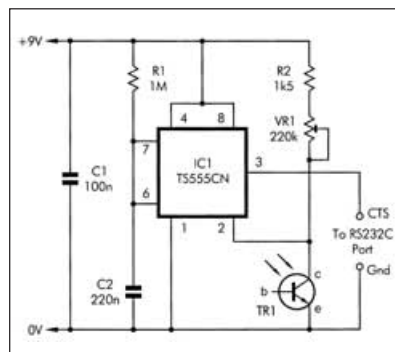


Fig.4. Circuit diagram for a light-activated sensor that includes a monostable to remove spurious pulses.

usually be a fairly wide range of acceptable settings.

## Software

An extremely simple program is all that is needed for lap/batch counting. The form is equipped with a label having a large font size, and this is used to display the count.

A command button labelled "RESET" is also, needed, and operating this will reset the count to zero. The MSCOMM ActiveX control must also be added to the form. The following simple routine is all that is needed to provide the counting action:

```
Dim counter As Variant
```

```
Private Sub Command1_Click()  
Label1.Caption = 0  
End Sub
```

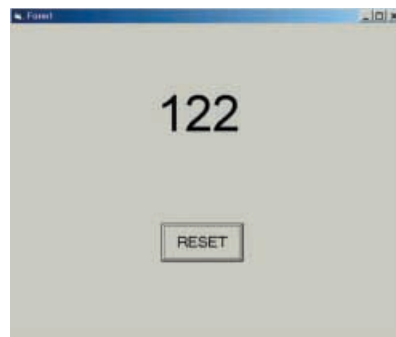


Fig.5. Screen shot of the batch counter program in operation.

```
Private Sub Form_Load()  
MSComm1.PortOpen = True  
End Sub
```

```
Private Sub MSComm1_OnComm()  
If (MSComm1.CommEvent =  
comEvCTS) Then  
counter = counter + 1  
Label1.Caption = counter \ 2  
End If  
End Sub
```

The first line of the program simply defines "counter" as a global variable. The routine for the form opens the serial port, and the routine for the MSCOMM control then waits for transitions on the CTS handshake input.

When a transition is detected, the value stored in "counter" is incremented by one. There is one pulse but two transitions per object, so the value in counter is divided by two before being transferred to the caption of the label.

Note that the division is provided by the backslash (\) character so that any decimals are stripped from the value. This means that the first transition is effectively ignored, and the displayed count is incremented by one on every second transition. This avoids having the counter briefly read "0.5", "1.5", "2.5", etc. The routine for the command button simply sets the caption at "0" when the button is left-clicked.

A high frequency on the CTS line seems to overload the program, causing erratic operation. It works well in batch counting and similar applications where the input frequency is very low, and will usually be just a fraction of one Hertz. Fig.5 shows an example of the program in operation.

Using a suitable interface it should be possible to use the handshake inputs in other low frequency counting applications, such as a heart rate monitor, which is something that will be covered next time.



## NEWSAGENTS ORDER FORM

Please reserve/deliver a copy of **Everyday Practical Electronics** for me each month

Signed .....

Name and Address .....

Post Code .....

**Everyday Practical Electronics** is published on the second Thursday of each month and distributed S.O.R. by COMAG. Make sure of your copy of **EPE** each month – cut out or photostat this form, fill it in and hand it to your newsagent.

# EPE IS PLEASED TO BE ABLE TO OFFER YOU THESE ELECTRONICS CD-ROMS


## ELECTRONICS PROJECTS



Logic Probe testing

*Electronic Projects* is split into two main sections: **Building Electronic Projects** contains comprehensive information about the components, tools and techniques used in developing projects from initial concept through to final circuit board production. Extensive use is made of video presentations showing soldering and construction techniques. The second section contains a set of ten projects for students to build, ranging from simple sensor circuits through to power amplifiers. A shareware version of Matrix's CADPACK schematic capture, circuit simulation and p.c.b. design software is included. The projects on the CD-ROM are: Logic Probe; Light, Heat and Moisture Sensor; NE555 Timer; Egg Timer; Dice Machine; Bike Alarm; Stereo Mixer; Power Amplifier; Sound Activated Switch; Reaction Tester. Full parts lists, schematics and p.c.b. layouts are included on the CD-ROM.

## ELECTRONICS CAD PACK

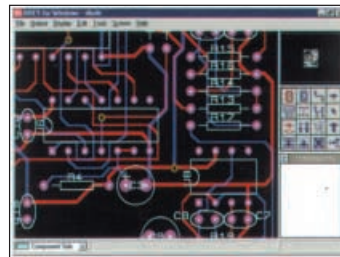

PCB Layout

Electronics CADPACK allows users to design complex circuit schematics, to view circuit animations using a unique SPICE-based simulation tool, and to design printed circuit boards. CADPACK is made up of three separate software modules. (These are restricted versions of the full Labcenter software.) **ISIS Lite** which provides full schematic drawing features including full control of drawing appearance, automatic wire routing, and over 6,000 parts. **PROSPICE Lite** (integrated into ISIS Lite) which uses unique animation to show the operation of any circuit with mouse-operated switches, pots, etc. The animation is compiled using a full mixed mode SPICE simulator. **ARES Lite** PCB layout software allows professional quality PCBs to be designed and includes advanced features such as 16-layer boards, SMT components, and an autorouter operating on user generated Net Lists.


## ELECTRONIC CIRCUITS & COMPONENTS V2.0



Circuit simulation screen

Provides an introduction to the principles and application of the most common types of electronic components and shows how they are used to form complete circuits. The virtual laboratories, worked examples and pre-designed circuits allow students to learn, experiment and check their understanding. Version 2 has been considerably expanded in almost every area following a review of major syllabuses (GCSE, GNVQ, A level and HNC). It also contains both European and American circuit symbols. Sections include: **Fundamentals**: units & multiples, electricity, electric circuits, alternating circuits. **Passive Components**: resistors, capacitors, inductors, transformers. **Semiconductors**: diodes, transistors, op.amps, logic gates. **Passive Circuits**. **Active Circuits**. The **Parts Gallery** will help students to recognise common electronic components and their corresponding symbols in circuit diagrams. Included in the Institutional Versions are multiple choice questions, exam style questions, fault finding virtual laboratories and investigations/worksheets.

## ANALOGUE ELECTRONICS

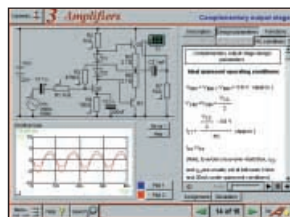

Complimentary output stage

*Analogue Electronics* is a complete learning resource for this most difficult branch of electronics. The CD-ROM includes a host of virtual laboratories, animations, diagrams, photographs and text as well as a SPICE electronic circuit simulator with over 50 pre-designed circuits. Sections on the CD-ROM include: **Fundamentals** – Analogue Signals (5 sections), Transistors (4 sections), Waveshaping Circuits (6 sections). **Op.Amps** – 17 sections covering everything from Symbols and Signal Connections to Differentiators. **Amplifiers** – Single Stage Amplifiers (8 sections), Multi-stage Amplifiers (3 sections). **Filters** – Passive Filters (10 sections), Phase Shifting Networks (4 sections), Active Filters (6 sections). **Oscillators** – 6 sections from Positive Feedback to Crystal Oscillators. **Systems** – 12 sections from Audio Pre-Amplifiers to 8-Bit ADC plus a gallery showing representative p.c.b. photos.

## ROBOTICS & MECHATRONICS




Case study of the Milford Instruments Spider

Robotics and Mechatronics is designed to enable hobbyists/students with little previous experience of electronics to design and build electromechanical systems. The CD-ROM deals with all aspects of robotics from the control systems used, the transducers available, motors/actuators and the circuits to drive them. Case study material (including the NASA Mars Rover, the Milford Spider and the Furby) is used to show how practical robotic systems are designed. The result is a highly stimulating resource that will make learning, and building robotics and mechatronic systems easier. The Institutional versions have additional worksheets and multiple choice questions.

- Interactive Virtual Laboratories
- Little previous knowledge required
- Mathematics is kept to a minimum and all calculations are explained
- Clear circuit simulations


## DIGITAL ELECTRONICS V2.0

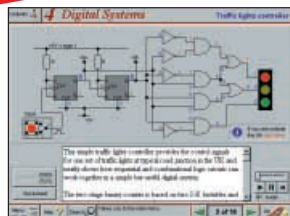

Virtual laboratory – Traffic Lights

*Digital Electronics* builds on the knowledge of logic gates covered in *Electronic Circuits & Components* (opposite), and takes users through the subject of digital electronics up to the operation and architecture of microprocessors. The virtual laboratories allow users to operate many circuits on screen. Covers binary and hexadecimal numbering systems, ASCII, basic logic gates, monostable action and circuits, and bistables – including JK and D-type flip-flops. Multiple gate circuits, equivalent logic functions and specialised logic functions. Introduces sequential logic including clocks and clock circuitry, counters, binary coded decimal and shift registers. A/D and D/A converters, traffic light controllers, memories and microprocessors – architecture, bus systems and their arithmetic logic units. Sections on Boolean Logic and Venn diagrams, displays and chip types have been expanded in Version 2 and new sections include shift registers, digital fault finding, programmable logic controllers, and microcontrollers and microprocessors. The Institutional versions now also include several types of assessment for supervisors, including worksheets, multiple choice tests, fault finding exercises and examination questions.

## FILTERS

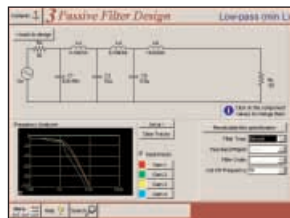

Filter synthesis

*Filters* is a complete course in designing active and passive filters that makes use of highly interactive virtual laboratories and simulations to explain how filters are designed. It is split into five chapters: **Revision** which provides underpinning knowledge required for those who need to design filters. **Filter Basics** which is a course in terminology and filter characterization, important classes of filter, filter order, filter impedance and impedance matching, and effects of different filter types. **Advanced Theory** which covers the use of filter tables, mathematics behind filter design, and an explanation of the design of active filters. **Passive Filter Design** which includes an expert system and filter synthesis tool for the design of low-pass, high-pass, band-pass, and band-stop Bessel, Butterworth and Chebyshev ladder filters. **Active Filter Design** which includes an expert system and filter synthesis tool for the design of low-pass, high-pass, band-pass, and band-stop Bessel, Butterworth and Chebyshev op.amp filters.

## PRICES

Prices for each of the CD-ROMs above are:

(Order form on third page)

(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

Hobbyist/Student .....	£45 inc VAT
Institutional (Schools/HE/FE/Industry).....	£99 plus VAT
Institutional 10 user (Network Licence) .....	£199 plus VAT
Site Licence.....	£499 plus VAT



# PICmicro TUTORIALS AND PROGRAMMING


## HARDWARE

### VERSION 2 PICmicro MCU DEVELOPMENT BOARD

*Suitable for use with the three software packages listed below.*

This flexible development board allows students to learn both how to program PICmicro microcontrollers as well as program a range of 8, 18, 28 and 40-pin devices. For experienced programmers all programming software is included in the PPP utility that comes with the development board. For those who want to learn, choose one or all of the packages below to use with the Development Board.

- Makes it easier to develop PICmicro projects
- Supports low cost Flash-programmable PICmicro devices
- Fully featured integrated displays – 13 individual I.e.d.s, quad 7-segment display and alphanumeric I.c.d. display
- Supports PICmicro microcontrollers with A/D converters
- Fully protected expansion bus for project work
- All inputs and outputs available on screw terminal connectors for easy connection

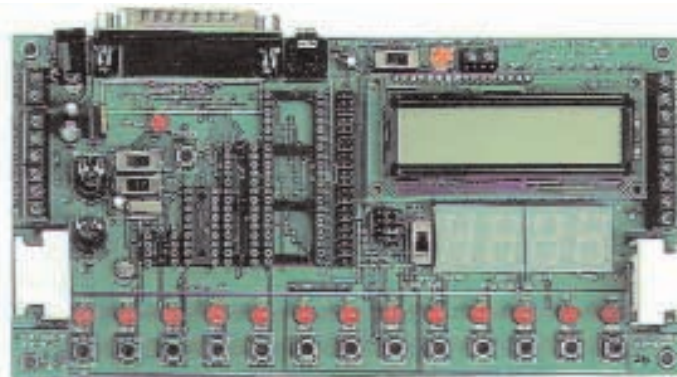

**£145 including VAT and postage**

**12V 500mA plug-top PSU (UK plug) £7**

**25-way 'D' type connecting cable £5**

## SOFTWARE

*Suitable for use with the Development Board shown above.*

### ASSEMBLY FOR PICmicro V2 (Formerly PICtutor)

Assembly for PICmicro microcontrollers V2.0 (previously known as PICtutor) by John Becker contains a complete course in programming the PIC16F84 PICmicro microcontroller from Arizona Microchip. It starts with fundamental concepts and extends up to complex programs including watchdog timers, interrupts and sleep modes. The CD makes use of the latest simulation techniques which provide a superb tool for learning: the Virtual PICmicro microcontroller. This is a simulation tool that allows users to write and execute MPASM assembler code for the PIC16F84 microcontroller on-screen. Using this you can actually see what happens inside the PICmicro MCU as each instruction is executed which enhances understanding.

- Comprehensive instruction through 39 tutorial sections
- Includes Vlab, a Virtual PICmicro microcontroller: a fully functioning simulator
- Tests, exercises and projects covering a wide range of PICmicro MCU applications
- Includes MPLAB assembler
- Visual representation of a PICmicro showing architecture and functions
- Expert system for code entry helps first time users
- Shows data flow and fetch execute cycle and has challenges (washing machine, lift, crossroads etc.)
- Imports MPASM files.




Virtual PICmicro

### 'C' FOR PICmicro VERSION 2

The C for PICmicro microcontrollers CD-ROM is designed for students and professionals who need to learn how to program embedded microcontrollers in C. The CD contains a course as well as all the software tools needed to create Hex code for a wide range of PICmicro devices – including a full C compiler for a wide range of PICmicro devices.

Although the course focuses on the use of the PICmicro microcontrollers, this CD-ROM will provide a good grounding in C programming for any microcontroller.

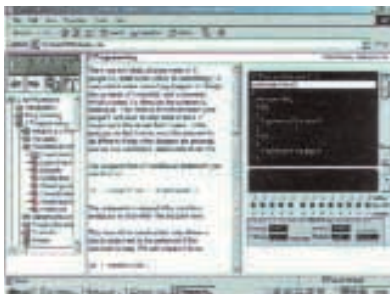- Complete course in C as well as C programming for PICmicro microcontrollers
- Highly interactive course
- Virtual C PICmicro improves understanding
- Includes a C compiler for a wide range of PICmicro devices
- Includes full Integrated Development Environment
- Includes MPLAB software
- Compatible with most PICmicro programmers
- Includes a compiler for all the PICmicro devices.



Minimum system requirements for these items: Pentium PC running Windows 98, NT, 2000, ME, XP; CD-ROM drive; 64MB RAM; 10MB hard disk space.

### FLOWCODE FOR PICmicro

Flowcode is a very high level language programming system for PICmicro microcontrollers based on flowcharts. Flowcode allows you to design and simulate complex robotics and control systems in a matter of minutes.

Flowcode is a powerful language that uses macros to facilitate the control of complex devices like 7-segment displays, motor controllers and I.c.d. displays. The use of macros allows you to control these electronic devices without getting bogged down in understanding the programming involved.

Flowcode produces MPASM code which is compatible with virtually all PICmicro programmers. When used in conjunction with the Version 2 development board this provides a seamless solution that allows you to program chips in minutes.

- Requires no programming experience
- Allows complex PICmicro applications to be designed quickly
- Uses international standard flow chart symbols (ISO5807)
- Full on-screen simulation allows debugging and speeds up the development process
- Facilitates learning via a full suite of demonstration tutorials
- Produces ASM code for a range of 8, 18, 28 and 40-pin devices
- Institutional versions include virtual systems (burglar alarms, car parks etc.).



Burglar Alarm Simulation

## PRICES

**Prices for each of the CD-ROMs above are:**

*(Order form on next page)*

*(UK and EU customers add VAT at 17.5% to "plus VAT" prices)*

Hobbyist/Student  
Institutional (Schools/HE/FE/Industry)  
Flowcode Institutional  
Institutional 10 user (Network Licence)  
Site Licence

£45 inc VAT  
£99 plus VAT  
£70 plus VAT  
£249 plus VAT  
£599 plus VAT



## TEACH-IN 2000 – LEARN ELECTRONICS WITH EPE


EPE's own *Teach-In* CD-ROM, contains the full 12-part *Teach-In* series by John Becker in PDF form plus the *Teach-In* interactive software covering all aspects of the series. We have also added Alan Winstanley's highly acclaimed *Basic Soldering Guide* which is fully illustrated and which also includes *Desoldering*. The *Teach-In* series covers: Colour Codes and Resistors, Capacitors, Potentiometers, Sensor Resistors, Ohm's Law, Diodes and L.E.D.s, Waveforms, Frequency and Time, Logic Gates, Binary and Hex Logic, Op.amps, Comparators, Mixers, Audio and Sensor Amplifiers, Transistors, Transformers and Rectifiers, Voltage Regulation, Integration, Differentiation, 7-segment Displays, L.C.D.s, Digital-to-Analogue.

Each part has an associated practical section and the series includes a simple PC interface so you can use your PC as a basic oscilloscope with the various circuits.

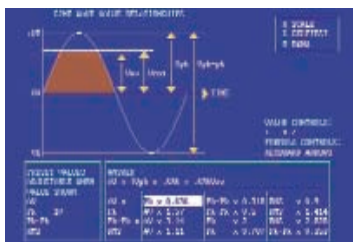**A hands-on approach to electronics with numerous breadboard circuits to try out.**


**£12.45 including VAT and postage.** Requires Adobe Acrobat (available free from the Internet – [www.adobe.com/acrobat](http://www.adobe.com/acrobat)).

**FREE WITH EACH TEACH-IN CD-ROM** – *Electronics Hobbyist Compendium* 80-page book by Robert Penfold. Covers Tools For The Job; Component Testing; Oscilloscope Basics.




Sine wave relationship values

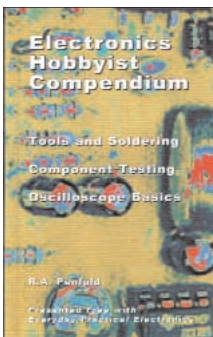**FREE BOOK  
WITH TEACH-IN  
2000 CD-ROM**



## DIGITAL WORKS 3.0

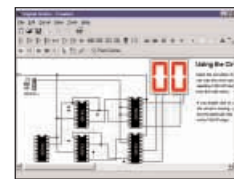

Counter project

*Digital Works Version 3.0* is a graphical design tool that enables you to construct digital logic circuits and analyze their behaviour. It is so simple to use that it will take you less than 10 minutes to make your first digital design. It is so powerful that you will never outgrow its capability. ● Software for simulating digital logic circuits ● Create your own macros – highly scalable ● Create your own circuits, components, and i.c.s ● Easy-to-use digital interface ● Animation brings circuits to life ● Vast library of logic macros and 74 series i.c.s with data sheets ● Powerful tool for designing and learning.

**Hobbyist/Student £45 inc. VAT.**  
**Institutional £99 plus VAT.**  
**Student 10 user £199 plus VAT.**  
**Site Licence £499 plus VAT.**

## ELECTRONICS IN CONTROL

Two colourful animated courses for students on one CD-ROM. These cover Key Stage 3 and GCSE syllabuses. **Key Stage 3:** A pictorial look at the Electronics section featuring animations and video clips. Provides an ideal introduction or revision guide, including multi-choice questions with feedback. **GCSE:** Aimed at the Electronics in many Design & Technology courses, it covers many sections of GCSE Electronics. Provides an ideal revision guide with Homework Questions on each chapter. Worked answers with an access code are provided on a special website.

**Single User £29 inc. VAT. Multiple User £39 plus VAT**

**Student copies (available only with a multiple user copy) £6 plus VAT**  
(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

## MODULAR CIRCUIT DESIGN

Contains a range of tried and tested analogue and digital circuit modules, together with the knowledge to use and interface them. Thus allowing anyone with a basic understanding of circuit symbols to design and build their own projects. Version 3 includes data and circuit modules for a range of popular PICs; includes PICAXE circuits, the system which enables a PIC to be programmed without a programmer, and without removing it from the circuit. Shows where to obtain free software downloads to enable BASIC programming. Essential information for anyone undertaking GCSE or "A" level electronics or technology and for hobbyists who want to get to grips with project design. Over seventy different Input, Processor and Output modules are illustrated and fully described, together with detailed information on construction, fault finding and components, including circuit symbols, pinouts, power supplies, decoupling etc.

**Single User £19.95 inc. VAT. Multiple User £34 plus VAT**  
(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

**VERSION 3**

Minimum system requirements for these CD-ROMs: Pentium PC, CD-ROM drive, 32MB RAM, 10MB hard disk space. Windows 95/98/NT/2000/ME/XP, mouse, sound card, web browser.

Please send me:

## CD-ROM ORDER FORM

- ☐ Electronic Projects  
☐ Electronic Circuits & Components V2.0  
☐ Analogue Electronics  
☐ Digital Electronics V2.0  
☐ Filters  
☐ Electronics CAD Pack  
☐ Robotics & Mechatronics  
☐ Assembler for PICmicro  
☐ 'C' for PICmicro  
☐ Flowcode for PICmicro  
☐ Digital Works 3.0

Version required:

- ☐ Hobbyist/Student  
☐ Institutional  
☐ Institutional 10 user  
☐ Site licence



- ☐ PICmicro Development Board (hardware)  
☐ Development Board UK plugtop power supply  
☐ Development Board 25-way connecting lead

- ☐ Teach-In 2000 + FREE BOOK  
☐ Electronic Components Photos  
☐ Electronics In Control – Single User  
☐ Electronics In Control – Multiple User  
☐ Modular Circuit Design – Single User  
☐ Modular Circuit Design – Multiple User

**Note:** The software on each version is the same, only the licence for use varies.

Full name: .....

Address: .....

Post code: ..... Tel. No: .....

Signature: .....

☐ I enclose cheque/PO in £ sterling payable to WIMBORNE PUBLISHING LTD for £ .....

☐ Please charge my Visa/Mastercard/Amex/Diners Club/Switch: £ ..... Card expiry date: .....

Card No: ..... Switch Issue No: .....

Card Security Code ..... (The last 3 digits on or just under the signature strip)

## ORDERING

**ALL PRICES INCLUDE UK POSTAGE**

**Student/Single User/Standard Version**  
price includes postage to most countries in the world  
**EU residents outside the UK add £5 for airmail postage per order**

**Institutional, Multiple User and Deluxe Versions** – overseas readers add £5 to the basic price of each order for airmail postage (do not add VAT unless you live in an EU (European Union) country, then add 17½% VAT or provide your official VAT registration number).

Send your order to:

**Direct Book Service  
Wimborne Publishing Ltd  
408 Wimborne Road East  
Ferndown, Dorset BH22 9ND**

To order by phone ring

**01202 873872. Fax: 01202 874562**

Goods are normally sent within seven days


E-mail: [orders@wimborne.co.uk](mailto:orders@wimborne.co.uk)

Online shop:

[www.epemag.wimborne.co.uk/shopdoor.htm](http://www.epemag.wimborne.co.uk/shopdoor.htm)

- 100MS/s Dual Channel Storage Oscilloscope
- 50MHz Spectrum Analyser
- Multimeter ● Frequency Meter
- Signal Generator

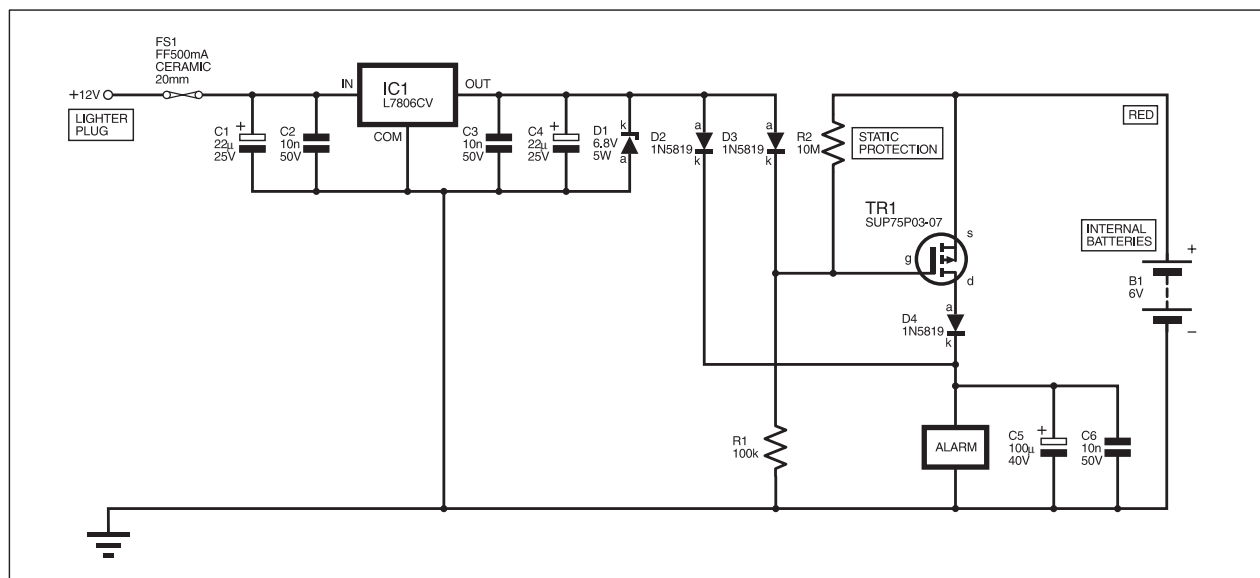If you have a novel circuit idea which would be of use to other readers then a Pico Technology PC based oscilloscope could be yours. Every 12 months, Pico Technology will be awarding an ADC200-100 digital storage oscilloscope for the best IU submission. In addition, a DrDAQ Data Logger/Scope worth £69 will be presented to the runner up.



423

# PICRONOS L.E.D. WALL CLOCK



JOHN BECKER Part One

*Ancient and modern techniques display timely brilliance on a grand scale!*

**P**ORTUGUESE reader Fernando Bentes de Jesus emailed us during the Autumn of 2002, saying that his favourite electronically-controlled wall clock had “ticked its last tock” and that it could not be revived. He asked if we knew of anyone who might be interested to design a replacement.

Questioning him further, he explained that in essence his “dream clock” consisted of 60 light emitting diodes, arranged in a circle having a diameter of 24 centimetres, and displayed the seconds count. In the centre were eight digits with each segment comprised of several l.e.d.s. These displayed hours, minutes and calendar information.

Thinking about the possibility of designing a clock along these lines, the author became


intrigued by the thought of designing one that embraced both old and new technologies – old in the form of l.e.d.s for the display rather than a liquid crystal screen, and new in the form of a PIC microcontroller (inevitably!).

Making some sketches, he ended up designing the circuit and printed circuit board for one over a weekend! With refinements, and after further discussions with Fernando, plus a lot of programming time, the clock presented here is that same one. Its achievement turned out to be a real exercise in multiplexing.

Whilst the design is not exactly the same as Fernando’s ideal, which also included some peripheral features, it very much sticks to a similar concept. It has the features shown in Panel 1.
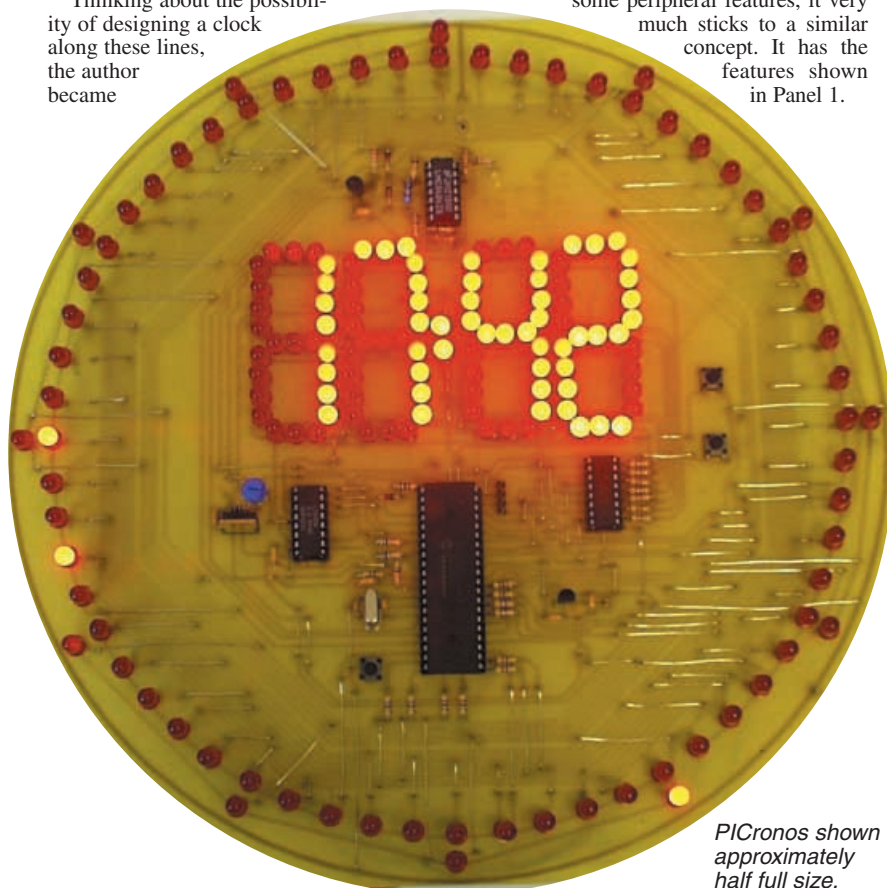
## PANEL 1 FEATURES

- Crystal controlled
- Circular display having diameter of 9.8 inches (250mm)
- Inner ring of 60 l.e.d.s displaying both seconds and minutes
- Outer ring of 12 l.e.d.s displaying hours in conventional (analogue) 12-hour format
- Inner zone of 100 l.e.d.s in 4-digit 7-segment numerical format, cyclically displaying hours (24-hour format) and minutes, months and days of month, and temperature in degrees Celsius to one decimal place
- Three switches provide adjustment for all display values, and for the precise calibration of the timing accuracy to compensate for normal manufacturing tolerance in the controlling crystal’s oscillating rate
- Powered at 9V to 12V d.c. via a mains supply adaptor, with battery back-up
- Current consumption only 65mA (thanks to heavy multiplexing of l.e.d.s)
- Adjustable brilliance of the l.e.d. numerals to suit personal taste



PICRONOS shown approximately half full size.

## MATRIXED ARRAYS

The use of multiplexing in this design was essential, to cut down on the current consumption and the number of logic gate devices that would otherwise have been required. Additionally, heavy use is made of matrixed arrays. The most significant example of this is in the circle of 60 l.e.d.s., whose array structure is shown in Fig.1.

In this matrix, applying positive power (e.g. +5V) to one of the eight horizontal connections (numbered 9 to 16) allows current to flow through any of the l.e.d.s in that row if its cathode (k) is taken low (e.g. to 0V) via a suitable ballast resistor. The cathodes are also mutually connected in groups of eight columns (numbered 1 to 8). By selecting which row and column are activated, any one (or more) of the l.e.d.s can be turned on.

For instance, applying power between connections 9 and 1 will cause current to flow through the top left l.e.d., D1. So that none of the other l.e.d.s in the other rows are turned on, their anode row connections are held at 0V. Similarly, to prevent other l.e.d.s in a column being turned on, their cathode connections are held positive.



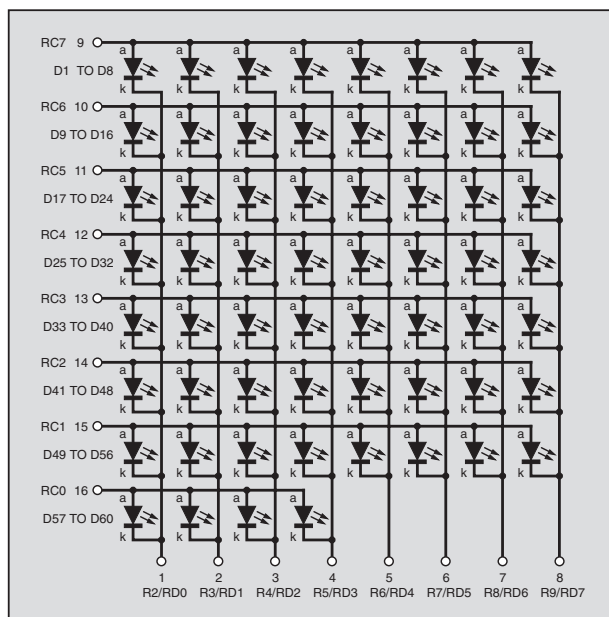


Fig.1. Matrixed array for the l.e.d.s that display minutes and seconds.

In theory, eight rows and eight columns can control 64 l.e.d.s. In this clock, though, only 60 l.e.d.s need to be controlled. Thus the last four positions of the matrix are left unused.

The other notations alongside each row and column (e.g. RC7 and R2/RD0) refer to the control points as shown later in Fig.5.

Multiplex control is used on this matrix. The 60 l.e.d.s are jointly used to show not only a seconds count but also a minutes count. This is achieved by first selecting the matrix co-ordinates for the seconds, turning on the required l.e.d. for a brief period, and then selecting the matrix co-ordinates for the minutes, and turning on that required l.e.d. for the same period. The alternating between the two matrix selections is so fast (around 400Hz) that both l.e.d.s appear to be on at the same time.

A second matrix is used for the l.e.d.s of the analogue hours display, as shown in Fig.2. Seven lines basically control this matrix, although it too is multiplexed by the control source, in conjunction with the 7-segment digits, i.e. as part of a 5-way multiplex switching format.

cathodes of the like-lettered segments of all four digits are connected together (e.g. A to A, B to B). The seven connection paths control current sinking from the segments.

As with the matrix displays, any digit and any of its segments can be turned on as required, in this case using 11 control lines (four source plus seven sink). Again multiplexing is used in the control sequence so that each digit appears to be active simultaneously.

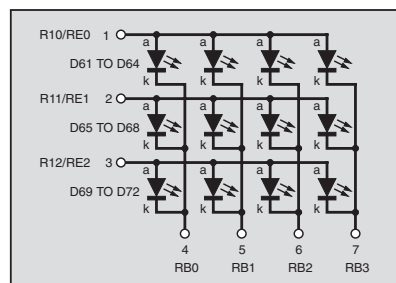


Fig.2. L.E.D. matrix for hours.

The basic l.e.d. format of a 7-segment digit is shown in Fig.3, and matrix diagram in Fig.4. Each of the four digits is identically arranged. Three l.e.d.s are connected in series for each of the horizontal segments (segment letters A, G and D), and four l.e.d.s are in series for each of the vertical segments (F, B, E and C). Different values of ballast resistor (R13 to R19) are used for the vertical and horizontal segments to achieve equal brilliance.

All four digits are multiplexed. There are four current source connections, each made to the primary anodes of all seven segments in one digit. The final

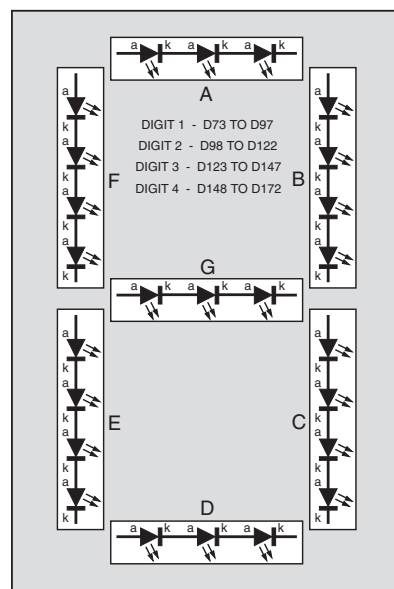


Fig.3. Basic format of a 7-segment digit.

## CONTROL CIRCUIT

The control circuit diagram is shown in Fig.5. A PIC16F877 microcontroller, IC1, is the principal component, routing the many multiplex and matrix voltages as required. The PIC is operated at 3.2768MHz, as set by crystal X1.

The circuit should be read in conjunction with the previous illustrations. For example, the matrix display for the minutes and seconds l.e.d.s D1 to D60 that is shown in Fig.1 is represented by the block diagram connected to PIC pins RD0 to RD7 (Port D) and RC0 to RC7 (Port C). Port C provides the current source for the matrix rows, and Port D sinks the current from the matrix columns, via ballast resistors R2 to R9.

Port E is primarily used to provide the power source, via ballast resistors R10 to R12, for the hours matrix in Fig.2. The connection to switch S3 at resistor R11 is discussed later, as are the functions of switches S1 and S2.

The function of Port B is two-fold. In its first role, via pins RB0 to RB3, it provides current sinking from the hours matrix fed from Port E. Secondly it controls the gating of the digital display segments via IC4.

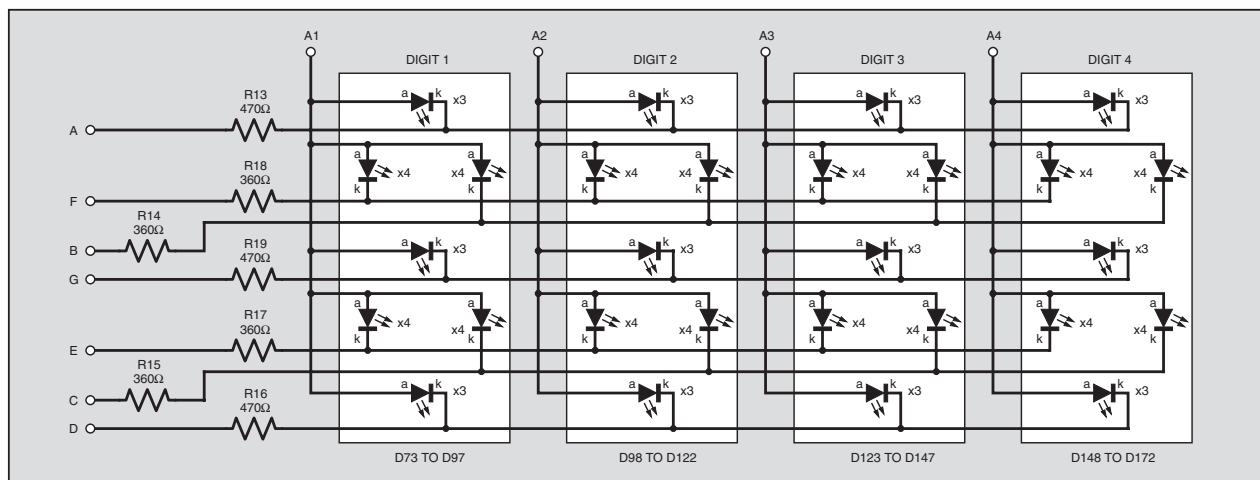


Fig.4. Interconnections between the four 7-segment digits. The x3 and x4 notations indicate the number of l.e.d.s in a segment.

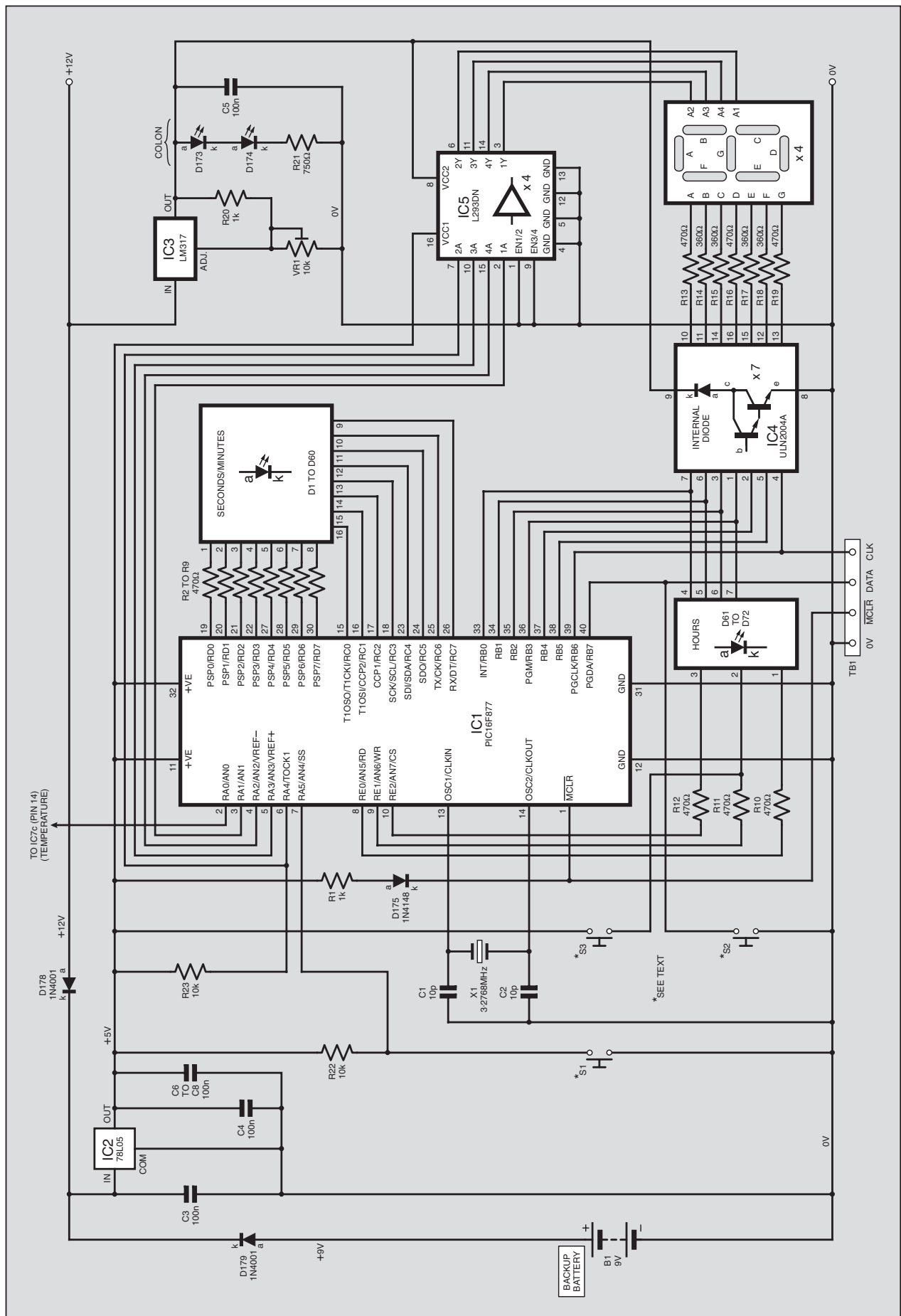


Fig.5. Main control circuit for the PICronos L.E.D. Wall Clock.





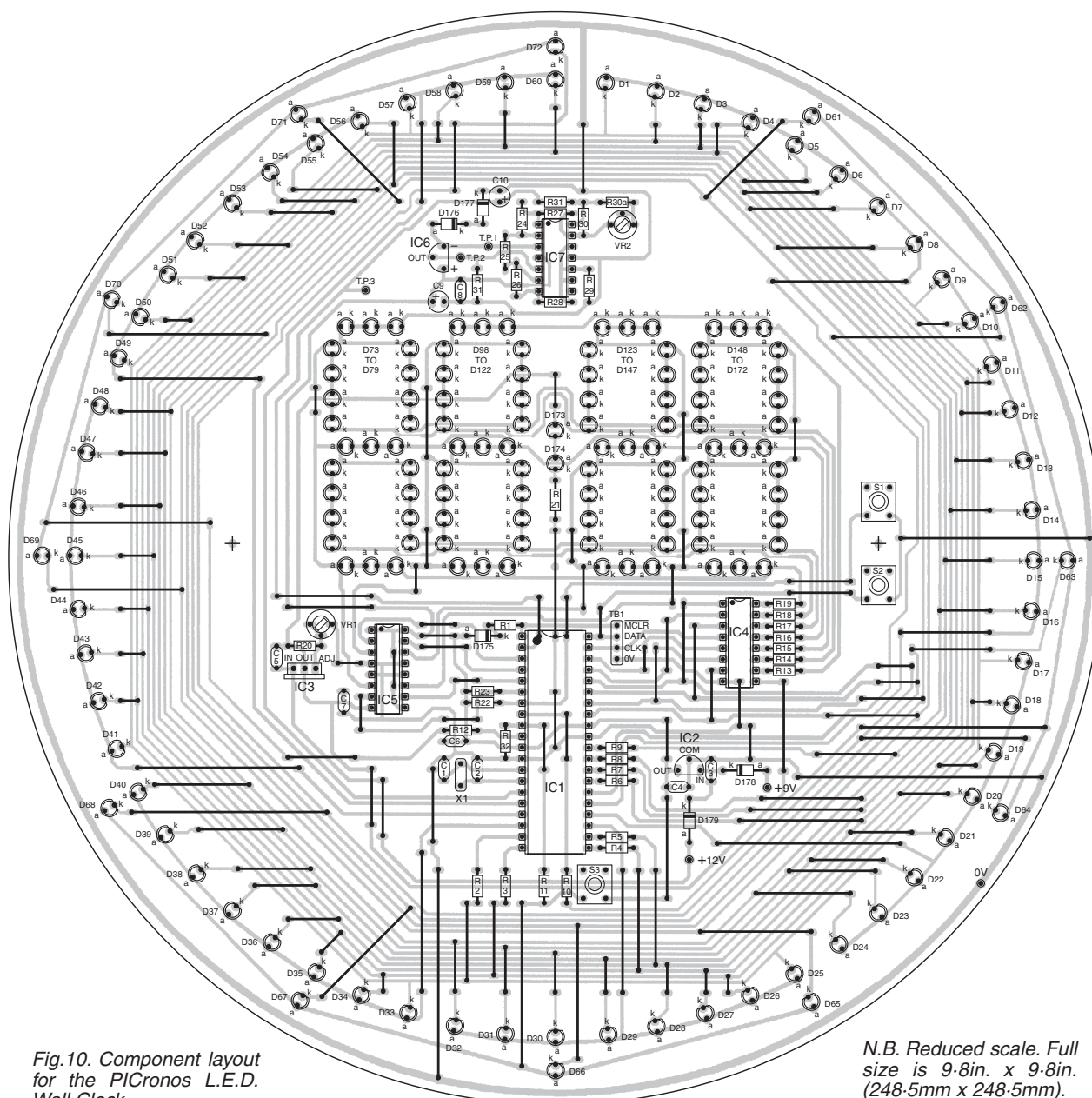


Fig.10. Component layout for the PICronos L.E.D. Wall Clock

N.B. Reduced scale. Full size is 9.8in. x 9.8in. (248.5mm x 248.5mm).

## COMPONENTS

### Resistors

R1, R20 1k (2 off)  
R2 to R13, R16, R19 470Ω (14 off)

R14, R15, R17, R18 360Ω (4 off)  
R21 750Ω  
R22, R23, R32 10k (3 off)  
R24 to R28 10k 1% 0.25W (5 off)  
R29, R30 33k 1% 0.25W (2 off)  
R30a 22k (see text)  
R31 18k

All 0.25W 5% except where stated.

### Potentiometer

VR1 10k min. round preset  
VR2 22k (or 25k) min. round preset (see text)

See  
**SHOP  
TALK**  
page

### Capacitors

C1, C2 10p disc ceramic, 0.5mm pitch (2 off)  
C3 to C8 100n disc ceramic, 0.5mm pitch (6 off)  
C9, C10 22μ radial elect. 10V (2 off)

### Semiconductors

D1 to D60, D73 to D174 red l.e.d., 5mm dia. ultrabright (162 off)  
D61 to D72 red l.e.d., 5mm dia, ultrabright (see text) (12 off)  
D175 to D179 1N4148 signal diode (5 off)  
D178, D179 1N4001 rectifier diode (2 off)  
IC1 PIC16F877-4 microcontroller, pre-programmed (see text)  
IC2 78L05 +5V 100mA voltage regulator  
IC3 LM317 adjustable voltage regulator

IC4 ULN2004A 7-way Darlington line driver  
IC5 L293DN 16-pin Half-H driver  
IC6 LM35CZ temperature sensor  
IC7 LMC6484 quad op.amp, rail-to-rail



### Miscellaneous

S1 to S3 min. push-to-make switch, p.c.b. mounting (3 off)  
TB1 1mm pin-header, 4-way (optional)

Printed circuit board, available from the EPE PCB Service, code 395; 22s.w.g. tinned copper wire, solid (for link wires); 14-pin d.i.l. socket; 16-pin d.i.l. socket (2 off); 40-pin d.i.l. socket; 1mm terminal pins or pin headers; connecting wire; solder, etc.

Approx. Cost  
Guidance Only

**£45**  
excl. batts

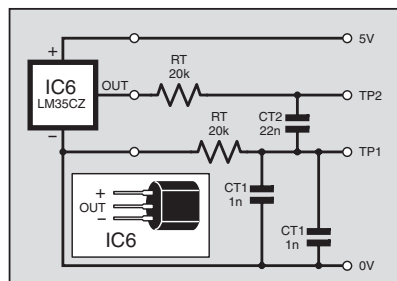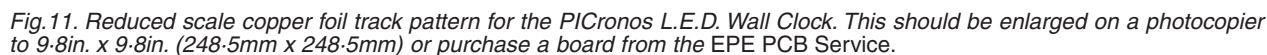

taxing in construction as inserting link wires.

Make the link wire connections first, especially noting that some go under d.i.l. (dual-in-line) i.c. positions. The links are best made using solid tinned copper wire of 24 s.w.g. (a roll of which should be part of anyone's toolkit).

Next insert all the d.i.l. i.c. sockets. Do not insert the i.c.s themselves, or the temperature sensor, until the board has been fully checked for poor soldering, incorrect component positioning, and the correctness of the power supply has been determined. Regulator IC3 can be mounted with its back against the board to keep the board's profile low.

Next insert the resistors, diodes (but not l.e.d.s), capacitors and voltage regulators in order of ascending size. Ensure the correct orientation of the semiconductors and electrolytic capacitors.

Finally, insert the l.e.d.s. Note that those in the two "rings" all have their cathodes (k) pointing towards the centre. Those in the horizontal segments all have their cathodes to the right, while the cathodes of those in the vertical segments all face downwards.

To assist in the best alignment of the l.e.d.s, initially just solder one leg of each so that it is easier to re-position a misplaced one by having to unsolder only one

lead. The l.e.d.s will have small spigots close to the body end of each lead, allowing their insertion depth to be maintained consistently.

Those who have good quality printed circuit board assembly frames with clip-on foam "lids" will find the entire p.c.b. assembly far easier than those who do not. The author's frame accepts p.c.b.s of 10in x 18in (254mm x 457mm) and the PICronos board was designed to just fit it.

It may be of interest to know that the author has used this frame for over 20 years and it considerably assists in the assembly of all the boards he designs.

It is strongly recommended that if you do not have an assembly frame, you should buy one. But only get a good quality one – those at the cheaper end of the selection may prove more trouble than they are worth, as the author once found to his detriment. Those in the professional class are the best.

Using this frame, assembly of the PICronos board took around four hours.

The author did not provide the clock with an enclosure and no recommendation for using one is offered.

### SOFTWARE

The software for the clock is available on a 3.5in disk (Disk 6) from the *EPE* Editorial office (a small handling charge

applies), or as a *free* download from the *EPE* ftp site. The easiest way into the latter is via the main *EPE* website page at [www.epemag.wimborne.co.uk](http://www.epemag.wimborne.co.uk) and click on the ftp site link at the top. Then click on down through folders PUB, PICS and then into the PICronos folder.

There are two files – ASM (source code in TASM grammar) and HEX (in standard MPASM format). The HEX file is the code file to be sent directly to the PIC via a suitable programmer (e.g. *TK3*). It contains embodied configuration and data EEPROM values.

For those whose programmers cannot handle embedded data, the configuration values must be set separately. The values are XT crystal, WDT off, POR on. All other factors should be off. Data EEPROM values can be set by switches during clock adjustment and calibration, as discussed next month. Note that unexpected display results may occur until the values have been set.

Pre-programmed PICs can also be purchased – for details of this and on obtaining the software disk, read this month's *Shoptalk* page.

### NEXT MONTH

In the final part next month, the clock's software and setting-up are discussed.

# Radio Bygones

## The leading magazine for vintage radio enthusiasts



Now Also  
Available To  
**BUY ONLINE**

[www.radiobygones.com](http://www.radiobygones.com)  
Log on, pay by credit card  
and download the magazine  
to your PC  
**ONLY \$9.99 (US dollars)**  
**FOR 6 ISSUES**  
A free issue is  
available

WHETHER your interest is in restoring domestic radio and TV or in amateur radio, in military, aeronautical or marine communications, in radar and radio navigation, in instruments, in broadcasting, in audio and recording, or in professional radio systems fixed or mobile, RADIO BYGONES is the magazine for you.

ARTICLES on restoration and repair, history, circuit techniques, personalities, reminiscences and just plain nostalgia – you'll find them all. Plus features on museums and private collections and a full-colour photo-feature in every issue.

IT'S MOSTLY about valves, of course, but 'solid-state' – whether of the coherer and spark-gap variety or early transistors – also has a place.

FROM THE DAYS of Maxwell, Hertz, Lodge and Marconi to what was the state-of-the-art just a few short years ago... There is also a selection of free readers' For Sale and Wanted advertisements in every issue.

## Radio Bygones covers it all!

THE MAGAZINE is published six times a year, and is available by postal subscription. **It is not available at newsagents.**

TO TAKE OUT a subscription, or to request a sample copy, please contact:

**RADIO BYGONES, Wimborne Publishing Ltd, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND.**

Tel: 01202 873872. Fax 01202 874562. Web sites: [www.radiobygones.co.uk](http://www.radiobygones.co.uk)

[www.radiobygones.com](http://www.radiobygones.com)



# READOUT

Email: [john.becker@epemag.wimborne.co.uk](mailto:john.becker@epemag.wimborne.co.uk)

**John Becker addresses some of the general points readers have raised. Have you anything interesting to say? Drop us a line!**

All letters quoted here have previously been replied to directly.

## WIN A DIGITAL MULTIMETER

A 3½ digit pocket-sized I.C.D. multimeter which measures a.c. and d.c. voltage, d.c. current and resistance. It can also test diodes and bipolar transistors.

Every month we will give a Digital Multimeter to the author of the best Readout letter.



## ★ LETTER OF THE MONTH ★

Dear EPE,

Thanks again for some really great articles and projects. The *Earth Resistivity Logger* (Apr/May '03) has some really great potential and is certainly timely, given all the attention archaeology is given across our country. It is these kinds of projects that stimulate ideas across disciplines and in my humble opinion, help us as a collective whole move to the next big idea.

I've been thinking of how I could use the unit for more than one thing, and I came across an idea that might work. I wonder if it could be adapted to use with a seismograph ([www.njsas.org/projects/tidal\\_forces/magnetic\\_gravimeter/baker/](http://www.njsas.org/projects/tidal_forces/magnetic_gravimeter/baker/)), as I think that along with the ground waves common with earthquakes a possible resistivity change caused by micro movement of the surrounding earth structure may also occur.

What I find is a need for a simple serial port datalogger that will collect and display  $\pm 5.0V$  d.c. changes in voltage levels collected by my existing seismograph and associated ADC, plus output from the ER unit. I currently use a small test software application from Iguana Labs ([www.iguanalabs.com/adc2051.htm](http://www.iguanalabs.com/adc2051.htm)), and it works ok for a single input, but if a way could be found to develop a simple serial port datalogger to use inputs from both the ER system and the seismo, and then generate a comparison chart, it could be interesting and a logical extension of the ER idea.

Do you think there be any value in a simple serial port reader application capable of

simultaneously reading, comparing, and displaying data inputs on COM1 and COM2?

I like the projects in *EPE*. I've been working on mixing and matching a couple of project circuits – nothing unique – and imagining other possible uses for things I'm doing with your circuits. Thanks for the wonderful work you are doing; lots of folks look at your magazine but not all write or acknowledge.

**Dave Mynatt,  
Manchaca, Texas, USA**

*Nice to hear from you again Dave. Let us know when you find anything interesting!*

*Regarding seismo – yes, I have in mind to do a solid-state one at some time (I did a mechanical unit many years back). It would use data logging techniques along the lines of ER. But I do not know if it would be of use to archaeologists to have seismic conditions recorded at the same time. In the UK it is rare for us to be knowingly shaken (or stirred!). The aim of my ER is to show relative differences in sub-surface conditions, not their absolute values.*

*Twin serial input via COM1 and COM2 – it seems that multiplexing data into one serial port will be just as good. In fact on my forthcoming Weather Centre, I'm multiplexing nine data sources into one output. Another good reason for not using two COMs ports is that many PCs are now being produced with only COM1, with USB as the second option.*

### PATting ER

Dear EPE,

*Earth Resistivity Logger* (Apr/May '03) – a brilliant project, I've been playing in this area of surveying for years but never with this level of sophistication!

Project built and running exactly as described. Multiple pats on the back all round!

**Barry Benson, via email**

*Thank you Barry, that's great news! I am really pleased to hear it. A lot of effort and field work has gone into producing ER. All the best – tell us when you find the next long-lost Roman city!*

### INDUCTIVE SURVEYING

Dear EPE,

Maybe the *Earth Resistivity Logger* could be combined with an Induced Polarization (IP) instrument. I believe that IP uses the same ground probes but inject a current at several different frequencies. The signal is ON+, OFF, ON-, OFF, over the timed period. When the signal is shut off IP instruments read the voltage while it is decaying. The measurements are of time domain and also frequency domain. Interfacing ER to a GPS handset would also be useful.

Here is a link that deals with IP: [www.geop.ubc.ca/ubcgif/tutorials/resip/ip.html](http://www.geop.ubc.ca/ubcgif/tutorials/resip/ip.html).

**Neil Pagel,  
via email**

*I've looked at the IP site you quote, Neil. It's interesting but I'm not sure how the technique might benefit amateur archeologists. Readers – your opinions please!*

*I'm currently in the middle of doing a PIC interface for use with GPS and things like ER and magnetometry – stick around!*

### SONIC FISH

Dear EPE

Just a word on the Babel Fish letter in *Readout* April '03 and hoping it wasn't intended as a joke . . . I remember one of the gadgets in my boyhood. The Tandy 75-in-1 kit was a Sonic Fish Caller – simply a low frequency oscillator, with the loudspeaker waterproofed and suspended in the water. It claimed that fish were attracted to the sound and that professional fishermen used similar devices. I was never interested in fish, but did try it once in a newt-pond. It didn't work – just like most of my projects.

**Nigel Rushbrook,  
via email**

*Well, Nigel, there was humour in what was being said by those who offered comments, but it was not intended to be a commemoration of April 1st! The questioner was really looking for a circuit for a form of depth sounder. Years ago I designed one for use when scuba diving, but the special transducer was too expensive to offer the design for publication.*

*Better luck with future projects you build!*

### REVERED CHEERS FOR ALAN

Dear EPE,

Readers everywhere will surely be sad to see the retirement of Alan Winstanley from *IU*. Over the years, Alan gave the column a common look and feel, and a lighthearted touch, that made it a pleasure to read. It was Alan and *IU* who introduced me to constructional articles, and I know that there are others whose "careers" in electronics were profoundly influenced by him and the column.

So a big thank you Alan, and long live *IU*.

**Rev. Thomas Scarborough,  
South Africa, via email**

*Three cheers for Alan, indeed, Thomas. It is the end of a significant era and Alan's seat will be hard to fill. It is colleague Dave Barrington and I who shall be attempting to continue where Alan left off.*

*Keep those IUs coming in folks – we want to share your ideas with others!*

### BOAT ALARM

Dear EPE

In Graham Johnston's *Letter of the Month*, March '03, he suggested an idea for a boat alarm that sent a message to his mobile phone. This is a good idea, one which a friend of mine thought of about three years ago (although not just for a boat). I designed the electronics for him and he went on to patent the idea (which he still holds). These devices are on the market to protect houses, boats, cars and industrial sites, the latter use radio PIRs and can protect a site of vast area.

I think *EPE* is invaluable and have gained most of my electronic knowledge from it. This brought about the confidence that I had when my friend asked me if I would be able to help him. I undertook the task not knowing whether I had bitten off more than I could chew but I surprised myself and went even further than he had asked. I put that down to reading *EPE* on a regular basis for years.

Keep up the good work guys and if by chance Graham or anyone else wants one of these devices they could contact my friend Roger Clifford at [roger@clifford.freemove.co.uk](mailto:roger@clifford.freemove.co.uk).

**Michael Read,  
via email**

*Thanks Michael for the kind words and the information, plus Roger's address.*

*Enjoy your electronics – and EPE!*

### UNPIC-ING DOS

Dear EPE,

I am currently using PIC Basic PRO and a John Morrison designed software/programmer to develop PIC software. The solution has served me well, but the limitations of the DOS environment are getting painful. Can you recommend a suitable replacement for both the development and the programming which are completely Windows compatible and allow 18, 28 and 40 pin PICs to be programmed?

I am an avid reader of *EPE* and enjoy it thoroughly. I feel, however, that there could be more detail in your circuit descriptions. In terms of the circuit detail, it might help if I explained that I am a qualified but not practicing electronics

technician. I qualified about 15 years ago and really have not used my skills (with the exception of some PIC programming) for the past 10 years. So I use *EPE* to keep in touch not only with modern technology but also with some of the principles which, like my hair, are getting a little grey now.

I am always thinking about what currents are flowing and what voltages I would expect at certain points in the circuit and what would happen if we used a different value capacitor here, etc. I'm sure I get it wrong a lot so it would be useful to know the correct answer. It would also be helpful to know alternative components which could be used (e.g. a 2N3904 where a BC108 is suggested). I appreciate I may be asking a lot and the above may be beyond the scope of *EPE*, but I hope feedback of any kind is not completely useless.

**Simon Smyth,**  
Dublin, via email

Well Simon, feedback is always welcome. Taking your first comment first – you could go the full hog and get Microchip's own system (browse [www.microchip.com](http://www.microchip.com)) or consider my Toolkit TK3 of Oct/Nov '01. Various advertisers also do good programming facilities, as many readers will confirm – browse the adverts. Texts of TK3 are available from our Online Shop via [www.epemag.wimborne.co.uk](http://www.epemag.wimborne.co.uk), or on our PIC Resources CD-ROM advertised in this issue.

I appreciate what you are suggesting, but it would be complex for us to add that extra info as designs are from the readership who don't usually give us that degree of detail. This is why we periodically publish tutorials such as our Teach-In series every two years, and of course our monthly Circuit Surgery. Regarding substitutes, we try to ensure that components are readily available and prefer readers to use those specified by the author.

## STEPPING RIGHT

Dear EPE,

I'm trying to develop a machine which needs several stepper motors and a couple of sensors to make it operate. I'm thinking of controlling (been advised) said machine with a PIC microcontroller. I'm also relatively new to electronics/engineering so I need to know before buying if a PIC is the right way to approach controlling my machine.

I have programmed in BBC Basic a long time ago and would welcome any advice on which programming languages are now available and/or would be easiest, viz a PIC. I also have an Acorn RISC PC as well as a Windows PC. Which would be best to use?

**John Amps,**  
via email

It's a matter of portability, John – it can be portable with a PIC, but not with a PC. Certainly a PIC is the route I would take.

With your previous programming experience you should have no difficulty learning about using PICs. The rest is then just down to you as an electronics designer, and your ability to think straight on software writing!

In terms of PCs I only use Windows and cannot comment on other systems.

## PIC16F62x AND ADC

Dear EPE,

I have recently been working on a circuit requiring analogue to digital conversion. Having seen the PIC16F627 in the Maplin catalogue with pins labelled AN, I had been planning on using this. I have since read the Microchip datasheet for this PIC, and from this understand these pins to be only comparator pins and not strictly A/D. I therefore changed to the PIC16C710, and have written the program to suit.

Since this will be my first PIC project I would rather use a Flash PIC. So I then looked around for methods of programming PICs and discovered *EPE*. Upon reading the April issue I found

## AUTOMATED SURVEYING

*The following are extracts from a series of threads that appeared towards the end of March on our Chat Zone following publication of the Earth Resistivity Logger, started off by Robin Turk:*

**Robin Turk:** I am an archaeology student in UCC Ireland. I was interested to see the *Earth Resistivity Logger* in *EPE* but I am interested in making an automated system for surveying an area, i.e. some kind of radio controlled vehicle for positioning and inserting the probes in the correct positions on the grid and subsequently logging the reading and moving on to the next position.

This would avoid the tedious and time consuming process of positioning probes etc. The actual mechanics of positioning the probes and inserting them would be relatively simple (some probe configurations would be easier than others) but I would need a relatively accurate way to make the device follow a grid pattern over the area to be surveyed. I was thinking maybe GPS or something. I would be grateful for any ideas on the matter!

**John Becker:** A fascinating subject is this "seeing beneath the soil" and what has been proved with my own tests and the surveys by friend Nick Tile (who has professional experience of seismic surveying on land and at sea) encourage me to take the subject further. The next step is probe-less surveying using magnetometry – early field tests on the prototype have started. I have a further idea for remote sensing for a later investigation (following a fair bit of research).

**Robin Turk:** Thanks for cool plan, John. I had another look at Anthony Clarke's *Seeing Beneath the Soil* book the other day and realised that he and others had done work in semi-automated surveys and continuous trace probing methods. In fact using an automated roving device one could achieve an almost continuous trace using either separate probes (in any configuration) with a short distance between each movement, or with probes attached to wheels or tracks (as Miguel suggests below and Clarke used in his design) using the twin electrode method. I look forward to a design for a magnetometry surveying device. It would be nice to be able to incorporate this into a rover as well!

**BWTS:** The roving logger could have a simple representation of the ground to be covered stored in its memory. This representation could be as simple as a rectangle. Each time you want it to go over a piece of ground you enter the dimensions of the rectangle. The logger then trundles off probing every so many metres (or feet if you prefer) in let's say the X direction. Getting to the end of one length it turns 90 degrees, let's say right to avoid confusion, takes a "step" forward in let's say the Y direction, turns another 90 degrees right so it's now facing the direction it came in from.

It repeats the process until it gets to the end of another length and this time turns left, takes a "step", turns left again and repeats the whole thing until it has gone as far in the Y direction as you specified in the first place.

This would avoid the need for external sensors or GPS if the ground to be covered was relatively clear of trees and so on. The hardware would be kept to a minimum and the only input you would have to make would be the X and Y dimensions.

**Robin Turk:** Yes this method would be probably the simplest but it would rely heavily on the accuracy of the measurement of the distance travelled by the rover. These errors would get progressively worse the further it travelled. There would also be problems in achieving an accurate 90 degree turn without the use of some kind of inertial guidance system, although a relatively straight line could probably be achieved by use of a gyro.

**Max:** I think GPS at its most accurate can only pinpoint its location to within about 20cm (I think – but that's plenty accurate enough for its normal uses!), a most accurate way would probably be to use ultrasonic or infra-red sensing to judge the vehicle's position to some fixed markers at the edges of the area being surveyed. It would be a lot easier (and cheaper) than GPS, but would probably need some serious hardware/software to control it, but then I guess it would take a lot of complicated interfacing to get something to interface with a GPS handheld thingy (a technical term).

*A fascinating set of chats (of which there were more, but no space here). As a postscript, by the time you read this I hope to have a GPS input for ER Logger completed. Stay tuned!*

the *Intelligent Garden Lights Controller* was using the PIC16F627, and from what I can tell it is being used for ADC. Could you please tell me how this PIC can be used in this way?

**Joe Dowsett,**  
via email

Disappointingly, Joe, you are right about the PIC16F627 not providing true ADC. In the Garden unit, the PIC's comparator can only be set to one of 16 different analogue input trigger levels, which is very limited. However, the PIC16F87x family have true ADC, providing 1024 levels of conversion. Read Part 3 of my PIC Tutorial V2 in this current issue.

## UPGRADING ATMOSPHERICS MONITOR

Dear EPE,

Regarding my *Atmospherics Monitor* (April '03), during late March/early April atmospheric pressure was very high at 1024mb to 1030mb. Under these conditions, Russian beacons above 9kHz become audible. I have re-worked the aerial input and the first IC1a stage of the monitor. This modification provides a better signal-to-noise floor, improving the resolution of atmospheric signals. The frequency response curve peaks at 7kHz, rolling off steeply above, and provides a gain lift at 2kHz. The modification is as follows:

- Amend C5 to 100nF
- Completely remove C7
- Amend C2 to 22nF and fit 10kΩ resistor in parallel with it
- Remove link wire connecting between stripboard tracks C and I at column 3 and replace by a 220kΩ resistor
- Amend R2 to 390kΩ
- Amend R3 to 470kΩ
- Amend R5 to 3k3Ω
- Amend R6 to 39kΩ
- Add a 47pF capacitor between stripboard tracks F and B in column 1 (between coil wire hole and track to collector of TR1/IC1 pin 5)


After modifying the circuit, the bias will need re-adjustment. With power supply at 9.0V, set VR1 for 4.5V at IC1 output pin 7.

**Brian Lucas,**  
Jersey, via email

*Thanks Brian. Readers, this is the same information as was placed on our Chat Zone in late March.*

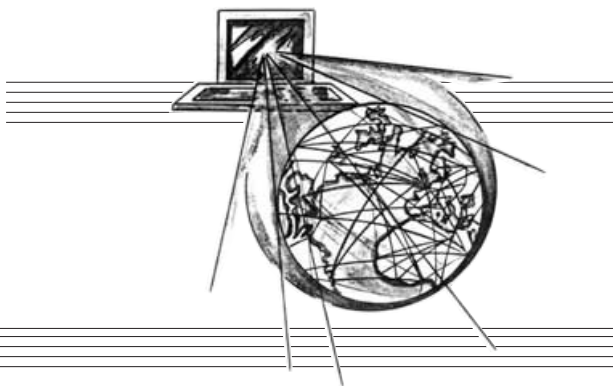*A few of you have commented that PIC subjects are dominant in Readout. That's because most letters received are about PICs. If you want other matters covered please write to us about them.*





## Credit When It's Due

**W**HEN setting up a business that will sell products via the Internet, one of the first obstacles to overcome is that of credit card processing. Much has been written over the past few years about the perils of buying over the Internet: consumers are warned about using only "secure" web sites and not sending credit card numbers through ordinary email.

So far so good, but for the uninitiated Internet user there is still plenty that can go wrong. Faced with the prospect of saving money (lots of money, sometimes), then, when it comes to buying a juicy-looking bargain online, a fool and his money are soon parted, and fools can get their fingers burned very easily. A number of users have been the victims of Internet fraud, losing thousands of pounds through bogus web sites created by fraudsters.

There is a flip side to all this: when opening up an online shop, it is probably the *owner of the business* that faces the greatest challenges from credit card fraud. Flinging open his virtual shop window, orders arrive literally through the ether, sent by customers whom the business will never meet in person. However, when things go wrong the online store faces the risk of losing both the goods as well as the money.

Problems start when the trader sends out the merchandise in good faith, only to learn a month later that the credit card number had actually been stolen or forged. The credit card company might have charged an innocent person's account, which then has to be refunded.

This cash is clawed back from the trader who is compelled to provide the refund (called a chargeback in the trade). This is bad news because the trader has then lost both the goods as well as the cash. Too many chargebacks, and the trader risks losing his merchant account altogether. Security and online vetting procedures are tightening all the time to help avoid this.

## Jump To It

In the UK, a trader (merchant) first needs an "Internet merchant account" to be able to receive credit card (CC) payments online. In practice these accounts are usually arranged via the trader's bank. In addition there are a number of online credit card processing organisations including Netbanx, SecPay, Secure Trading and WorldPay (which in the UK is now part of RBS/Natwest) all of whom can process credit cards for a fee.

Add in standard bank charges as well, and the online business could see no less than three percentages deducted from every deal. Things are somewhat different in the USA where a trader's credit card processing business can be sub-contracted out to any number of competing independent sales organisations.

In view of the almost paranoid risk of chargebacks, money laundering, fraud and theft, it is not surprising that many UK traders are forced to jump through hoops before acquiring an Internet merchant

account. Some alternatives include using a CC processing company (e.g. WorldPay or Netbanx) to handle the transaction in its entirety, i.e. paying a net amount directly into the trader's bank account. It costs money to set up, the interest rates are higher and (worse still) the trader has to wait up to four weeks before receiving his cash, rendering this type of "bureau account" completely unfeasible for many Internet traders who would have to send out the goods but wait a month for their cash to arrive.

## Pay-up Pal

So the viable trading alternatives start to run out. One very tempting option is to use Paypal (<https://www.paypal.com>) to handle all online credit card transactions. The online auctioneer eBay ([www.ebay.com](http://www.ebay.com)) now owns this American credit card processing and payment company, which is why Paypal has been heavily integrated into eBay's checkout system.

On the surface, Paypal appears to be the perfect solution to almost every trader's credit card processing requirements. Paypal claims there are 20 million users in over 30 countries that entrust credit card payment processing to them. Its account-based system lets you send or receive money using a credit card or cheque (checking) account.

It is free to open a Paypal account. "Members" can sign up online in a simple-looking process but finer details become apparent the deeper you dig. In order to validate your details, Paypal makes a \$1.95 test transaction to a designated credit card account: a

nice little earner. A Member ID number is printed alongside the transaction details that appear on the credit card statement, which has to be entered back into the Paypal web site. That is how Paypal confirms your details and you then become a verified member.

By upgrading to a Premier account and entering your bank account details, you suddenly gain the ability to accept credit card payments, because Paypal can process the CC transaction for you and pay the balance straight into your bank account. More accurately, Paypal actually pays the cash into your *Paypal member's account*, from where you can withdraw it into your designated bank account. Paypal deal in several currencies including US\$, Sterling and Euros.

Apart from one glitch when Mastercard locked up my credit card following a series of "suspicious looking" \$1 Paypal payments, I have purchased a number of items using Paypal without any problems. Other users have not been so lucky, especially when they rely on Paypal for their business income. As long as you are mindful of the pitfalls, Paypal may or may not be an ideal solution for the budding Internet start-up or small enterprise.

Next month I'll look in more detail at Paypal, and also show you how you can set up a simple online shop for yourself, using Paypal's selling tools to handle payments. If you have any comments on this topic, you can email me at [alan@epemag.demon.co.uk](mailto:alan@epemag.demon.co.uk).

A screenshot of the PayPal website's account selection page. The page has a blue header with the PayPal logo and navigation links: Welcome, Send Money, Request Money, Shop, and Sell. Below the header, there's a section titled "Which account type is right for you?". It lists three account types: Personal, Premier, and Business, each with a brief description and a link to "Core Features". Below this, there's a section titled "Core Features: Personal, Premier, and Business Accounts" which lists various services like Send Money, Request Money, Auction Tools, Accept payments on your website, and Money Market, each with a brief description.

*Paypal is an account-based online payment system that lets you send or receive money online.*



# PCB SERVICE

Printed circuit boards for most recent *EPE* constructional projects are available from the PCB Service, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for airmail outside of Europe. Remittances should be sent to **The PCB Service, Everyday Practical Electronics, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872; Fax 01202 874562; Email: orders@epemag.wimborne.co.uk. On-line Shop: www.epemag.wimborne.co.uk/shopdoor.htm.** Cheques should be crossed and made payable to *Everyday Practical Electronics* (Payment in £ sterling only).

**NOTE: While 95% of our boards are held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery – overseas readers allow extra if ordered by surface mail.**

**Back numbers or photostats of articles are available if required – see the *Back Issues* page for details. We do not supply kits or components for our projects.**

**Please check price and availability in the latest issue.**

**A number of older boards are listed on our website.**

Boards can only be supplied on a payment with order basis.





PROJECT TITLE	Order Code	Cost
Hosepipe Controller <b>JUNE '01</b>	301	£5.14
Magfield Monitor (Sensor Board)	302	£4.91
Dummy PIR Detector	303	£4.36
★PIC16F87x Extended Memory <b>Software only</b>	—	—
Stereo/Surround Sound Amplifier <b>JULY '01</b>	304	£4.75
Perpetual Projects Uniboard-1	305	£3.00
Solar-Powered Power Supply & Voltage Reg.		
MSF Signal Repeater and Indicator		
Repeater Board	306	£4.75
Meter Board	307	£4.44
★PIC to Printer Interface	308	£5.39
Lead/Acid Battery Charger <b>AUG '01</b>	309	£4.99
Shortwave Loop Aerial	310	£5.07
★Digitimer – Main Board	311	£6.50
– R.F. Board	312	£4.36
Perpetual Projects Uniboard-2		
L.E.D. Flasher — Double Door-Buzzer	305	£3.00
Perpetual Projects Uniboard-3 <b>SEPT '01</b>	305	£3.00
Loop Burglar Alarm, Touch-Switch Door-Light and Solar-Powered Rain Alarm		
L.E.D. Super Torches – Red Main	313	} Set £6.10
– Display Red	314	
– White L.E.D.	315	
★Sync Clock Driver	316	
★Water Monitor	317	£4.91
Camcorder Power Supply <b>OCT '01</b>	318	£5.94
PIC Toolkit Mk3	319	£8.24
Perpetual Projects Uniboard-4. Gate Sentinel, Solar-powered Bird Scarer and Solar-Powered Register	305	£3.00
Teach-In 2002 Power Supply <b>NOV '01</b>	320	£4.28
Lights Needed Alert	321	£5.39
Pitch Switch	322	£5.87
Capacitance Meter – Main Board (double-sided)	323	} Set £12.00
– Display Board (double-sided)	324	
★★PIC Toolkit TK3 – <b>Software only</b>	—	—
4-Channel Twinkling Lights <b>DEC '01</b>	325	£6.82
Ghost Buster – Mic	326	} Set £5.78
– Main	327	
★PIC Polywhatsit – Digital	328	} Set £7.61
– Analogue	329	
Forever Flasher <b>JAN '02</b>	330	£4.44
Time Delay Touch Switch	331	£4.60
★PIC Magick Musick	332	£5.87
Versatile Bench Power Supply	333	£5.71
★PIC Spectrum Analyser <b>FEB '02</b>	334	£7.13
Versatile Current Monitor	335	£4.75
Guitar Practice Amp	336	£5.39
★PIC Virus Zapper <b>MAR '02</b>	337	£4.75
RH Meter	338	£4.28
★PIC Mini-Enigma – <b>Software only</b>	—	—
★Programming PIC Interrupts – <b>Software only</b>	—	—
★PIC Controlled Intruder Alarm <b>APR '02</b>	339	£6.50
★PIC Big Digit Display <b>MAY '02</b>	341	£6.02
Washing Ready Indicator	342	£4.75
Audio Circuits-1 – LM386N-1	343	£4.28
– TDA7052	344	£4.12
– TBA820M	345	£4.44
– LM380N	346	£4.44
– TDA2003	347	£4.60
– Twin TDA2003	348	£4.75
World Lamp <b>JUNE '02</b>	340	£5.71
Simple Audio Circuits-2 – Low, Med and High		
Input Impedance Preamplifiers (Single Trans.)	349	£4.60
Low-Noise Preamplifier (Dual Trans.)	350	£4.75
Tone Control	351	£4.60
Bandpass Filter	352	£4.75
Frequency Standard Generator – Receiver	353	£4.12
– Digital	354	£6.82
★Biopic Heartbeat Monitor	355	£5.71
Simple Audio Circuits – 3 <b>JULY '02</b>		
– Dual Output Power Supply	356	£4.60
– Crossover/Audio Filter	357	£4.44
Infra-Red Autoswitch	358	£4.91
★EPE StyloPIC	359	£6.50
Rotary Combination Lock – Main Board	360	£5.39
– Interface Board	361	£4.91
★Using the PIC's PCLATH Command – <b>Software only</b>	—	—

PROJECT TITLE	Order Code	Cost
Big-Ears Buggy <b>AUG '02</b>	362	£5.71
★PIC World Clock	363	£5.39
Simple Audio Circuits-4 – Low Freq. Oscillator	364	£4.44
– Resonance Detector	365	£4.28
Vinyl-To-CD Preamplifier <b>SEPT '02</b>	366	£5.71
★Freebird Glider Control	367	£4.91
★Morse Code Reader	368	£5.23
Headset Communicator <b>OCT '02</b>	369	£4.75
EPE Bounty Treasure Hunter	370	£4.77
★★Digital I.C. Tester	371	£7.14
★PIC-Pocket Battleships – <b>Software only</b>	—	—
Transient Tracker <b>NOV '02</b>	372	£4.75
★PICAXE Projects-1: Egg Timer; Dice Machine;		
Quiz Game Monitor (Multiboard)	373	£3.00
★Tuning Fork & Metronome	374	£5.39
★★EPE Hybrid Computer – Main Board } double-sided	375	£18.87
– Atom Board	376	£11.57
★PICAXE Projects-2: Temperature Sensor; <b>DEC '02</b>		
Voltage Sensor; VU Indicator (Multiboard)	373	£3.00
★Versatile PIC Flasher	377	£5.07
★PICAXE Projects-3: Chaser Lights <b>JAN '03</b>	373	£3.00
6-Channel Mains Interface	381	£5.08
EPE Minder – Transmitter	378	£4.75
– Receiver	379	£5.39
★Wind Speed Monitor	380	£5.08
Tesla Transformer <b>FEB '03</b>	382	£5.07
★Brainbot Buggy	383	£3.00
★Wind Tunnel	384	£6.02
200kHz Function Generator <b>MAR '03</b>	385	£6.34
Wind-Up Torch Mk II	386	£4.75
★Driver Alert	387	£6.35
★Earth Resistivity Logger <b>APR '03</b>	388	£6.02
★Intelligent Garden Lights Controller	389	£3.96
★PIC Tutorial V2 – <b>Software only</b>	—	—
Door Chime <b>MAY '03</b>	390	£5.07
Super Motion Sensor	391	£5.55
Radio Circuits-1 <b>JUNE '03</b>		
MK484 TRF Receiver	392	£4.44
Headphone Amp.	393	£4.28
★Fido Pedometer	394	£4.91
★PICronos L.E.D. Wall Clock	395	£14.65

## EPE SOFTWARE

Software programs for *EPE* projects marked with a single asterisk ★ are available on 3.5 inch PC-compatible disks or **free** from our Internet site. The following disks are available: **PIC Tutorial** (Mar-May '98); **PIC Tutorial V2** (Apr-June '03); **EPE Disk 1** (Apr '95-Dec '98); **EPE Disk 2** (1999); **EPE Disk 3** (2000); **EPE Disk 4** (2001); **EPE Disk 5** (2002); **EPE Disk 6** (Jan 2003 issue to current cover date – excl. Earth Resistivity); **EPE Earth Resistivity Logger** (Apr-May '03); **EPE Teach-In 2000**; **EPE Spectrum**; **EPE Interface Disk 1** (October '00 issue to current cover date). ★★ The software for these projects is on its own CD-ROM. The 3.5 inch disks are £3.00 each (UK), the CD-ROMs are £6.95 (UK). Add 50p each for overseas surface mail, and £1 each for airmail. All are available from the *EPE PCB Service*. All files can be downloaded **free** from our Internet FTP site: <ftp://ftp.epemag.wimborne.co.uk>.


## EPE PRINTED CIRCUIT BOARD SERVICE

Order Code	Project	Quantity	Price
.....			
Name .....			
Address .....			
.....			
Tel. No. ....			
I enclose payment of £..... (cheque/PO in £ sterling only) to:			
   			
<b>Everyday Practical Electronics</b> <b>MasterCard, Amex, Diners Club, Visa or Switch</b>			
Card No. ....			
Card Exp. Date ..... Switch Issue No .....			
Card Security Code .....			
(The last 3 digits on or just under the signature strip)			
Signature .....			

**NOTE:** You can also order p.c.b.s by phone, Fax, Email or via our Internet site on a secure server:

<http://www.epemag.wimborne.co.uk/shopdoor.htm>

# EPE PIC RESOURCES CD-ROM

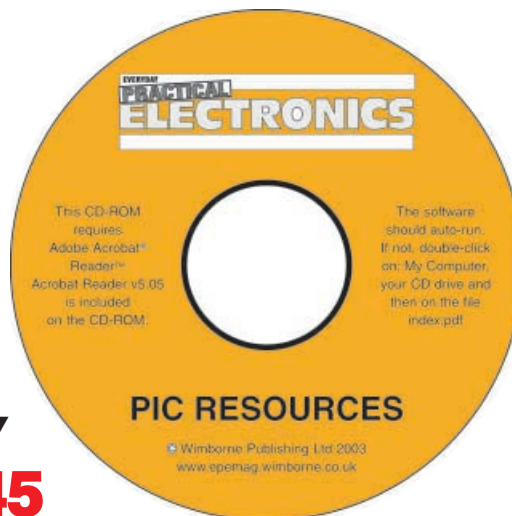

**A companion to the EPE PIC  
Tutorial V2 series of Supplements  
(EPE April, May, June 2003)**

**ONLY  
£14.45**  
INCLUDING  
VAT and P&P

**Contains the following Tutorial-related  
software and texts:**

- EPE PIC Tutorial V2 complete demonstration software, John Becker, April, May, June '03
- PIC Toolkit Mk3 (TK3 hardware construction details), John Becker, Oct '01
- PIC Toolkit TK3 for Windows (software details), John Becker, Nov '01

Plus these useful texts to help you get the most out of your PIC programming:

- How to Use Intelligent L.C.D.s, Julian Ilett, Feb/Mar '97
- PIC16F87x Microcontrollers (Review), John Becker, April '99
- PIC16F87x Mini Tutorial, John Becker, Oct '99
- Using PICs and Keypads, John Becker, Jan '01
- How to Use Graphics L.C.D.s with PICs, John Becker, Feb '01
- PIC16F87x Extended Memory (how to use it), John Becker, June '01
- PIC to Printer Interfacing (dot-matrix), John Becker, July '01
- PIC Magick Musick (use of 40kHz transducers), John Becker, Jan '02
- Programming PIC Interrupts, Malcolm Wiles, Mar/Apr '02
- Using the PIC's PCLATH Command, John Waller, July '02
- EPE StyloPIC (precision tuning musical notes), John Becker, July '02
- Using Square Roots with PICs, Peter Hemsley, Aug '02
- Using TK3 with Windows XP and 2000, Mark Jones, Oct '02
- PIC Macros and Computed GOTOs, Malcolm Wiles, Jan '03
- Asynchronous Serial Communications (RS-232), John Waller, unpublished
- Using I<sup>2</sup>C Facilities in the PIC16F877, John Waller, unpublished
- Using Serial EEPROMs, Gary Moulton, unpublished
- Additional text for EPE PIC Tutorial V2, John Becker, unpublished

NOTE: The PDF files on this CD-ROM are suitable to use on any PC with a CD-ROM drive. They require Adobe Acrobat Reader – included on the CD-ROM

**Order on-line from**

**[www.epemag.wimborne.co.uk/shopdoor.htm](http://www.epemag.wimborne.co.uk/shopdoor.htm)  
or [www.epemag.com](http://www.epemag.com) (USA \$ prices)  
or by Phone, Fax, Email or Post.**

## EPE PIC RESOURCES CD-ROM ORDER FORM

Please send me ..... (quantity) EPE PIC RESOURCES CD-ROM

Price £14.45 each – includes postage to anywhere in the world.

Name .....

Address .....

.....

.....

..... Post Code .....

☐ I enclose cheque/P.O./bank draft to the value of £ .....

☐ Please charge my Visa/Mastercard/Amex/Diners Club/Switch

£ .....

Card No. ....

Card Security Code ..... (The last 3 digits on or just under the signature strip)

Expiry Date ..... Switch Issue No. ....

**SEND TO: Everyday Practical Electronics,  
Wimborne Publishing Ltd.,  
408 Wimborne Road East, Ferndown, Dorset BH22 9ND.  
Tel: 01202 873872. Fax: 01202 874562.  
Email: [orders@epemag.wimborne.co.uk](mailto:orders@epemag.wimborne.co.uk)**

Payments must be by card or in £ Sterling – cheque or bank draft drawn on a UK bank.

Normally supplied within seven days of receipt of order.

Send a copy of this form, or order by letter if you do not wish to cut your issue.

**BECOME A PIC WIZARD WITH THE HELP OF EPE!**

# DIRECT BOOK SERVICE

NOTE: ALL PRICES INCLUDE UK POSTAGE

FREE *Electronics Hobbyist Compendium*  
book with Teach-In 2000 CD-ROM



## EPE TEACH-IN 2000 CD-ROM

The whole of the 12-part *Teach-In 2000* series by John Becker (published in *EPE* Nov '99 to Oct 2000) is now available on CD-ROM. Plus the *Teach-In 2000* interactive software covering all aspects of the series and Alan Winstanley's *Basic Soldering Guide* (including illustrations and Desoldering).

*Teach-In 2000* covers all the basic principles of electronics from Ohm's Law to Displays, including Op.Amps, Logic Gates etc. Each part has its own section on the interactive software where you can also change component values in the various on-screen demonstration circuits.

The series gives a hands-on approach to electronics with numerous breadboard circuits to try out, plus a simple computer interface which allows a PC to be used as a basic oscilloscope.

ONLY **£12.45** including VAT and p&p

Order code Teach-In CD-ROM

### PRACTICAL REMOTE CONTROL PROJECTS Owen Bishop

Provides a wealth of circuits and circuit modules for use in remote control systems of all kinds; ultrasonic, infra-red, optical fibre, cable and radio. There are instructions for building fourteen novel and practical remote control projects. But this is not all, as each of these projects provides a model for building dozens of other related circuits by simply modifying parts of the design slightly to suit your own requirements. This book tells you how.

Also included are techniques for connecting a PC to a remote control system, the use of a microcontroller in remote control, as exemplified by the BASIC Stamp, and the application of ready-made type-approved 418MHz radio transmitter and receiver modules to remote control systems.

160 pages

Order code BP413

£6.49

### DISCOVERING ELECTRONIC CLOCKS W. D. Phillips

This is a whole book about designing and making electronic clocks. You start by connecting HIGH and LOW logic signals to logic gates. You find out about and then build and test bistables, crystal-controlled astables, counters, decoders and displays. All of these subsystems are carefully explained, with practical work supported by easy to follow prototype board layouts.

Full constructional details, including circuit diagrams and a printed circuit board pattern, are given for a digital electronic clock. The circuit for the First Clock is modified and developed to produce additional designs which include a Big Digit Clock, Binary Clock, Linear Clock, Andrew's Clock (with a semi-analogue display), and a Circles Clock. All of these designs are unusual and distinctive.

This is an ideal resource for project work in GCSE Design and Technology: Electronics Product, and for

project work in AS-Level and A-Level Electronics and Technology.

194 pages, A4 spiral bound Order code DEP1 £17.50

### DOMESTIC SECURITY SYSTEMS A. L. Brown

This book shows you how, with common sense and basic do-it-yourself skills, you can protect your home. It also gives tips and ideas which will help you to maintain and improve your home security, even if you already have an alarm. Every circuit in this book is clearly described and illustrated, and contains components that are easy to source. Advice and guidance are based on the real experience of the author who is an alarm installer, and the designs themselves have been rigorously put to use on some of the most crime-ridden streets in the world.

The designs include all elements, including sensors, -detectors, alarms, controls, lights, video and door entry systems. Chapters cover installation, testing, maintenance and upgrading.

192 pages

Order code NE25

£17.95

### MICROCONTROLLER COOKBOOK Mike James

The practical solutions to real problems shown in this cookbook provide the basis to make PIC and 8051 devices really work. Capabilities of the variants are examined, and ways to enhance these are shown. A survey of common interface devices, and a description of programming models, lead on to a section on development techniques. The cookbook offers an introduction that will allow any user, novice or experienced, to make the most of microcontrollers.

240 pages

Order code NE26

£21.99

### A BEGINNER'S GUIDE TO TTL DIGITAL ICs R. A. Penfold

This book first covers the basics of simple logic circuits in general, and then progresses to specific TTL logic integrated circuits. The devices covered include gates, oscillators, timers, flip/flops, dividers, and decoder circuits. Some practical circuits are used to illustrate the use of TTL devices in the "real world".

142 pages

Order code BP332

£5.45

### PRACTICAL ELECTRONICS CALCULATIONS AND FORMULAE F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M.

Bridges the gap between complicated technical theory, and "cut-and-try" methods which may bring success in design but leave the experimenter unfulfilled. A strong practical bias - tedious and higher mathematics have been avoided where possible and many tables have been included.

The book is divided into six basic sections: Units and Constants, Direct-Current Circuits, Passive Components, Alternating-Current Circuits, Networks and Theorems, Measurements.

256 pages

Order code BP53

£5.49

## Computing & Robotics

### WINDOWS XP EXPLAINED N. Kantaris and P. R. M. Oliver

If you want to know what to do next when confronted with Microsoft's Windows XP screen, then this book is for you. It applies to both the Professional and Home editions.

The book was written with the non-expert, busy person in mind. It explains what hardware requirements you need in order to run Windows XP successfully, and gives an overview of the Windows XP environment.

The book explains: How to manipulate Windows, and how to use the Control Panel to add or change your printer, and control your display; How to control information using WordPad, Notepad and Paint, and how to use the Clipboard facility to transfer information between Windows applications; How to be in control of your filing system using Windows Explorer and My Computer; How to control printers, fonts, characters, multimedia and images, and how to add hardware and software to your system; How to configure your system to communicate with the outside world, and use Outlook Express for all your email requirements; How to use the Windows Media Player 8 to play your CDs, burn CDs with your favourite tracks, use the Radio Tuner, transfer your videos to your PC, and how to use the Sound Recorder and Movie Maker; How to use the System Tools to restore your system to a previously working state, using Microsoft's Website to update your Windows set-up, how to clean up, defragment and scan your hard disk, and how to backup and restore your data; How to successfully transfer text from those old but cherished MS-DOS programs.

268 pages

Order code BP514

£7.99

### INTRODUCING ROBOTICS WITH LEGO MINDSTORMS Robert Penfold

Shows the reader how to build a variety of increasingly sophisticated computer controlled robots using the brilliant Lego Mindstorms Robotic Invention System (RIS). Initially covers fundamental building techniques and mechanics needed to construct strong and efficient robots using the various "click-together" components supplied in the basic RIS kit. Explains in simple terms how the "brain" of the robot may be programmed on screen using a PC and "zapped" to the robot over an infra-red link. Also, shows how a more sophisticated Windows programming language such as Visual BASIC may be used to control the robots.

Detailed building and programming instructions provided, including numerous step-by-step photographs.

288 pages - large format

Order code BP901

£14.99

### MORE ADVANCED ROBOTICS WITH LEGO MINDSTORMS - Robert Penfold

Covers the Vision Command System

Shows the reader how to extend the capabilities of the brilliant Lego Mindstorms Robotic Invention System (RIS) by using Lego's own accessories and some simple home constructed units. You will be able to build robots that can provide you with 'waiter service' when you clap your hands, perform tricks, 'see' and avoid objects by using 'bats radar', or accurately follow a line marked on

the floor. Learn to use additional types of sensors including rotation, light, temperature, sound and ultrasonic and also explore the possibilities provided by using an additional (third) motor. For the less experienced, RCX code programs accompany most of the featured robots. However, the more adventurous reader is also shown how to write programs using Microsoft's VisualBASIC running with the ActiveX control (Spirit.OCX) that is provided with the RIS kit.

Detailed building instructions are provided for the featured robots, including numerous step-by-step photographs. The designs include rover vehicles, a virtual pet, a robot arm, an intelligent sweet dispenser and a colour conscious robot that will try to grab objects of a specific colour.

298 pages

Order code BP902

£14.99

### PIC YOUR PERSONAL INTRODUCTORY COURSE SECOND EDITION John Morton

Discover the potential of the PIC microcontroller through graded projects - this book could revolutionise your electronics construction work!

A uniquely concise and practical guide to getting up and running with the PIC Microcontroller. The PIC is one of the most popular of the microcontrollers that are transforming electronic project work and product design.

Assuming no prior knowledge of microcontrollers and introducing the PICs capabilities through simple projects, this book is ideal for use in schools and colleges. It is the ideal introduction for students, teachers, technicians and electronics enthusiasts. The step-by-step explanations make it ideal for self-study too: this is not a reference book - you start work with the PIC straight away.

The revised second edition covers the popular reprogrammable EEPROM PICs: P16C84/16F84 as well as the P54 and P71 families.

270 pages

Order code NE36

£13.99

### INTRODUCTION TO MICROPROCESSORS John Crisp

If you are, or soon will be, involved in the use of microprocessors, this practical introduction is essential reading. This book provides a thoroughly readable introduction to microprocessors, assuming no previous knowledge of the subject, nor a technical or mathematical background. It is suitable for students, technicians, engineers and hobbyists, and covers the full range of modern microprocessors.

After a thorough introduction to the subject, ideas are developed progressively in a well-structured format. All technical terms are carefully introduced and subjects which have proved difficult, for example 2's complement, are clearly explained. John Crisp covers the complete range of microprocessors from the popular 4-bit and 8-bit designs to today's super-fast 32-bit and 64-bit versions that power PCs and engine management systems etc.

222 pages

Order code NE31

£18.99

The books listed have been selected by *Everyday Practical Electronics* editorial staff as being of special interest to everyone involved in electronics and computing. They are supplied by mail order direct to your door. Full ordering details are given on the last book page.

FOR A FURTHER  
SELECTION OF BOOKS  
SEE THE NEXT TWO  
ISSUES OF EPE

All prices include UK  
postage



## Theory and Reference

### ELECTRONICS MADE SIMPLE

Ian Sinclair

Assuming no prior knowledge, *Electronics Made Simple* presents an outline of modern electronics with an emphasis on understanding how systems work rather than on details of circuit diagrams and calculations. It is ideal for students on a range of courses in electronics, including GCSE, C&G and GNVQ, and for students of other subjects who will be using electronic instruments and methods.

Contents: waves and pulses, passive components, active components and ICs, linear circuits, block and circuit diagrams, how radio works, disc and tape recording, elements of TV and radar, digital signals, gating and logic circuits, counting and correcting, micro-processors, calculators and computers, miscellaneous systems.

199 pages

Order code NE23

£13.99

### SCROGGIE'S FOUNDATIONS OF WIRELESS AND ELECTRONICS – ELEVENTH EDITION

S. W. Amos and Roger Amos

Scroggie's Foundations is a classic text for anyone working with electronics, who needs to know the art and craft of the subject. It covers both the theory and practical aspects of a huge range of topics from valve and tube technology, and the application of cathode ray tubes to radar, to digital tape systems and optical recording techniques.

Since *Foundations of Wireless* was first published over 60 years ago, it has helped many thousands of readers to become familiar with the principles of radio and electronics. The original author Sowerby was succeeded by Scroggie in the 1940s, whose name became synonymous with this classic primer for practitioners and students alike. Stan Amos, one of the fathers of modern electronics and the author of many well-known books in the area, took over the revision of this book in the 1980s and it is he, with his son, who have produced this latest version.

400 pages

Order code NE27

£21.99

### GETTING THE MOST FROM YOUR MULTIMETER

R. A. Penfold

This book is primarily aimed at beginners and those of limited experience of electronics. Chapter 1 covers the basics of analogue and digital multimeters, discussing the relative merits and the limitations of the two types. In Chapter 2 various methods of component checking are described, including tests for transistors, thyristors, resistors, capacitors and diodes. Circuit testing is covered in Chapter 3, with subjects such as voltage, current and continuity checks being discussed.

In the main little or no previous knowledge or experience is assumed. Using these simple component and circuit testing techniques the reader should be able to confidently tackle servicing of most electronic products.

96 pages

Order code BP239

£4.49

### PRACTICAL ELECTRONIC FILTERS

Owen Bishop

This book deals with the subject in a non-mathematical way. It reviews the main types of filter, explaining in simple terms how each type works and how it is used.

The book also presents a dozen filter-based projects with applications in and around the home or in the constructor's workshop. These include a number of audio projects such as a rhythm sequencer and a multi-voiced electronic organ.

Concluding the book is a practical step-by-step guide to designing simple filters for a wide range of purposes, with circuit diagrams and worked examples.

188 pages

Order code BP299

£5.49

### PREAMPLIFIER AND FILTER CIRCUITS

R. A. Penfold

This book provides circuits and background information for a range of preamplifiers, plus tone controls, filters, mixers, etc. The use of modern low noise operational amplifiers and a specialist high performance audio preamplifier i.c. results in circuits that have excellent performance, but which are still quite simple. All the circuits featured can be built at quite low cost (just a few pounds in most cases). The preamplifier circuits featured include: Microphone preamplifiers (low impedance, high impedance, and crystal). Magnetic cartridge pick-up preamplifiers with R.I.A.A. equalisation. Crystal/ceramic pick-up preamplifier. Guitar pick-up preamplifier. Tape head preamplifier (for use with compact cassette systems).

Other circuits include: Audio limiter to prevent overloading of power amplifiers. Passive tone controls. Active tone controls. PA filters (highpass and lowpass). Scratch and rumble filters. Loudness filter. Mixers. Volume and balance controls.

92 pages

Order code BP309

£4.49

## Project Building

### ELECTRONIC PROJECTS FOR EXPERIMENTERS

R. A. Penfold

Many electronic hobbyists who have been pursuing their hobby for a number of years seem to suffer from the dreaded "seen it all before" syndrome. This book is fairly and squarely aimed at sufferers of this complaint, plus any other electronics enthusiasts who yearn to try something a bit different.

The subjects covered include: Magnetic field detector, Basic Hall effect compass, Hall effect audio isolator, Voice scrambler/descrambler, Bat detector, Bat style echo location, Noise cancelling, LED stroboscope, Infra-red "torch", Electronic breeze detector, Class D power amplifier, Strain gauge amplifier, Super hearing aid.

138 pages

Order code BP371

£5.45

### PRACTICAL FIBRE-OPTIC PROJECTS

R. A. Penfold

While fibre-optic cables may have potential advantages over ordinary electric cables, for the electronics enthusiast it is probably their novelty value that makes them worthy of exploration. Fibre-optic cables provide an innovative interesting alternative to electric cables, but in most cases they also represent a practical approach to the problem. This book provides a number of tried and tested circuits for projects that utilize fibre-optic cables.

The projects include:- Simple audio links, F.M. audio link, P.W.M. audio links, Simple d.c. links, P.W.M. d.c. link, P.W.M. motor speed control, RS232C data links, MIDI link, Loop alarms, R.P.M. meter.

All the components used in these designs are readily available, none of them require the constructor to take out a second mortgage.

132 pages

Order code BP374

£5.45

### ELECTRONIC MUSIC AND MIDI PROJECTS

R. A. Penfold

Whether you wish to save money, boldly go where no musician has gone before, rekindle the pioneering spirit,

or simply have fun building some electronic music gadgets, the designs featured in this book should suit your needs. The projects are all easy to build, and some are so simple that even complete beginners at electronic project construction can tackle them with ease. Stripboard layouts are provided for every project, together with a wiring diagram. The mechanical side of construction has largely been left to the individual constructors to sort out, simply because the vast majority of project builders prefer to do their own thing.

None of the designs requires the use of any test equipment in order to get them set up properly. Where any setting up is required, the procedures are very straightforward, and they are described in detail.

Projects covered: Simple MIDI tester, Message grabber, Byte grabber, THRU box, MIDI auto switcher, Auto/manual switcher, Manual switcher, MIDI patchbay, MIDI controlled switcher, MIDI lead tester, Program change pedal, Improved program change pedal, Basic mixer, Stereo mixer, Electronic swell pedal, Metronome, Analogue echo unit.

138 pages

Order code PC116

£4.95

### VIDEO PROJECTS FOR THE ELECTRONICS CONSTRUCTOR

NEW LOW PRICE

R. A. Penfold

Written by highly respected author R. A. Penfold, this book contains a collection of electronic projects specially designed for video enthusiasts. All the projects can be simply constructed, and most are suitable for the newcomer to project construction, as they are assembled on stripboard.

There are faders, wipers and effects units which will add sparkle and originality to your video recordings, an audio mixer and noise reducer to enhance your soundtracks and a basic computer control interface. Also, there's a useful selection on basic video production techniques to get you started.

Circuits include: video enhancer, improved video enhancer, video fader, horizontal wiper, improved video wiper, negative video unit, fade to grey unit, black and white keyer, vertical wiper, audio mixer, stereo headphone amplifier, dynamic noise reducer, automatic fader, pushbutton fader, computer control interface, 12 volt mains power supply.

124 pages

Order code PC115

£4.95

## BOOK ORDERING DETAILS

**All prices include UK postage.** For postage to Europe (air) and the rest of the world (surface) please add £2 per book. For the rest of the world airmail add £3 per book. CD-ROM prices include VAT and/or postage to anywhere in the world. Send a PO, cheque, international money order (£ sterling only) made payable to **Direct Book Service** or card details, Visa, Mastercard, Amex, Diners Club or Switch to:

**DIRECT BOOK SERVICE, WIMBORNE PUBLISHING LTD.,  
408 WIMBORNE ROAD EAST, FERNDOWN, DORSET BH22 9ND.**

Books are normally sent within seven days of receipt of order, but please allow 28 days for delivery – more for overseas orders. *Please check price and availability (see latest issue of Everyday Practical Electronics) before ordering from old lists.*

**For a further selection of books see the next two issues of EPE.**

Tel 01202 873872 Fax 01202 874562. Email: [dbs@epemag.wimborne.co.uk](mailto:dbs@epemag.wimborne.co.uk)

**Order from our online shop at: [www.epemag.wimborne.co.uk/shopdoor.htm](http://www.epemag.wimborne.co.uk/shopdoor.htm)**

## BOOK ORDER FORM

Full name: .....

Address: .....

.....

.....

..... Post code: ..... Telephone No: .....

Signature: .....

☐ I enclose cheque/PO payable to DIRECT BOOK SERVICE for £ .....

☐ Please charge my card £ ..... Card expiry date: .....

Card Number ..... Switch Issue No. ....

Card Security Code ..... (the last three digits on or just under the signature strip)

Please send book order codes: .....

.....

Please continue on separate sheet of paper if necessary  
If you do not wish to cut your magazine, send a letter or copy of this form

Everyday Practical Electronics reaches twice as many UK readers as any other UK monthly hobby electronics magazine, our sales figures prove it. We have been the leading monthly magazine in this market for the last eighteen years.

If you want your advertisements to be seen by the largest readership at the most economical price our classified and semi-display pages offer the best value. The prepaid rate for semi-display space is £8 (+VAT) per single column centimetre (minimum 2.5cm). The prepaid rate for classified adverts is 30p (+VAT) per word (minimum 12 words).

All cheques, postal orders, etc., to be made payable to Everyday Practical Electronics. **VAT must be added.** Advertisements, together with remittance, should be sent to Everyday Practical Electronics Advertisements, Mill Lodge, Mill Lane, Thorpe-le-Soken, Essex CO16 0ED. Phone/Fax (01255) 861161.

For rates and information on display and classified advertising please contact our Advertisement Manager, Peter Mew as above.

## TOTALROBOTS

### ROBOTICS, CONTROL & ELECTRONICS TECHNOLOGY

High quality robot kits and components  
UK distributor of the OOPic microcontroller

Secure on-line ordering  
Rapid delivery  
Highly competitive prices

Visit [www.totalrobots.com](http://www.totalrobots.com)

**Tel: 0208 823 9220**

### BTEC ELECTRONICS TECHNICIAN TRAINING

VCE ADVANCED ENGINEERING  
ELECTRONICS AND ICT  
HNC AND HND ELECTRONICS  
NVQ ENGINEERING AND IT  
**PLEASE APPLY TO COLLEGE FOR  
NEXT COURSE DATE**  
FULL PROSPECTUS FROM

**LONDON ELECTRONICS COLLEGE**  
(Dept EPE) 20 PENYVERN ROAD  
EARLS COURT, LONDON SW5 9SU  
TEL: (020) 7373 8721

### LUV-IT-ELECTRONICS COMPONENTS AUCTIONS

June 21st/22nd

SUSSEX - INDOORS

SEE WEB SITE: [www.luv-it-electronics.co.uk](http://www.luv-it-electronics.co.uk)  
or phone 01843 570905  
FREE PARKING - NO CHILDREN

### X-10® Home Automation We put you in control™

#### Why tolerate when you can automate?

An extensive range of 230V X-10 products  
and starter kits available. Uses proven Power  
Line Carrier technology, no wires required.

Products Catalogue available Online.

Worldwide delivery.

#### Laser Business Systems Ltd.

E-Mail: [info@laser.com](mailto:info@laser.com)

<http://www.laser.com>

Tel: (020) 8441 9788

Fax: (020) 8449 0430

### VVT TRANSFORMERS

Transformers and Chokes for all types  
of circuits including specialist valve units  
Custom design or standard range  
High and low voltage

#### Variable Voltage Technology Ltd

Unit 3, Sheat Manor Farm, Chilterton,  
Newport, Isle of Wight, PO30 3HP  
Tel: 0870 243 0414 Fax: 01983 721572

email: [sales@vvt-cowes.freeserve.co.uk](mailto:sales@vvt-cowes.freeserve.co.uk)

[www.vvttransformers.co.uk](http://www.vvttransformers.co.uk)

### BOWOOD ELECTRONICS LTD

Contact Will Outram for your  
Electronic Components

Email: [sales@bowood-electronics.co.uk](mailto:sales@bowood-electronics.co.uk)

Web: [www.bowood-electronics.co.uk](http://www.bowood-electronics.co.uk)

7 Bakewell Road, Baslow, Derbyshire DE45 1RE

Tel/Fax: 01246 583777

Send 41p stamp for catalogue

**GREENWELD**  
Mail Order Specialists  
**ELECTRICAL & ELECTRONIC  
COMPONENTS & KITS, TOOLS,  
MATERIALS & HARDWARE**  
Ask now for  
our FREE  
catalogue  
with the  
latest  
special offers  
Greenweld Limited  
Unit 14 Homdon Industrial Park  
West Homdon • Brentwood • Essex • CM13 3XD  
Tel: 01277 811042 • Fax: 01277 812419  
Email: [bargains@greenweld.co.uk](mailto:bargains@greenweld.co.uk)  
Visit our website: [www.greenweld.co.uk](http://www.greenweld.co.uk)

### TRANSFORMERS

- Custom Wound to Specification
- 1VA-50kVA Single Phase
- 100VA-100kVA + 3 Phase
- A.C. and D.C. Chokes
- H.T. Transformers up to 5kV
- Transformer Kits with Pre-wound Primaries
- Air-Cored Coils up to 1m Diameter
- Transformer Rectifiers
- Motor Generators for Frequency Conversion
- Fast Delivery, Quality Products

Visit [www.jemelec.com](http://www.jemelec.com) for details

Jemelec, Unit 7, Shirebrook Business Park,  
Mansfield, NG20 8RN

**Tel: 0870 787 1769**

### Miscellaneous

**FREE PROTOTYPE PRINTED CIRCUIT  
BOARDS!** Free prototype p.c.b. with quantity  
orders. Call Patrick on 028 9073 8897 for  
details. Agar Circuits, Unit 5, East Belfast  
Enterprise Park, 308 Albertbridge Road, Belfast  
BT5 4GX.

**PRINTED CIRCUIT BOARDS - QUICK  
SERVICE.** Prototype and production artwork  
raised from magazines or draft designs at low  
cost. PCBs designed from schematics.  
Production assembly, wiring and software pro-  
gramming. For details contact Patrick at Agar  
Circuits, Unit 5, East Belfast Enterprise Park,  
308 Albertbridge Road, Belfast, BT5 4GX.  
Phone 028 9073 8897, Fax 028 9073 1802,  
Email [agar@argonet.co.uk](mailto:agar@argonet.co.uk).

**G.C.S.E. ELECTRONICS KITS, TOOLS,**  
pocket money prices. S.A.E. for free catalogue.  
SIR-KIT Electronics, 52 Severn Road, Clacton,  
CO15 3RB. [www.geocities.com/sirkituk](http://www.geocities.com/sirkituk).

**VALVES AND ALLIED COMPONENTS IN  
STOCK** - please ring for free list. Valve equip-  
ment repaired. Geoff Davies (Radio). Phone  
01788 574774.

**BUILD A COMMUNICATIONS RECEIV-  
ER!** Fascinating projects from £10.50. Free cat-  
alogue, 33p sae. QRP, 27 Amberley Street,  
Bradford, W. Yorkshire, BD3 8QZ.

**30 WATT 2030 BRIDGE** mono module com-  
plete with heatsinks. 1-4 @ £17.63 each, 5+ @  
£16.02 each. FCAV. Tel: 01594 564552, Fax  
01594 564556.

**COMPONENTS AND COMPONENT KITS**  
for *Everyday Practical Electronics* projects, and  
more! Visit [www.metastable.electronics.  
btinternet.co.uk](http://www.metastable.electronics.btinternet.co.uk).

## EPE NET ADDRESSES

**EPE FTP site:** <ftp://ftp.epemag.wimborne.co.uk>

Access the FTP site by typing the above into your web browser, or by setting up an FTP  
session using appropriate FTP software, then go into quoted sub-directories:

PIC-project source code files: **/pub/PICS**

PIC projects each have their own folder; navigate to the correct folder and open it, then  
fetch all the files contained within. *Do not try to download the folder itself!*

EPE text files: **/pub/docs**

Basic Soldering Guide: **solder.txt**

Ingenuity Unlimited submission guidance: **ing\_unlt.txt**

New readers and subscribers info: **epe\_info.txt**

Newsgroups or Usenet users advice: **usenet.txt**

Ni-Cad discussion: **nicadfaq.zip** and **nicad2.zip**

Writing for EPE advice: **write4us.txt**

You can also enter the FTP site via the link at the top of the main page of our home site at:

<http://www.epemag.wimborne.co.uk>

Shop now on-line: [www.epemag.wimborne.co.uk/shopdoor.htm](http://www.epemag.wimborne.co.uk/shopdoor.htm)

## ELECTRONICS SURPLUS CLEARANCE SALE

**A DIGITAL HANDHELD LCR METER.** Measuring inductance, capacitance, resistance. LCD display. Range 2mH to 20H inductance. 2000pF to 200µF capacitance. 200 ohm to 20 megohm resistance. Brand new with test leads and manual. **£44.00. P&P £4.**

**12V D.C. TO 240V A.C. 300 WATT POWER INVERTER.** Ideal for use in your caravan, car, boat, to run TV, lighting, fridges, recharge your mobile phone, etc. Compact size, brand new and boxed, fully guaranteed. **£49.50, p&p £6.50.**

**MAGNETIC CREDIT CARD READER.** Keyboard and lap top display system. part of point-of-sale unit. Cost over £150. Our price **£13.50.** Carriage **£7.** Two units for **£35** including carriage.

**DOUBLE-GANG 365+365pF TUNING CAPACITOR.** Plessey, size 1½in. x 1¼in. with slow motion drive, 1½in. long spindle. **£5.00** each. P&P **£1.** Two for **£10.00** post free.

250 ¼ watt metal/carbon film resistors	£1
30 5mm red i.e.d.s	£1
30 BCY71	£1
30 BCY72	£1
30 BFX30	£1
30 BC640	£1
30 BC558	£1
10 OC42 Military spec	£2.50
30 2N4393	£1
10 555 Timer chips	£1

**TO3 FINNED HEATSINK.** 2in. x 2½in. 2 for **£1.**

**100k LOG POTS.** ¼in. spindle, military spec. 2 for **£1.**

**1 MEG LOG POTS.** ¼in. spindle, military spec. 2 for **£1.**

**SINGLE-SIDED COPPER CLAD BOARD.** Size approx. 10in. x 4in. 2 for **£3.**

### VALVE ITEMS

**VALVE BASES.** Octal B7G B9A. **50p** each.

**HIGH VOLTAGE CAPACITORS.** 0.1µF 1000V wkg mixed dielectric axial. 0.05µF 600V wkg axial. 0.68µF 800V wkg Mylar dipped axial. All **60p** each. 1µF 250V wkg axial type, 10 for **£2.00.**

**HIGH VOLTAGE ELECTROLYTICS.** 10µF 250V wkg axial. 22µF wkg axial. 47µF 385V wkg radial. All **50p** each.

**HIGH VOLTAGE ELECTROLYTICS.** 32 + 32µF 450V wkg. **£5** each.

**VINTAGE CARBON ONE WATT RESISTORS.** Useful values. Pack of 50 **£3.00.**

**VINTAGE CARBON ½ WATT RESISTORS.** Pack of 50 **£2.25.**

**FILAMENT TRANSFORMERS.** 6.3V 1.5 amp. mains input, **£5.95.** P&P **£2.00.** 6.3V lamp **£4.95.** P&P **£2.00.**

**MH84 MULLARD VALVE DATA AND EQUIVALENTS HANDBOOK.** Over 300 pages of valve data, base connections, characteristics and operating conditions for Mullard Valves and their equivalent makes. Facsimile reprint **£16.50.** P&P **£3.50.**

### MAINS TRANSFORMERS

**TYPE A.** Mains input, output 230V at 45mA, 6.3V at 1½ amp.

**TYPE B.** Mains input, output 215V at 100mA, 1.3V at 2 amp. **£9.50.** P&P **£4.50.**

**THE ELECTRONICS SURPLUS TRADER** - This is a listing of new first class components and electronics items at below trade prices. Includes manufacturers' surplus and overstocks. Also obsolete semiconductors, valves and high voltage caps and components. Electronic components and books. Send for the catalogue **FREE.**

## (Dept E) CHEVET BOOKS AND SUPPLIES

157 Dickson Road, BLACKPOOL FY1 2EU

Tel: (01253) 751858. Fax: (01253) 302979

Email: chevett@globalnet.co.uk Telephone Orders Accepted

Callers welcome Tuesday, Thursday, Friday and Saturday 10 am to 6 pm

# SQUIRES

## MODEL & CRAFT TOOLS

A COMPREHENSIVE RANGE OF MINIATURE HAND AND POWER TOOLS AND AN EXTENSIVE RANGE OF ELECTRONIC COMPONENTS

FEATURED IN A FULLY ILLUSTRATED

624 PAGE MAIL ORDER CATALOGUE

## 2003 ISSUE

**SAME DAY DESPATCH  
FREE POST AND PACKAGING**

Catalogues: **FREE OF CHARGE** to addresses in the UK. Overseas: CATALOGUE **FREE**, postage at cost charged to credit card

## SHOP EXTENSION NOW OPEN

**Squires, 100 London Road,  
Bognor Regis, West Sussex, PO21 1DD**

TEL: 01243 842424

FAX: 01243 842525



## Autonomous Programmable Robot Kits Accessories - Sensors - Controller Boards

**competition-robotics.com**

Secure on-line ordering. Fast, friendly service.



Web: [www.competition-robotics.com](http://www.competition-robotics.com)

Tel: 01793 636119 Fax: 01793 705772

e-Mail: [sales@competition-robotics.com](mailto:sales@competition-robotics.com)

## YOUR FUTURE LOOKS BRIGHT WITH ICS

Make a real success of yourself by gaining the vital skills and qualifications you need with an ICS home study course. You learn in your own time, at your own pace and from the comfort of your home. And with over 13 million successful students, you'll be joining the most experienced home study school in the world. You can do it with ICS! So why not improve your job prospects today by calling us now or returning the coupon below:

Electrical Contracting & Installation  
Electrical Engineering  
C&G Basic Electronic Engineering  
C&G Basic Mechanical Engineering  
TV & Video Servicing  
Radio & Hi-Fi Servicing  
Refrigeration, Heating & Air Conditioning  
Motorcycle Maintenance

**FREEPHONE 0500 581 557 [www.icslearn.co.uk](http://www.icslearn.co.uk)**

Or write to: ICS, FREEPOST 882, Glasgow, G3 8BR. Tel: Eire call 1800 620 490

Please send me my Free Information on your Technical Courses.

Mr/Ms/Ms/Ms (BLOCK CAPITALS PLEASE)		Date of Birth: / /
Address:		
Postcode:		
Email:		Tel No.:

From time to time, we permit other carefully screened organisations to contact you about products and services. If you prefer not to hear from such organisations please tick box

☐ Dept ZEEVC1E3

## N. R. BARDWELL LTD (Est. 1948)

100	Signal Diodes 1N4148	£1.00
75	Rectifier Diodes 1N4001	£1.00
50	Rectifier Diodes 1N4007	£1.00
10	W01 Bridge Rectifiers	£1.00
10	555 Timer I.C.s	£1.00
4	741 Op Amps	£1.00
50	Assorted Zener Diodes 400mW	£1.00
12	Assorted 7-segment Displays	£1.00
35	Assorted I.e.d.s, various shapes, colours & sizes	£1.00
25	5mm i.e.d.s, red or green or yellow	£1.00
25	3mm i.e.d.s, red or green or yellow	£1.00
75	5mm i.e.d.s, green, 6-5mm legs	£1.00
50	Axial i.e.d.s, 2mcd red Diode Package	£1.00
25	Assd. High Brightness I.e.d.s, var colr	£1.00
20	BC182L Transistors	£1.00
25	BC212L Transistors	£1.00
20	BC237 Transistors	£1.00
30	BC239 Transistors	£1.00
30	BC247 Transistors	£1.00
20	BC547B Transistor	£1.00
30	BC548 Transistors	£1.00
30	BC549 Transistors	£1.00
25	BC557 Transistors	£1.00
30	BC558 Transistors	£1.00
30	BC559 Transistors	£1.00
20	2N3904 Transistors	£1.00
100	1nF 50V wkg Axial Capacitors	£1.00
100	4n7 50V wkg Axial Capacitors	£1.00
80	Assd capacitors electrolytic	£1.00
200	Assd. disc ceramic capacitors	£1.00
50	Assd. Skel Presets (sm, stand, cermet)	£1.00
50	Assd. RF chokes (inductors)	£1.00
50	Assd. grommets	£1.00
10	Assd. crystals - plug in	£1.00
8	Assd. di switches	£1.00
20	Miniature slide switches sp/co	£1.00
8	Assd. push-button switches, multi-bank, multi-pole	£1.00
30	Assd. di sockets up to 40 way	£1.00
10	TV coax plugs, plastic	£1.00
40	metres very thin connecting wire, red	£1.00
20	1in. glass reed switches	£1.00
100	Any one value ¼W 5% of resistors range 1R to 10M	£0.45
10	7812 Voltage Regulators	£1.00
300	Assd. resistors, ¼W/½W, mostly on tapes	£1.00

288 Abbeydale Road, Sheffield S7 1FL

Phone (local rate): 0845 166 2329

Fax: 0114 255 5039

e-mail: [sales@bardwells.co.uk](mailto:sales@bardwells.co.uk) Web: [www.bardwells.co.uk](http://www.bardwells.co.uk)

Prices include VAT/Postage £1.65

44p stamp for lists or disk

POs, Cheques and Credit Cards accepted



## DIGITAL TEST METER

Built-in transistor test socket and diode test position.  
DC volts 200mV to 1000V.  
AC volts 200V to 750V.  
DC current 200mA to 10A.  
Resistance 200 ohms to 2000K ohms.

**£5.99** incl. VAT

SEE OUR WEB PAGES FOR  
MORE COMPONENTS AND  
SPECIAL OFFERS  
[www.bardwells.co.uk](http://www.bardwells.co.uk)